

Power System Simulation with LTspice

Practical Examples, Simulations and Models

Friedrich Schmidt

Version 1.0 Book Template

Power System Simulation with LTspice
Practical Examples, Simulation and Models

Copyright © 2026 Friedrich Schmidt.

All rights reserved. No part of this publication may be reproduced or distributed without permission of the copyright holder, except where permitted by law.

The software names and trademarks mentioned in this book remain the property of their respective owners. The examples are provided for educational purposes. Users are responsible for validating models and results for their own applications.

First working edition, 2026.

*For everyone who wants to understand power systems
by building and testing their own models.*

Preface

This book presents practical methods for modelling and analysing electrical power systems with LTspice. The emphasis is placed on reproducible examples that connect physical interpretation, manual calculation and numerical simulation.

The material is intended for students, engineers and technically interested readers. Each chapter combines a concise theoretical introduction with worked calculations, circuit models, simulation results and practical remarks.

Friedrich Schmidt
Austria, July 2026

Acknowledgements

I would like to express my sincere thanks for the wonderful examples in the book "Dynamic Behavior of Electrical Machines" by Prof. Otto Justus, which provided me with a great deal of inspiration for my own book.

Contents

Preface	vii
Acknowledgements	ix
List of Figures	xv
List of Tables	xix
List of Listings	xxi
1 Transformer and Shunt Reactor	1
1.1 General	1
1.2 Circuit Design	1
1.2.1 Transformer Without Shunt Reactor	2
1.2.2 One Transformer and Shunt Reactor	2
1.2.3 Two Transformers in Parallel and Shunt Reactor	2
1.2.4 Two Transformers in Series and Shunt Reactor	2
1.2.5 Transformer and Shunt Reactor for AC-Analysis	3
1.3 Manual Calculation for line to line voltage drop in case of two transformers in series	3
2 Short-Circuit Current in the Medium-Voltage Grid	7
2.1 General	7
2.2 Circuit Design	7
2.3 Transient Simulation	8
2.3.1 Before the Fault	8
2.3.2 Fault Inception	8
2.3.3 Settled Fault Current	8
2.4 Estimating the Steady-State Short-Circuit Current	8
2.5 Short-Circuit Current with Initial Load	9
2.6 Short-Circuit Reactor	9
2.6.1 Manual Calculation	10
2.7 AC Analysis	10
3 Initializing Transformers with Residual Flux	17
3.1 General	17
3.2 Circuit Design	17
3.3 Energization at 40 ms Without Residual Flux	18
3.4 Energization at 40 ms with Unfavourable Residual Flux	19
3.5 Energization at 40 ms with Favourable Residual Flux	19
3.6 Energization at 45 ms with Unfavourable Residual Flux	20
4 Switching Lines	23
4.1 General	23
4.2 Circuit Design	23
4.2.1 Adjustment of the Petersen Coil	23

4.3	Energization of an Unloaded 110 kV Cable	24
4.3.1	Natural Frequency	24
4.3.2	Petersen-Coil Oscillation	25
4.4	Energization of a Loaded Line	25
4.5	Energization of a Second Line	25
4.6	Energization of a Transformer-Terminated Line	26
4.7	Extended-Line Study: Charging Current Near Rated Current	26
5	Earth Faults in 110 kV and 10 kV Power Grids	33
5.1	General	33
5.2	Circuit design	33
5.3	Compensated 110 kV Network Without a Fault	33
5.3.1	Adjustment of the Petersen Coil	33
5.3.2	Neutral Displacement Voltage in the Transient Analysis	34
5.3.3	Corrected Petersen-Coil Setting	34
5.3.4	Reason about the reduction of the starpoint voltage	34
5.3.5	Resonant Frequency at about 50Hz	35
5.4	Low-Resistance Earth Fault in the 110 kV Network	36
5.4.1	Network Designed for 300 A Earth-Fault Current	36
5.4.2	Reactive Power detailed	37
5.4.3	Reactive-Power Increase at Fault Inception	37
5.4.4	Additional Transformer Loading with Petersen current	37
5.4.5	Loaded and Unloaded Transformer	38
5.5	High-Resistance Earth Fault	38
5.6	Comparison of coupled and uncoupled line impedance	38
5.7	Compensated 10 kV Network with a grounding Transformer	38
5.8	Solid starpoint earthing and transformer with fiveleg magnetic core	39
5.9	Characteristic Resonance Frequencies	39
5.9.1	Resonance at 1.2 kHz	39
5.9.2	Resonance at 260 Hz	39
6	Switching Whole Networks	51
6.1	General	51
6.2	Circuit Design	51
6.3	Petersen-Coil Setting	51
6.4	Calculation of the Network Resonance	52
6.5	Rated current of the main transformer	52
6.6	Case 1: Closing at the Phase-R Voltage Zero	53
6.7	Case 2: Closing at the Phase-R Voltage Maximum	57
6.8	Case 3: Closing at Voltage Zero with Full Residual Flux	60
6.9	Case 4: Main-Transformer Tap Position L+13	63
6.10	Case 5: Energizing a Larger Network	67
6.11	Case 6: Energization with Load	71
6.12	Case 7: Skin-Effect Model	74
6.13	Case 8: Energization from a Weak Network	74
6.14	Case 9: Network Startup by a Voltage Ramp	75

7	Coupled Lines with Resonance	81
7.1	General	81
7.2	Circuit design	81
7.3	Determining the Compensation Rating	81
7.4	Line 1 Energized and Line 2 Open: Untransposed Lines	82
7.5	AC Analysis of the Untransposed Open Line	84
7.5.1	Exercises	84
7.6	Line 1 Energized and Line 2 Open: Transposed Lines	84
7.7	AC Analysis of the Transposed Open Line	87
7.8	Line 2 Initially Grounded and Then Ungrounded	87
7.9	Line 2 Energized and Subsequently Switched Off	89
7.10	Line 2 Switched Off Without a Compensation Reactor	89
7.11	Stored Energy on the Open Line	92
A	Synchronous Generator Model	94
B	Transformer Model	105
C	Behavioral Sources in LTspice	119
C.1	Behavioral E and G Sources	119
C.2	Functions in Behavioral Expressions	119
C.3	Operators and Precedence	121
C.4	Example: Single-Phase Transformer	122
C.4.1	Differential equations	122
C.4.2	Flux-current equations	122
C.4.3	LTspice netlist	123
D	Installing LTspice and the Toolboxes	125
D.1	Purpose and Required Downloads	125
D.2	Installing LTspice 24.0.12	125
D.3	Installing the Toolboxes	126
D.4	Configuring Search Paths	126
D.5	Configuring the Simulator	128
D.5.1	SPICE tab	128
D.5.2	Save Defaults tab	129
D.5.3	Schematic tab	130
D.5.4	Waveforms tab	130
D.5.5	Operation tab	131
D.6	Verifying the Installation	132
E	Q&A: Transient Simulation	133
E.1	Basic Simulation Setup	133
E.2	Transformer Models and Magnetic Quantities	134
E.3	Selecting and Analysing Models	137
E.4	Inductive Coupling and Flux	138
E.5	Lines, Cables, and Compensation	140
E.6	Plot Files and Verification	142

F	LTspice Schematic Editor	145
F.1	Main Areas of the Schematic Editor	145
F.2	Menu Bar	145
F.3	Toolbar Symbols	147
F.4	Basic Workflow	147
F.5	References	148
Index		153
About the Author		155

List of Figures

1.1	Transformer and shuntreactor schematic	5
1.2	AC voltages and currents at the shunt reactors.	6
2.1	Shortcircuit in the medium voltage grid - schematic	12
2.2	Shortcircuit in the medium voltage grid - waveform	12
2.3	Shortcircuit in the medium voltage grid with initial load - schematic	13
2.4	Shortcircuit in the medium voltage grid with initial load - waveform	13
2.5	Shortcircuit in the medium voltage grid with scr - schematic	14
2.6	Shortcircuit in the medium voltage grid with scr - waveform	14
2.7	Shortcircuit in the medium voltage grid AC analysis - schematic	15
2.8	Shortcircuit in the medium voltage grid AC analysis - waveform	15
3.1	Initializing Transformer with residual flux - schematic	21
3.2	Initializing Transformer with residual flux - Currents	21
3.3	Initializing Transformer with residual flux - Fluxes	22
4.1	Switching lines - schematic	28
4.2	Switching lines1 - waveform	28
4.3	Switching lines2 - waveform	29
4.4	Switching lines3ab - waveform	29
4.5	Switching lines4 - waveform	30
4.6	Switching lines 15s - waveform	30
4.7	Switching lines 70km - schematic	31
4.8	Switching lines 70km - waveform1	31
4.9	Switching lines 70km - waveform2	32
5.1	Petersen without fault - schematic	40
5.2	Petersen without fault TRAN - waveform	40
5.3	Petersen without fault AC starpoint (Petersen) voltage - waveform	41
5.4	Petersen with fault AC hierarchical model - waveform	41
5.5	Phasedifference of the phase voltages U0B,U0C drawn with GeoGebra	42
5.6	Petersen with fault TRAN - schematic	42
5.7	Petersen with fault TRAN - waveform	43
5.8	Petersen with fault AC - waveform	43
5.9	Petersen with fault and load AC - schematic	44
5.10	Petersen with fault and load AC - waveform	44
5.11	Petersen with highohmic fault AC - schematic	45
5.12	Petersen with highohmic fault AC - waveform	45
5.13	Petersen with fault and load AC - schematic	46
5.14	Petersen with fault and load AC - waveform	46
5.15	Petersen without fault and external petersen starpoint TRAN - schematic	47
5.16	Petersen without fault and external petersen starpoint TRAN - waveform	47
5.17	Petersen without fault and external petersen starpoint AC - schematic	48
5.18	Petersen without fault and external petersen starpoint AC - waveform	48
5.19	FFT of current through capacitor C11	49

6.1	Switching on networks schematic	54
6.2	Switching on networks voltages - case1	54
6.3	Switching on networks currents - case1	55
6.4	Switching on networks currents line1, line4 - case1	55
6.5	Switching on networks fluxes - case1	56
6.6	Switching on networks FFT - case1	56
6.7	Switching on networks voltages - case2	58
6.8	Switching on networks currents - case2	58
6.9	Switching on networks currents line1, line4 - case2	59
6.10	Switching on networks fluxes - case2	59
6.11	Switching on networks voltages - case3	61
6.12	Switching on networks currents - case3	61
6.13	Switching on networks currents line1, line4 - case3	62
6.14	Switching on networks fluxes - case3	62
6.15	Switching on networks voltages - case4	64
6.16	Switching on networks currents - case4	64
6.17	Switching on networks currents line1, line4 - case4	65
6.18	Switching on networks fluxes - case4	65
6.19	Switching on networks FFT - case4	66
6.20	Switching on networks voltages - case5	68
6.21	Switching on networks currents - case5	68
6.22	Switching on networks currents line1, line4 - case5	69
6.23	Switching on networks fluxes - case5	69
6.24	Switching on networks FFT - case5	70
6.25	Switching on networks voltages - case6	71
6.26	Switching on networks currents - case6	72
6.27	Switching on networks currents line1, line4 - case6	72
6.28	Switching on networks fluxes - case6	73
6.29	Switching on networks voltages - case7	74
6.30	Switching on networks voltages - case8	75
6.31	Switching on networks voltages - case9	76
6.32	Switching on networks currents - case9	76
6.33	Switching on networks currents line1, line4 - case9	77
6.34	Switching on networks fluxes - case9	77
6.35	Switching on networks FFT - case9	78
7.1	Coupled lines resonance - Sum of voltages not zero - scale*1e5	82
7.2	Coupled lines resonance schematic - Lines2 is open untransposed TRAN analysis	83
7.3	Coupled lines resonance TRAN - Lines2 is open untransposed TRAN analysis . .	83
7.4	Coupled lines resonance schematic - Lines2 is open untransposed AC analysis . .	85
7.5	Coupled lines resonance AC - Lines2 is open untransposed	85
7.6	Coupled lines resonance schematic - Lines2 is open transposed - TRAN analysis .	86
7.7	Coupled lines resonance TRAN - Lines2 is open transposed	86
7.8	Coupled lines resonance schematic Lines2 is open transposed	87
7.9	Coupled lines resonance AC - Lines2 is open transposed	88
7.10	Coupled lines resonance TRAN line2 grounded than ungrounded	88
7.11	Coupled lines resonance TRAN line2 grounded than ungrounded	89

7.12	Coupled lines resonance TRAN line2 switched off schematic	90
7.13	Coupled lines resonance TRAN line2 switched off	90
7.14	Coupled lines resonance TRAN line2 switched off without shunt reactor schematic	91
7.15	Coupled lines resonance TRAN line2 switched off without shunt reactor	91
7.16	Coupled lines resonance TRAN line2 stored energy schematic	92
7.17	Coupled lines resonance TRAN line2 stored energy	93
A.1	Synchronous machine schematic model	99
A.2	Matlab Listing for converting standard to fundamental parameters	103
A.3	Matlab Listing for converting standard to fundamental parameters used in LTspice model	104
B.1	Three phase three leg Yy0 transformer magnetic and electrical model (with magnetic tank reluctance)	113
B.2	One winding and one leg of the transformer model	114
D.1	Symbol and Library search path tab	128
D.2	Spice tab	129
D.3	Save defaults tab	129
D.4	Schematic tab	130
D.5	Waveforms tab	130
D.6	Operation tab	131
F.1	Annotated LTspice 24 schematic-editor window showing the title and menu bars, functional toolbar groups, schematic drawing area, grid, and status bar. The appearance of individual icons depends on the selected toolbar style and LTspice version.	146
F.2	Most used symbols for transient toolbox	149

List of Tables

6.1	signal values case1, min-max values are all peak values, but Bus0-Bus1 values are RMS values	57
6.2	signal values case2, min-max values are all peak values, but Bus0-Bus1 values are RMS values	60
6.3	signal values case3, min-max values are all peak values, but Bus0-Bus1 values are RMS values	63
6.4	signal values case4, min-max values are all peak values, but Bus0-Bus1 values are RMS values	66
6.5	signal values case5, min-max values are all peak values, but Bus0-Bus1 values are RMS values	70
6.6	signal values case6, min-max values are all peak values, but Bus0-Bus1 values are RMS values	73
6.7	signal values case9, min-max values are all peak values, but Bus0-Bus1 values are RMS values	78
C.1	Functions available in LTspice behavioral expressions.	120
C.2	LTspice behavioral-expression operators in ascending order of precedence.	121
D.1	Required LTspice symbol and library search paths.	128
D.2	Summary of the recommended LTspice settings.	131

List of Listings

A.1	Behavioral implementation of a synchronous generator.	100
B.1	Behavioral implementation of a three-phase transformer.	115
C.1	Behavioral implementation of a single-phase transformer.	123

1 Transformer and Shunt Reactor

1.1 General

In the first example, a three-phase circuit is examined. The case of an inductive load, namely the switching-on of a shunt reactor, and its impact on the voltage are investigated. The load is energized first by one transformer and then by two transformers. Finally, a special case with two transformer in series is presented. Such a configuration can occur when a de-energized part of a network is restored from a network section that is already energized (for instance after a blackout). For the transient (.TRAN) analysis the example filename is `Transformer_and_shunt_reactor.asc`. Additional measurements defined with `.meas` in the ltspice schematic are written to the `spice-output-logfile` file at the end of the simulation. In LTspice, this file can be opened with *View → SPICE Output Log*. To set simulation accuracy for voltages and currents the LTspice netlist settings are:

```
.options vntol=1m  
.options abstol=1u
```

These values are much higher as at normal LTspice simulations with electronic circuits.

Remark 1.1 – (Convergence)

If you walk into convergence issues you can try to set `vntol` and `abstol` to higher values. You can also try to set the relative tolerance `reltol` to 0.01. Changing the default integration mode can also be helpful.

The following line for frequency and angular velocity should be included in every schematic:

```
.param tdv=1 tdt=1 fn1=50Hz(60Hz) omega_n={2*pi*fn1}
```

`tdv=1` and `tdt=1` are LTspice parameters used to avoid convergence problems with high energy networks

1.2 Circuit Design

This first example contains buses, an impedance, transformers, and shunt reactors. The bus elements provide external measurement pins and the setting for the line-to-line voltage. Elements with three pins, such as `bus_v`, measure all three phase line to line voltages as instantaneous values (`bus_v`) or RMS-values (`bus_Veff`). During simulation the RMS values require some time to settle.

Two types of impedance models (`impedance` and `impedance_sk`) are available. One model uses separate values of resistance and inductance for each phase. The other model uses nominal voltage and short-circuit power as inputs, assuming equal values for all phases. The `impedance_sk` symbol is placed on the schematic and the values for SN and UN should be:

```
SN=40e9
UN=400k
```

The transformer model used in this circuit is a simple linear model without a magnetic core, because a nonlinear core is not required for this example. After placing the symbol `trafo_yy`, the model `RUYy0_400k_120k_300MVA_simple` is selected under `spicemodel` (double click for dropdown list) in the attribute editor. Other default parameter lines are removed.

The three-phase voltage source is started with exponential damping using the parameter `Texp=50ms`. This accelerates the settling of the current of the shunt reactor. The shunt reactor has a rating of 50 Mvar and a nominal voltage of 110 kV. Its nominal current is approximately 250 A RMS. The total simulation time is set to 1 500 ms. Only the final 500 ms are saved, because data storage begins at 1 000 ms.

This is set by the `.tran` command of `ltspice`

```
.tran 0 1500m 1000m 0.1m
```

0.1m means the maximal timestep is 0.1ms and should be small enough to simulate/output accurate sine waves at 50/60Hz. For higher frequencies this time step should be set smaller.

1.2.1 Transformer Without Shunt Reactor

The voltage at the shunt-reactor bus is approximately 119.7 kV. Thus, the nominal voltage of 120 kV is nearly reached. The small difference is caused by the series impedance of the network, which slightly reduces the voltage.

1.2.2 One Transformer and Shunt Reactor

In this case, the shunt reactor reduces the voltage to approximately 115.2 kV. The RMS current is approximate 275 A. This is higher than the rough estimate of 250 A, because the operating voltage is higher than the nominal voltage of the shunt reactor.

1.2.3 Two Transformers in Parallel and Shunt Reactor

With two transformers connected in parallel, the equivalent internal impedance is reduced by a factor of two. Consequently, the voltage drop is smaller, and the voltage reaches approximately 117.5 kV. The current through the shunt reactor increases to approximate 280 A because of the higher operating voltage.

1.2.4 Two Transformers in Series and Shunt Reactor

The shunt reactor is now supplied from a 120 kV source through two transformers connected in series. The transformer impedance is therefore doubled, and the voltage is reduced from 119.2 kV to approximately 110.5 kV which is a delta of 8.7 kV. The shunt-reactor current is approximate 264 A. This configuration can arise when a de-energized part of a network is restored from a network section that remains energized (for instance after a blackout). Because of the high sum of transformer impedance the voltage acts particularly sensitive at this configuration

1.2.5 Transformer and Shunt Reactor for AC-Analysis

For an AC analysis the filename of the example is `Transformer_and_shunt_reactor_AC.asc`. For the AC analysis, the voltage-source model is changed to `V_3phase_AC`. The transient-analysis directive `.tran` is replaced by an `.ac` directive. For measuring the bus voltages the transient bus models has to be exchanged with the appropriate ac bus models `bus_V` with `bus_V_AC` for line to line voltages and `bus_Veff` with `bus_V0_AC` for line to earth voltages.

Important 1.1 – (AC-Analysis)

AC-Analysis works only for examples with linear elements !! (e.g linear Transformers)

1.3 Manual Calculation for line to line voltage drop in case of two transformers in series

The internal impedance of a 400 kV/120 kV transformer is approximately 9.6Ω inductive when referred to the secondary side. (See equation 1.9). For two transformers connected in series, the total impedance is therefore approximately

Calculation 1.1 – (Voltage reduction)

$$X_{T,tot} = 2 \cdot 9.6 \Omega = 19.2 \Omega. \quad (1.1)$$

With a current of approximately 264 A, the phase-voltage drop is

$$\Delta U_{ph} = I X_{T,tot} \quad (1.2)$$

$$= 264 \text{ A} \cdot 19.2 \Omega \quad (1.3)$$

$$= 5 \text{ kV}. \quad (1.4)$$

The corresponding line-to-line voltage drop is approximately

$$\Delta U_{LL} = \sqrt{3} \Delta U_{ph} \quad (1.5)$$

$$\approx 1.73 \cdot 5 \text{ kV} \quad (1.6)$$

$$\approx \boxed{8.65 \text{ kV}} \quad (1.7)$$

This result agrees well with the simulated voltage reduction in Section 1.2.4.

To get the value of the leakage impedance of the transformer see the output log file where we search for the leakage inductance of e.g. transformer1 (the ohmic part is neglected). Then we can compute the leakage inductance times the angular velocity at 50Hz which is 314.159 to get the impedance. We are searching for `1:trafo1:u:1p` which is `l1p` the primary reactance with the value `1.6976e-01`.

Alternatively you can see the wxmaxima file `transformer_400kV_120kV.yy.wxmx` and search for `L1s` Now we can compute: `X1s` related to the high voltage side and `X2s` related to the low voltage side of the transformer:

Calculation 1.2 – (Leakage impedance)


$$\begin{aligned}X_{1s} &= L_{1s} \omega \\&= 0.1697 \cdot 314.159 \\&= 53.33 \, \Omega\end{aligned}\tag{1.8}$$

$$\begin{aligned}X_{2s} &= X_{1s} \frac{(120 \, \text{kV})^2}{(400 \, \text{kV})^2} \\&= \boxed{9.60 \, \Omega}\end{aligned}\tag{1.9}$$

Transformer and shuntreactor AC-Analysis

```
.param tdv=1 tdt=1 fn1=50 omega_n={2*pi*fn1} ; should always be present
.options numdgt=10 plotwinsize=0 ; for accuracy .meas statements
.options vntol=1m abstol=1u ; for accuracy voltage and current
.options meascplxfmt=polar ; for meas AC values in polar format
.options logparams ; To put input parameters of all devices to the log file
```

```
.ac list 49.999 50 50.001
```

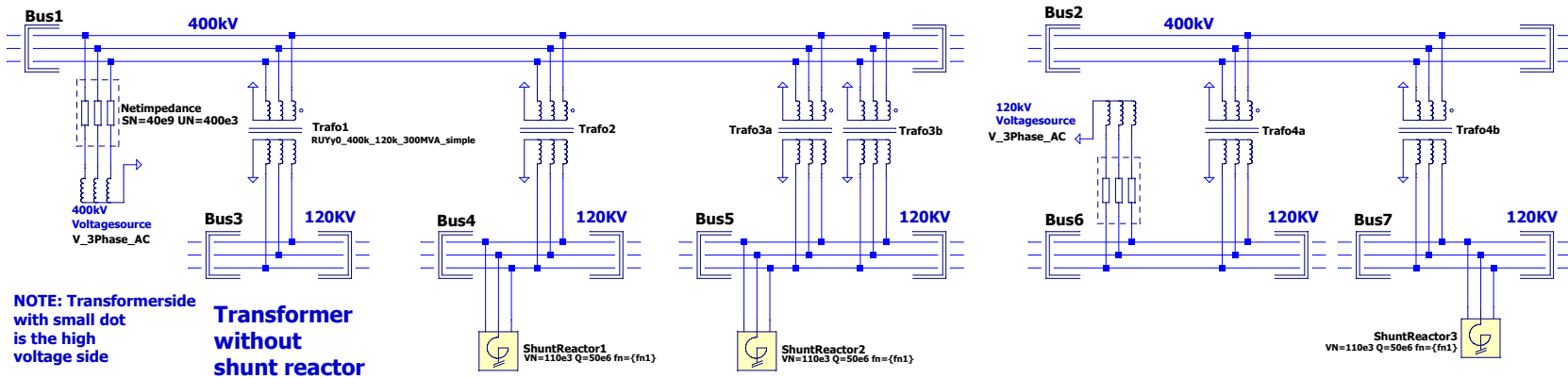

See the measurements:
Activate schematic window
View->Spice Output log
Scroll to the end of the file

```
; Reactive powers: (at Shuntreactor 1,2,3)
.meas AC QSR_1 FIND 3*Ix(ShuntReactor1:L1)*v(bus4a:L1) at 50
.meas AC QSR_2 FIND 3*Ix(ShuntReactor2:L1)*v(bus5a:L1) at 50
.meas AC QSR_3 FIND 3*Ix(ShuntReactor3:L1)*v(bus7a:L1) at 50
; Voltages: (at Shuntreactor 1,2,3)
.meas AC VSR_1 FIND v(bus4:L1) at 50
.meas AC VSR_2 FIND v(bus5:L1) at 50
.meas AC VSR_3 FIND v(bus7:L1) at 50
; Currents: (at Shuntreactor 1,2,3)
.meas AC ISR_1 FIND Ix(ShuntReactor1:L1) at 50
.meas AC ISR_2 FIND Ix(ShuntReactor2:L1) at 50
.meas AC ISR_3 FIND Ix(ShuntReactor3:L1) at 50
```

To see the simulation voltage results simply click on the lines
To see the currents click on the input pins of the device
The left buses measurement pins shows the line to line voltages
The right buses measurement pins shows the line to ground voltages

Figure 1.1: Transformer and shuntreactor schematic

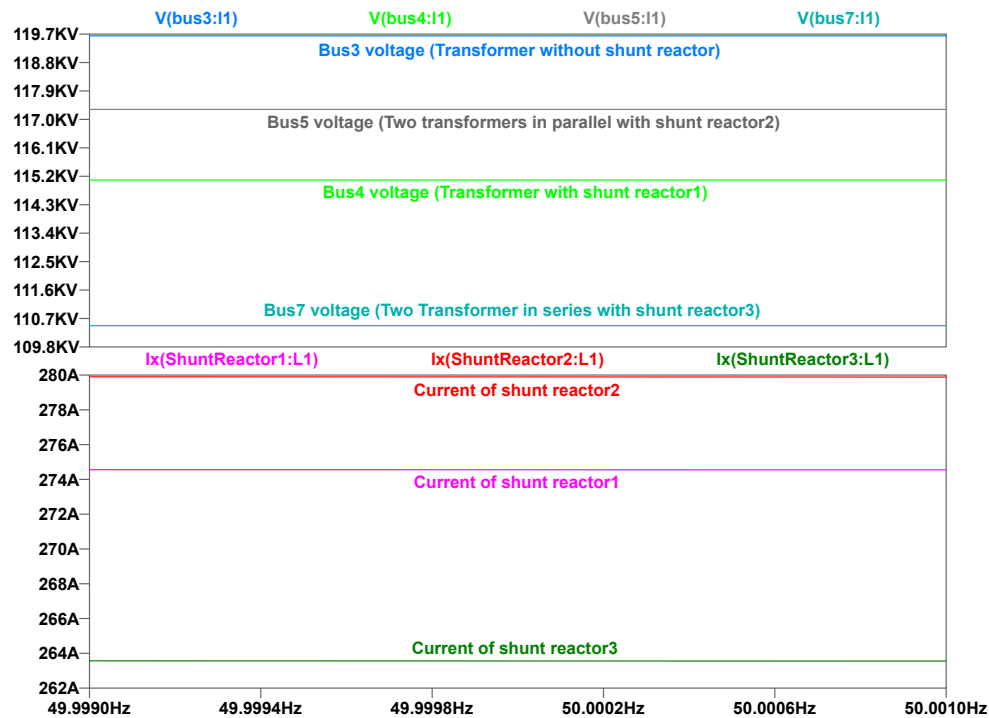


Figure 1.2: AC voltages and currents at the shunt reactors.

Chapter Summary

Shunt reactors are used to regulate the voltage in a power grid. It operates as standalone device or is switched to the tertiary winding of a high voltage transformer. In this chapter, we have seen that loading a circuit with a shunt reactor reduces the voltage in direction to the shunt reactor. This voltage reduction occurs whenever an inductive current flows through transformers or the line impedance, which is also highly inductive. As a rule of thumb, inductive reactive power flows always from the higher voltage level to the lower voltage level. When the transformer is loaded with pure active power, active power always flows from the larger voltage angle to the smaller voltage angle. Real-world example: After energizing a power district via two transformers in series, the voltage is highly volatile. It is best to energize the power district with balanced reactive power. Voltage regulation in the power district should be performed using the regulating transformers and not the shunt reactor.

2 Short-Circuit Current in the Medium-Voltage Grid

2.1 General

This example investigates the short-circuit current close to a substation when two medium-voltage transformers, each rated at 40 MVA, are operated in parallel. The transient simulation is compared with simple manual estimates. The influence of an initial load and an additional short-circuit reactor is then examined, followed by a steady-state AC analysis.

2.2 Circuit Design

This example introduces the line device. Depending on the selected model, this device represents either an overhead line or an underground cable. Here, an oil-insulated underground cable with a conductor cross-section of 500 mm^2 is assumed.

After placing the line element, open its attribute window by right-clicking the symbol. Double-click the `SpiceModel` field and select the required model. Delete the attributes `Value2`, `SpiceLine`, and `SpiceLine2`. In the `Value` attribute, change the length parameter from 1 to 3, corresponding to a line length of 3 km.

The high-voltage transformer uses the model `RUYyo_400k_120k_300MVA_simple`, as in the preceding example. Its 400 kV side is permanently grounded, whereas the 120 kV side is isolated. The tap changer is set to L+3 using

```
l_=3 (transformer tap value, pos. sign lower secondary voltage, neg. sign  
      higher secondary voltage)  
stproz=1.5 (percentual nominal voltage change per transformer tap)
```

so that the secondary voltage is approximately 115 kV.

For the medium-voltage transformers, select the model `RUYd5_110k_10k_40MVA`. Their relative short-circuit voltage (ohmic part neglected) is set to 18 % with

```
ux=0.18 (uk=sqrt(ux*ux+ur*ur))
```

The star points on the medium voltage transformers at the 110 kV side are grounded through a Petersen coil, represented by the additional circuit element `pet`. The two 110 kV lines are assumed to be compensated by this coil. One cable produces an earth-fault current of approximately 76 A; This can be verified by deleting all the circuit elements after the line elements. Now simulate the circuit `Shortcircuit_Current.asc` and measure the peak current into the line by dividing the peak current by 1.414 and multiply it by 3. The earth faultcurrent can now be seen in the waveformviewer. The Petersen coil is rated at 150 A ($\sim 2 \times 76 \text{ A}$) and is connected to both transformer neutral points. Measuring the Petersen voltage you see the swing in by changing slowly the height of the voltage. This is because of the small under/over compensation of the Petersen.

To obtain a realistic voltage across the Petersen coil, the phase-1 capacitance of line 1 is changed from 400 nF to 401 nF. This introduces a small asymmetry. A Petersen coil is in this example not modelled on the 10 kV side. Because the transformer secondary is delta-connected, a neutral point would be created with the star-point builder `Trafo_gnd` element, connected to the transformer secondary terminals.

The earth-fault element `fault_earth` is also introduced. It is switched on at 500 ms by setting

```
t_start=500m
```

Remark 2.1 – (Model asymmetry)

The deliberate 1 nF capacitance difference prevents a perfectly symmetrical zero-voltage condition across the Petersen coil.

2.3 Transient Simulation

2.3.1 Before the Fault

But enough about Petersen coil for now—she doesn't play a role in this example. We now load the file `Shortcircuit_Current.asc` and start the simulation. Before the fault, the line-to-line voltage is approximately 116 kV. The line currents are predominantly capacitive charging currents with a peak value of approximately 35 A.

2.3.2 Fault Inception

At fault inception, the short-circuit current at the fault position reaches a maximum instantaneous value of approximately 53 kA. The 116 kV voltage decreases to approximately 98 kV. The RMS voltage can be checked at the right buselement at bus4 at their measurement pins.

Remark 2.2 – (Output of measurement values)

Some measurement values computed with the `.meas` statement can be seen in the Spice outputfile by activating the schematic window and choose `view/SpiceOutputLog`. Scroll to the end of the file.

2.3.3 Settled Fault Current

After the transient components have largely decayed—approximately 200 ms after fault inception—the steady state short-circuit current is approximately 30 kA peak, or 22 kA RMS. The voltage on the 400 kV side is approximately 396 kV.

2.1

Result 2.1 – (Transient simulation results)

The principal simulated values are a first peak of approximately 53 kA and a settled RMS short-circuit current of approximately 22 kA.

2.4 Estimating the Steady-State Short-Circuit Current

The RMS value of the steady-state short-circuit current can be estimated from the transformer rating and relative short-circuit voltage. The rated current on the medium-voltage side of one transformer is

Calculation 2.1 – (Short-circuit current estimate)

$$I_N = \frac{S_N}{\sqrt{3} U_N} \quad (2.1)$$

$$= \frac{40 \text{ MV A}}{\sqrt{3} \cdot 10.6 \text{ kV}} \quad (2.2)$$

$$\approx 2.18 \text{ kA}. \quad (2.3)$$

For a relative short-circuit voltage of $u_k = 0.18$, the approximate short-circuit-current factor is

$$\frac{1}{u_k} = \frac{1}{0.18} \approx 5.5. \quad (2.4)$$

Thus, one transformer contributes approximately

$$I_{k,1} \approx 5.5 \cdot 2.18 \text{ kA} = 12 \text{ kA}. \quad (2.5)$$

For two identical transformers in parallel,

$$I_{k,2} \approx 2I_{k,1} = 24 \text{ kA}. \quad (2.6)$$

This value applies at the nominal primary voltage of 110 kV. Because the 110kV operating voltage decreases to approximately 100 kV, the corrected estimate is

$$I_k \approx \frac{100}{110} \cdot 24 \text{ kA} = \boxed{21.8 \text{ kA}}. \quad (2.7)$$

Considering the simplifying assumptions, the manual estimate of approximately 21.8 kA agrees well with the simulated RMS value of approximately 22 kA in ??.

2.5 Short-Circuit Current with Initial Load

Open the file `Shortcircuit_Current_with_initial_load.asc`. A shunt reactor is used as the initial load. It reduces the operating voltage and therefore also reduces the short-circuit current. The first current peak is slightly lower, and the settled RMS current is approximately 20.8 kA.

2.6 Short-Circuit Reactor

Load file `Shortcircuit_Current_with_scr.asc`. An additional short-circuit reactor, denoted by `scr` in the model, is now introduced. For strongly inductive currents, its reactance causes a larger voltage drop and limits the short-circuit current. During normal operation with predominantly resistive current, the voltage drop across the reactor is much smaller. The parameter `delta_un=5%` specifies the percentage voltage drop at rated, purely inductive current.

With this reactor, the first transient current peak is reduced to approximately 11 kA, and the settled RMS short-circuit current is approximately 4.4 kA. The voltages are approximately 112.2 kV on the 110 kV level, 399.3 kV on the 400 kV level and 9 kV on the 10 kV level.

2.6.1 Manual Calculation

For a reactor rated at $U_N = 10 \text{ kV}$ and $I_N = 250 \text{ A}$ and with $\Delta u_N = 5\%$, the nominal three-phase apparent power is

Calculation 2.2 – (Fault current behind the reactor)

$$S_D = \sqrt{3} U_N I_N \quad (2.8)$$

$$= \sqrt{3} \cdot 10 \text{ kV} \cdot 250 \text{ A} \quad (2.9)$$

$$\approx 4.33 \text{ MV A.} \quad (2.10)$$

With the specified relative inductive voltage drop, the reactor impedance is

$$X_D = \frac{\Delta u_N}{100} \frac{U_N^2}{S_D} \approx 1.15 \Omega. \quad (2.11)$$

The maximum RMS fault current immediately behind the reactor is therefore

$$I_{kD} = \frac{U_N}{\sqrt{3} X_D} \quad (2.12)$$

$$= \frac{10 \text{ kV}}{\sqrt{3} \cdot 1.15 \Omega} \quad (2.13)$$

$$\approx 5 \text{ kA.} \quad (2.14)$$

This assumes a perfectly stiff operating voltage. In the example, the voltage drops from 10.2 kV to 8.8 kV; consequently, the short-circuit current falls to approximately

$$I_{kD} \approx \boxed{4.4 \text{ kA}}. \quad (2.15)$$

2.7 AC Analysis

Load the file `Shortcircuit_Current_AC.asc`. For the AC analysis, first replace the transient voltage-source model with the corresponding AC source model. Then adapt the `.meas` directives, delete the fault switch, and place the new ground element ground on the schematic. Add the following option so that complex measurement results are reported in polar form instead of decibels:

```
.options measplxfmt=polar
```

The magnitudes of the voltages and currents agree good with the settled values from the transient analysis. Directly at the phase-1 fault location, however, the current angle is approximately 120° rather than the initially expected -90° . Closer to the voltage source—for example, at the transformer primary—the expected current angle of approximately -90° and voltage angle of approximately 0° are obtained.

Important 2.1 – (Effect of transformer vector group)

The transformer vector group is Yd5, corresponding to a phase shift of $5 \cdot -30^\circ = -150^\circ$. For an almost purely inductive fault path, the current lags the voltage by approximately -90° . Hence,

$$\varphi_I \approx -150^\circ + (-90^\circ) = -240^\circ = 120^\circ. \quad (2.16)$$

Because the fault resistance is assumed to be purely resistive, the current and the voltage at the fault have approximately the same angle. The theoretical voltage angle can be checked by removing the ground elements and repeating the simulation.

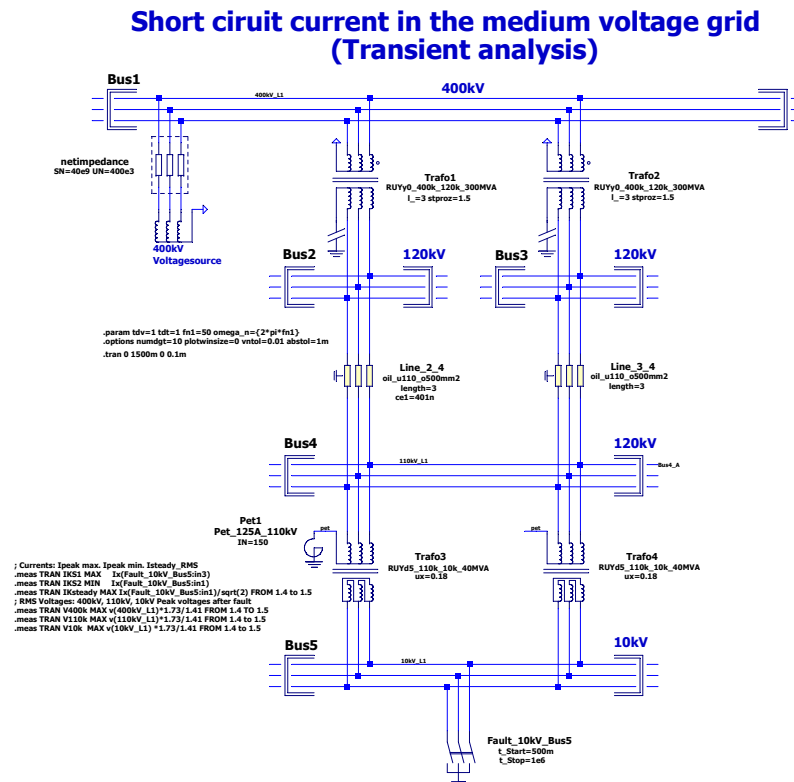


Figure 2.1: Shortcircuit in the medium voltage grid - schematic

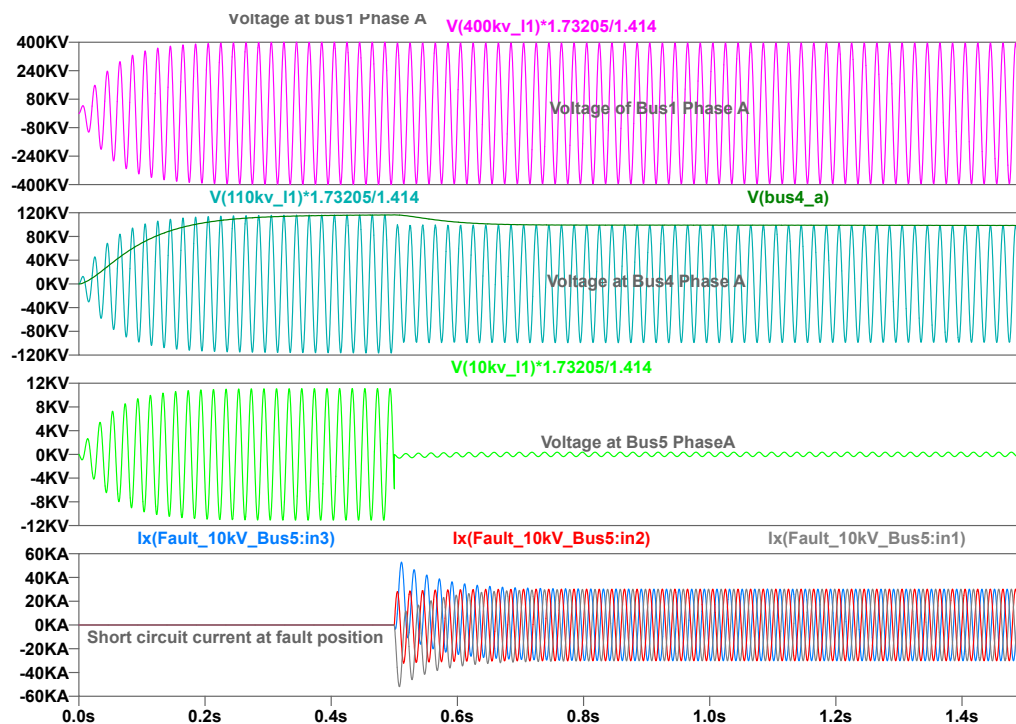


Figure 2.2: Shortcircuit in the medium voltage grid - waveform

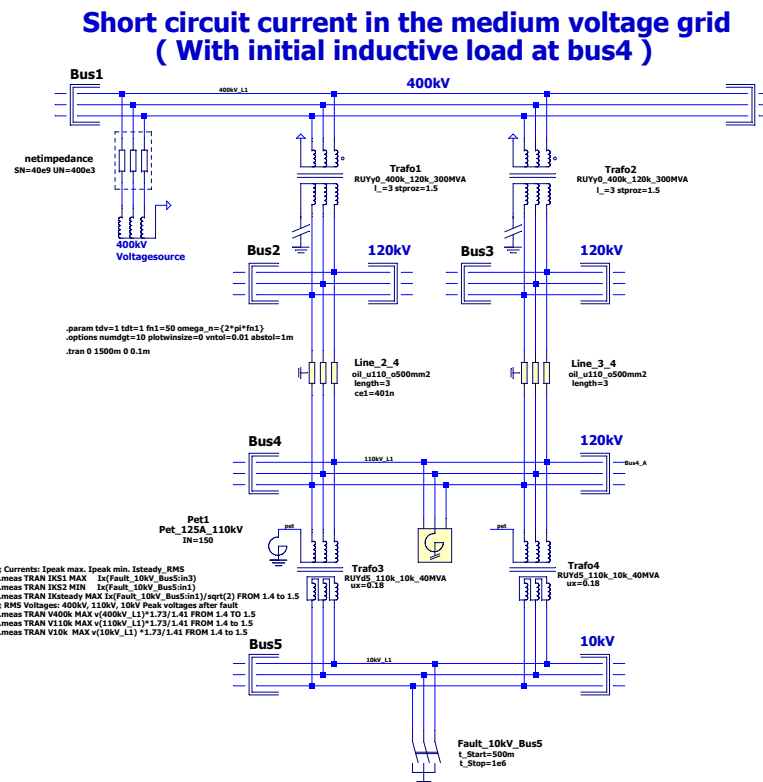


Figure 2.3: Shortcircuit in the medium voltage grid with initial load - schematic

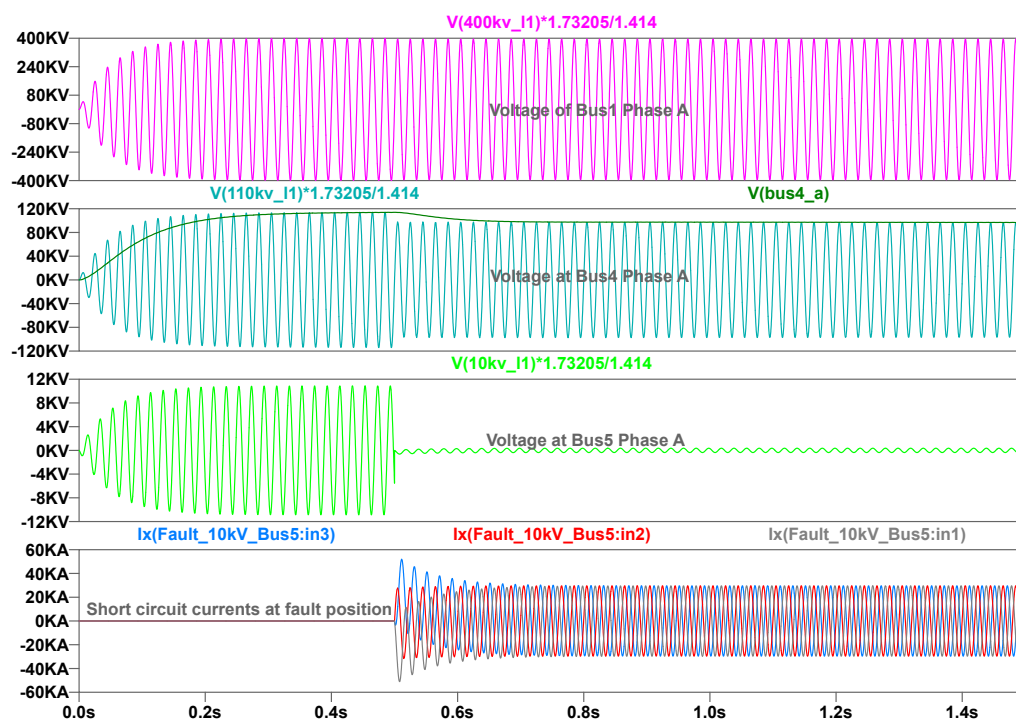


Figure 2.4: Shortcircuit in the medium voltage grid with initial load - waveform

Short circuit current in the medium voltage grid (Tran analysis with 10kV short circuit reactance at bus5)

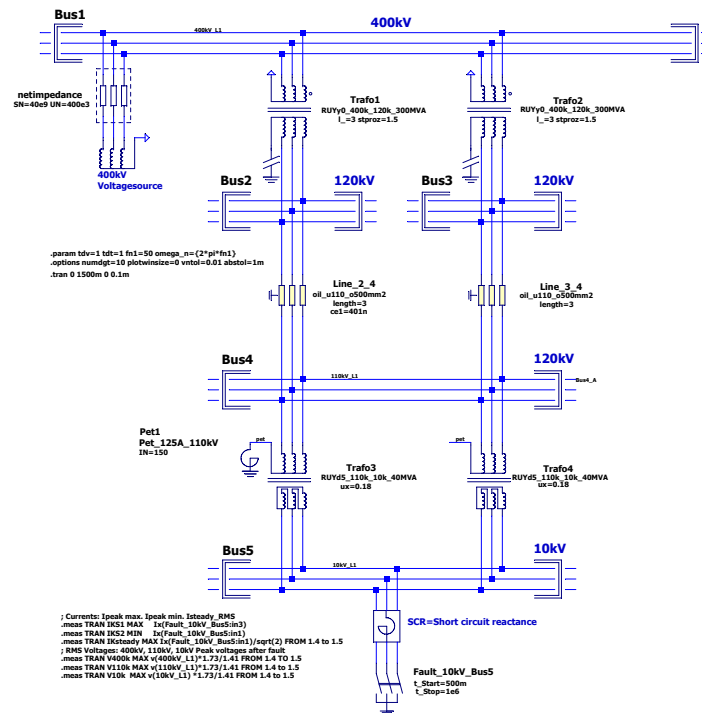


Figure 2.5: Shortcircuit in the medium voltage grid with scr - schematic

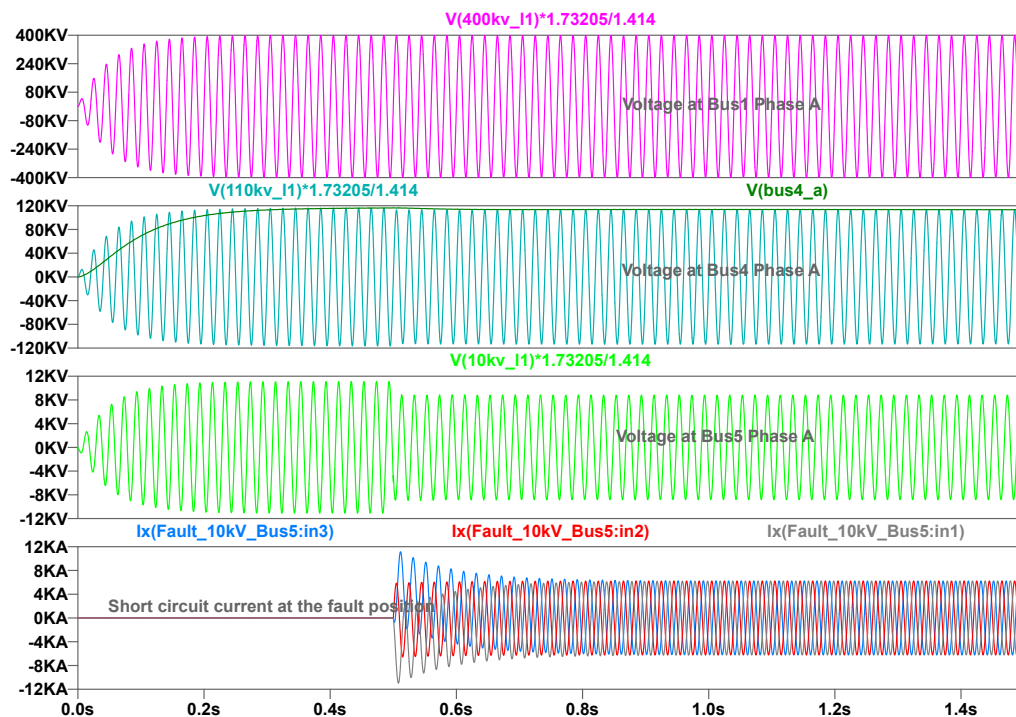


Figure 2.6: Shortcircuit in the medium voltage grid with scr - waveform

Short circuit current in the medium voltage grid (AC-Analysis with fault)

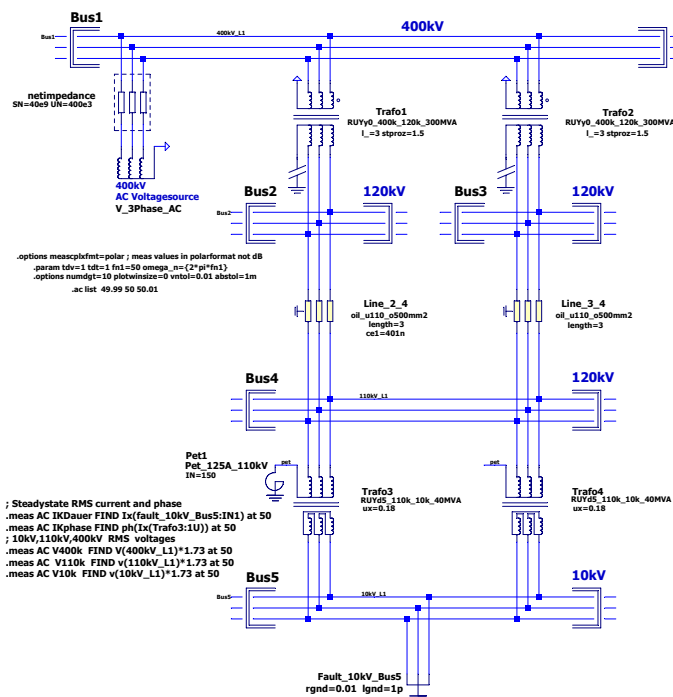


Figure 2.7: Shortcircuit in the medium voltage grid AC analysis - schematic

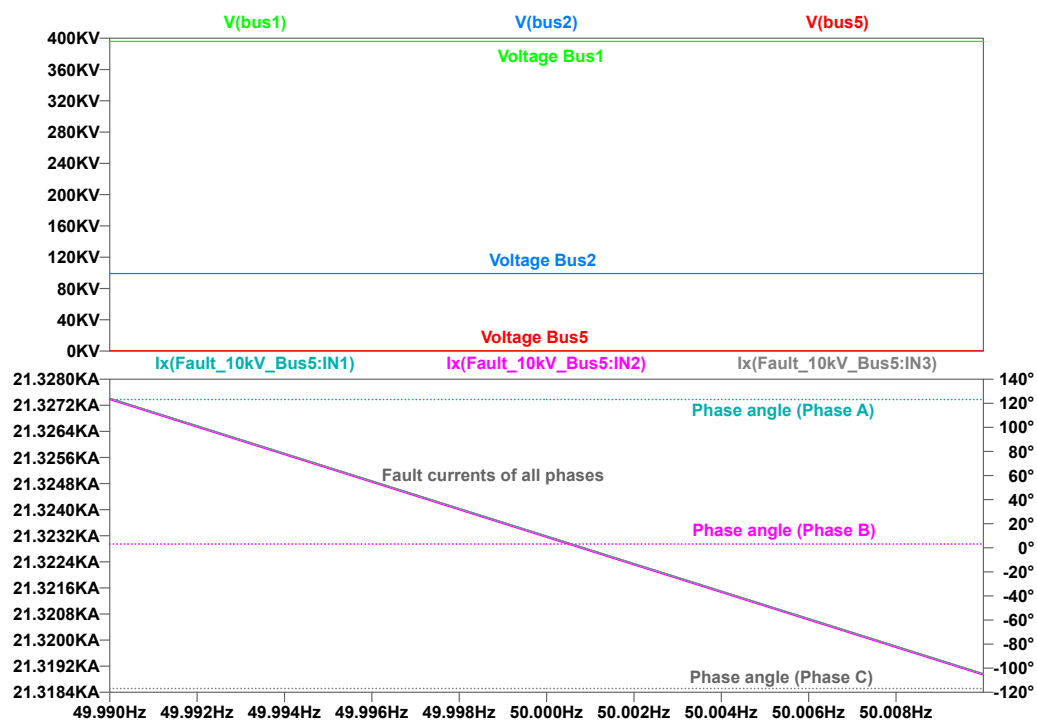


Figure 2.8: Shortcircuit in the medium voltage grid AC analysis - waveform

Chapter Summary

Two 40 MV A medium-voltage transformers operated in parallel produce a settled short-circuit current of approximately 22 kA RMS in the investigated network. A simple estimate based on rated current, relative short-circuit voltage, parallel operation, and the actual operating voltage closely reproduces this result. An initial inductive load reduces the current slightly, whereas an additional short-circuit reactor limits it substantially to approximately 4.4 kA. The AC analysis also demonstrates that transformer vector groups must be considered when interpreting phase angles.

3 Initializing Transformers with Residual Flux

3.1 General

This chapter demonstrates how a transformer model can be initialized with residual magnetic flux. The examples show how the switching instant and the polarity of the residual flux determine the maximum core flux and the resulting magnetizing inrush current.

For an ideal winding, neglecting the winding resistance, the applied voltage and core flux are related by

$$u(t) = N \frac{d\Phi(t)}{dt}, \quad \Phi(t) = \Phi(0) + \frac{1}{N} \int_0^t u(\tau) d\tau. \quad (3.1)$$

Consequently, the flux is determined by the time integral of the imposed voltage and by the initial flux $\Phi(0)$. If a transformer is energized at an unfavourable point on the voltage waveform, the transient flux can reach twice its normal steady-state peak. With full residual flux of the same polarity, it can approach three times the normal peak. Because the core characteristic is nonlinear, this overfluxing can produce a magnetizing current many times larger than the normal no-load current.

Important 3.1 – (Switching instant and residual flux)

The initial flux, the voltage phase angle at switching, and the parameter that applies the initial condition must always be coordinated. A physically reasonable residual-flux vector in a three-leg core also satisfies approximately $\Phi_{r0} + \Phi_{s0} + \Phi_{t0} = 0$.

3.2 Circuit Design

Four transformer circuits are arranged on the right side of the schematic. They are supplied at 115 kV; each transformer is rated 110 kV/10.6 kV. A switch is placed between each source and transformer.

The first three circuits are energized at a phase-1 voltage zero crossing and use different residual-flux settings:

- no residual flux: $\text{psi0}=0$,
- unfavourable residual flux: $\text{psi0}=1$,
- favourable residual flux: $\text{psi0}=-1$.

The fourth circuit is energized at a different point on the voltage waveform and uses explicitly specified phase residual fluxes. See section ??.

Remark 3.1 – (Coordination of initialization time)

The transformer parameter tpsi0 must match the switch closing time t_start . For the first three circuits, use

```
t_start=40m  tpsi0=40m
```

For the final circuit, use

```
t_start=45m  tpsi0=45m
```

The tpsi0 event rapidly initializes the voltage integrator capacitor that represents the residual flux.

3.3 Energization at 40 ms Without Residual Flux

Set the transformer parameter psi0 to zero. The parameter tpsi0 may either be set to 40 ms or placed well outside the simulation interval, for example at 1 000 s, because no nonzero initial flux has to be applied.

At 40 ms, the phase-1 voltage starts at zero and initially becomes positive. Its integral therefore acquires a unidirectional offset. At 10 ms after energization, the phase-1 flux reaches approximately twice the normal steady-state peak, and the magnetizing current rises accordingly.

The phase fluxes can be displayed in the LTspice waveform viewer with

```
V(Trafo1:u:_w1:phi)
V(Trafo1:v:_w1:phi)
V(Trafo1:w:_w1:phi)
```

Both flux and current decay slowly because a large power transformer has a high magnetizing inductance and a long electrical time constant. Increasing the resistance of the source impedance accelerates the decay. This can be examined with $R = 10\ \Omega$, $100\ \Omega$, and $1\ 000\ \Omega$.

The rated primary current is approximately 210 A RMS. In this case, the peak magnetizing current is approximately 70 A, or about 50 A RMS, and therefore remains below the rated current.

For a sinusoidal phase voltage, the steady-state peak flux is

Calculation 3.1 – (Rated steady-state flux)

$$\hat{\Phi}_N = \frac{\sqrt{2} U_{ph}}{\omega N_1} = \frac{\sqrt{2} U_{LL}}{\sqrt{3} \omega N_1}. \quad (3.2)$$

With $U_{LL} = 115\ \text{kV}$, $\omega = 2\pi \cdot 50\ \text{Hz}$, and the toolbox default $N_1 = 1000$, this gives

$$\hat{\Phi}_N = \frac{\sqrt{2} \cdot 115\ \text{kV}}{\sqrt{3} \cdot 2\pi \cdot 50\ \text{Hz} \cdot 1000} \approx \boxed{0.299\ \text{Wb}}. \quad (3.3)$$

Remark 3.2 – (Line-to-line and phase voltage)

The source document used 115 kV directly in $U/(\omega N)$. For a star-connected three-phase winding, Calculation ?? uses the phase voltage $U_{ph} = U_{LL}/\sqrt{3}$ and includes the RMS-to-peak factor $\sqrt{2}$.

3.4 Energization at 40 ms with Unfavourable Residual Flux

Set `psi0=1`. Unless the individual phase parameters are overridden, the model initializes the phase residual-flux values to

$$(\psi_{r0}, \psi_{s0}, \psi_{t0}) = (1, -0.5, -0.5) \text{ p.u.} \quad (3.4)$$

Phase 1 therefore starts with full positive residual flux, while phases 2 and 3 start with half the negative value. Since the phase-1 voltage becomes positive immediately after the switch closes, its integral adds to the positive residual flux. Approximately 10 ms later, the flux reaches about three times the steady-state peak.

The phase-1 current reaches approximately 900 A peak, or 640 A RMS. This is about three times the rated transformer current and roughly 15 times the magnetizing current obtained without residual flux. The inrush current then decays comparatively quickly because the high current increases the effective damping of the transient.

The corresponding flux traces are

```
V(Trafo2:u:_w1:phi)
V(Trafo2:v:_w1:phi)
V(Trafo2:w:_w1:phi)
```

The residual-flux values are visible as the initial values at the switching instant.

3.5 Energization at 40 ms with Favourable Residual Flux

Set `psi0=-1`. The internal phase residual-flux vector becomes

$$(\psi_{r0}, \psi_{s0}, \psi_{t0}) = (-1, 0.5, 0.5) \text{ p.u.} \quad (3.5)$$

The maximum negative phase-1 residual flux compensates the positive flux increment that follows switching at 40 ms. Apart from a short numerical switching spike, the flux moves directly into its steady-state trajectory and the magnetizing current remains very small.

A similarly smooth startup can be obtained by setting the voltage-source parameter `texp`, for example to 50 ms. This causes the source voltage to rise exponentially from zero. Alternatively, setting the transformer parameter `m=1` replaces the nonlinear magnetization curve with a linear characteristic for diagnostic purposes.

To inspect the small steady-state current in the waveform viewer, manually limit the current-axis range after the switching spike. The nonlinear magnetization curve produces a small but visibly distorted current. The phase fluxes are displayed with

```
V(Trafo3:u:_w1:phi)
V(Trafo3:v:_w1:phi)
V(Trafo3:w:_w1:phi)
```

They are symmetrical about zero and already settled after energization.

Remark 3.3 – (Default residual-flux vector)

The default vectors $(1, -0.5, -0.5)$ and $(-1, 0.5, 0.5)$ produce the behaviour described above only at equivalent points of the 50 Hz waveform, such as 0, 20, and 40 ms. At other switching instants, specify the individual values with `psir`, `psis`, and `psit`.

3.6 Energization at 45 ms with Unfavourable Residual Flux

For switching at 45 ms, the unfavourable residual-flux vector differs from the default vector used at the voltage zero crossing. The required values are as follows:

```
psi0=1
psir=0
psis=0.866
psit=-0.866
t_start=45m
tpsi0=45m
```

With these settings, the phase-1 current is the smallest, whereas the currents in phases 2 and 3 are the largest. The currents remain high, but their maxima are lower than in the unfavourable 40 ms case seen in ??.

The phase fluxes can be displayed with

```
V(Trafo4:u:_w1:phi)
V(Trafo4:v:_w1:phi)
V(Trafo4:w:_w1:phi)
```

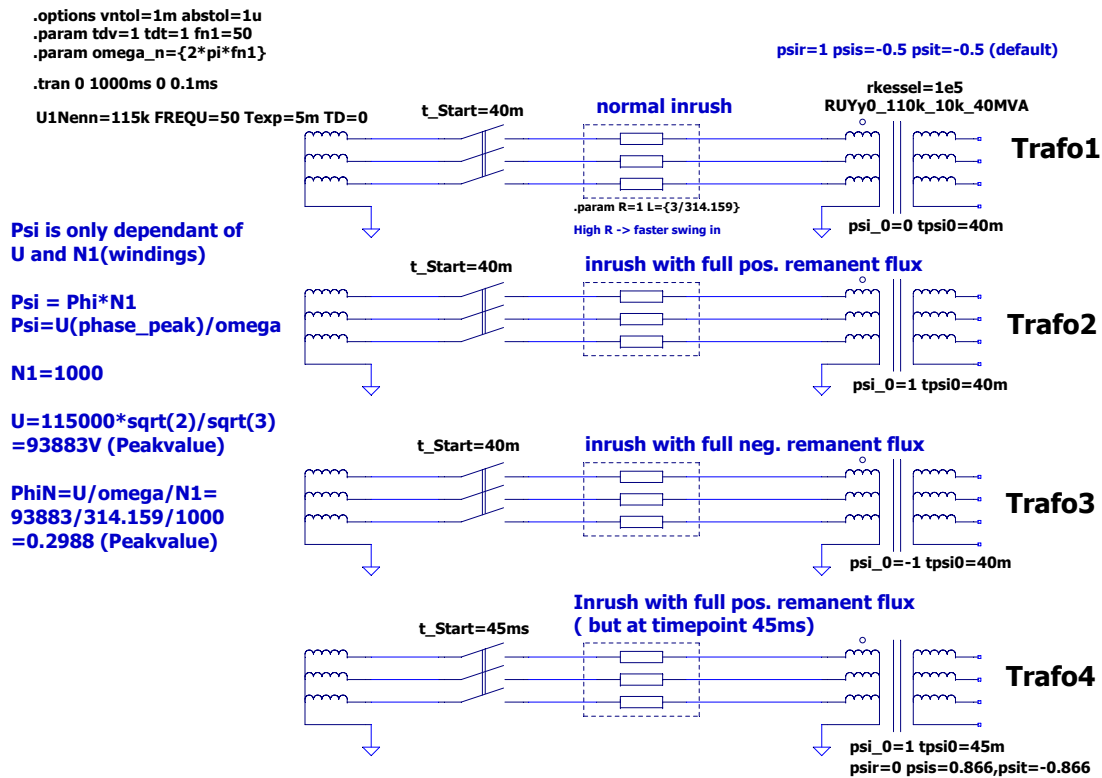


Figure 3.1: Initializing Transformer with residual flux - schematic

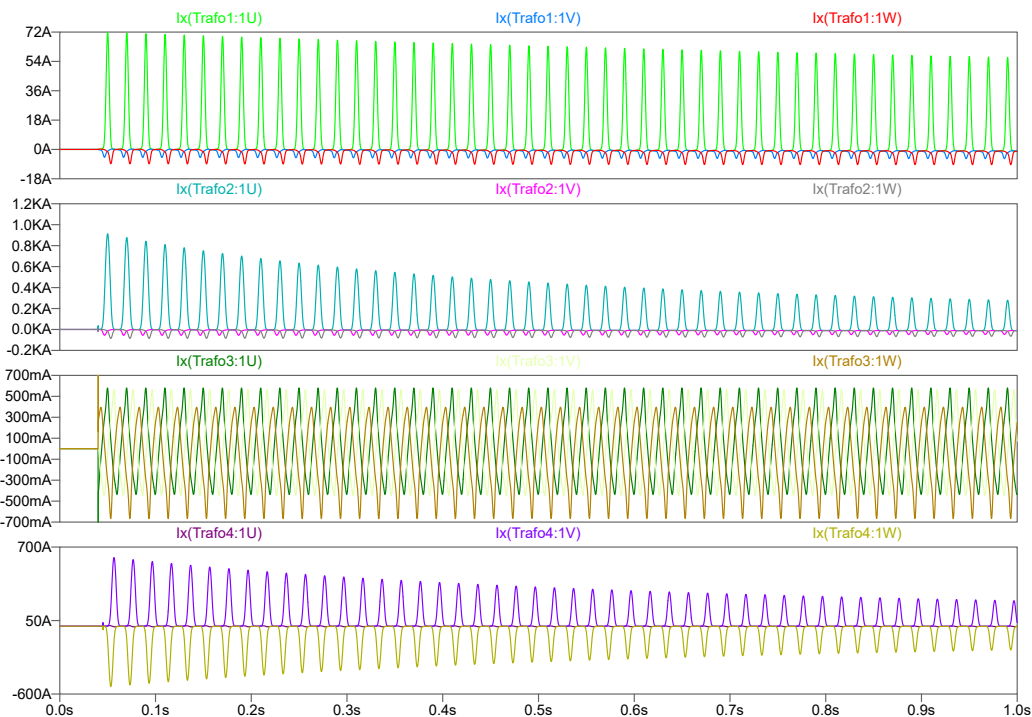


Figure 3.2: Initializing Transformer with residual flux - Currents

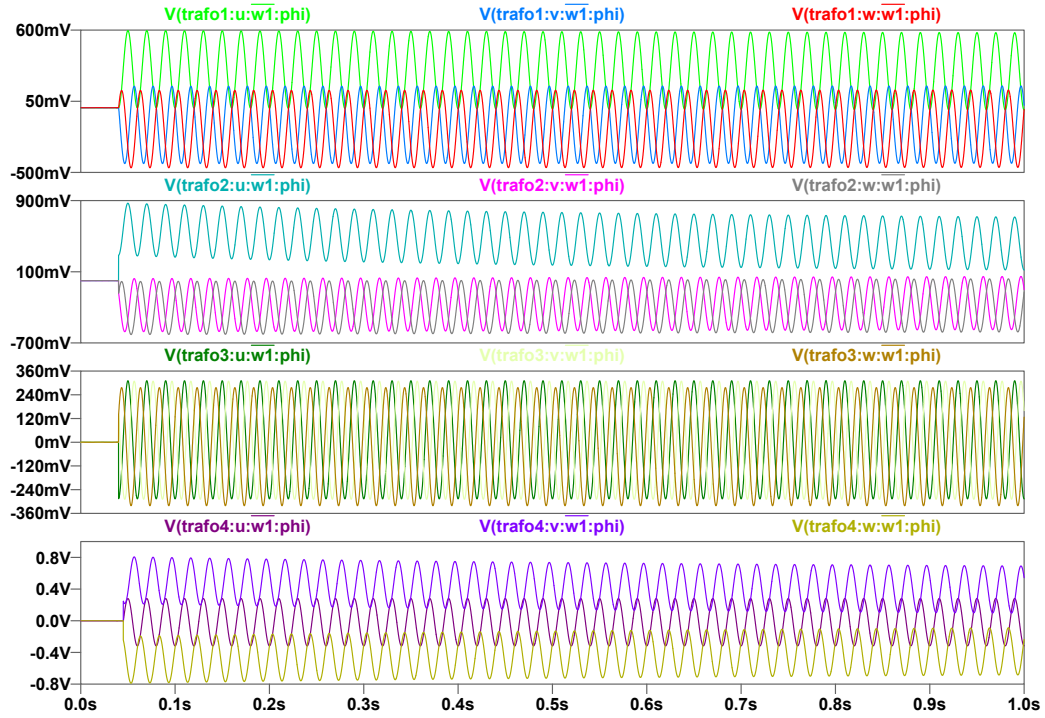


Figure 3.3: Initializing Transformer with residual flux - Fluxes

Chapter Summary

Transformer energization is governed by the integral of the applied voltage and by the residual core flux at the switching instant. Closing at a voltage zero crossing without residual flux can produce approximately twice the normal steady-state peak flux. Unfavourable full residual flux can increase this to about three times the normal peak and cause a large inrush current. Favourable residual flux, controlled switching, or a gradual source-voltage ramp can greatly reduce the transient. The initialization time and all three phase residual-flux values must be coordinated with the switch closing instant. Hint: It is often mentioned in the literature that the inrush current is attenuated by connecting the transformer to a load. However, this is not the case unless the load is truly very high—which, in turn, causes the total current to be very high, thereby masking the inrush current. See ltspice example `Hidden_inrush.asc`

4 Switching Lines

4.1 General

This chapter examines the energization of unloaded and loaded cable lines. It also considers the energization of a second line connected to an already energized busbar and the energization of a cable terminated by a transformer. The examples illustrate the influence of switching instant, line capacitance, network inductance, load damping, and transformer residual flux on the resulting transients.

The switching transients are oscillations at the natural frequencies of the electrical network. Such oscillations occur whenever the system state changes abruptly, for example during line energization or at the inception of an earth fault or short circuit.

4.2 Circuit Design

Open the file: `switching_lines.asc`. The LTspice schematic contains four circuits. Each line is a 5 km, 110 kV oil-filled cable with a conductor cross-section of 500 mm². The circuits represent:

1. energization of an unloaded cable,
2. energization of a cable supplying a 100 MW load,
3. energization of a second unloaded cable connected to an energized busbar,
4. energization of a cable terminated by a transformer with unfavourable full residual flux.

Each single line is earth-fault compensated by a 125 A Petersen coil. The double-line arrangement uses 125 A compensation at the begin and 250 A compensation started at 400ms

4.2.1 Adjustment of the Petersen Coil

To determine the required compensation, temporarily reduce the load in the second circuit from 100e6 to 100e-6 and run the simulation. The phase-1 charging-current peak is approximately 60 A. For a shielded single-core cable whose dominant capacitances are phase-to-earth, the earth-fault charging current is approximately

$$I_{E,\text{peak}} \approx 3I_{0,\text{peak}} = 3 \cdot 60 \text{ A} = 180 \text{ A}, \quad (4.1)$$

or approximately 127 A RMS. A 125 A Petersen coil is therefore appropriate. After this adjustment, restore the load to 100e6.

Remark 4.1 – (Applicability of the threefold charging current)

The relation $I_E \approx 3I_0$ applies to the zero-sequence charging current of the cable. Overhead lines have appreciable phase-to-phase capacitances, so the same simplified interpretation must not be transferred without checking the complete capacitance matrix.

4.3 Energization of an Unloaded 110 kV Cable

For the selected switching instant, phase 1 is closed close to a voltage zero crossing. Its peak current is therefore the smallest, approximately 130 A. Immediately after closing, the cable capacitances behave like short circuits and draw large, rapidly changing charging currents. The phase-2 and phase-3 current peaks reach approximately 1.5 kA. The oscillations have substantially decayed after approximately 200 ms.

The phase-1 voltage transient is likewise the smallest. The phase-2 and phase-3 voltages reach approximately –160 kV peak, about 30 % above the nominal phase-voltage peak. The precise current and voltage maxima depend strongly on the switching instant. This can be investigated by changing the switch parameter t_{start} from 40 ms to 45 ms.

Important 4.1 – (Origin of the voltage transient)

The capacitive charging current flows through the inductive source and line impedances. The resulting voltage drop is superimposed on the source voltage at the cable terminal. Consequently, the phases with the largest charging current also show the largest voltage transient.

4.3.1 Natural Frequency

The natural frequency can be identified in LTspice with VIEW/FFT. For example, an FFT of the phase-2 voltage shows peaks at 50 Hz and approximately 1.44 kHz.

The short-circuit power of the network is 7.5 GV A. Its nominal reactance is

Calculation 4.1 – (Natural frequency of the 5 km cable)

$$X_N = \frac{U_N^2}{S_k} = \frac{(110 \text{ kV})^2}{7.5 \text{ GV A}} = 1.613 \Omega, \quad (4.2)$$

$$X_{\text{line}} = 0.11 \Omega/\text{km} \cdot 5 \text{ km} = 0.55 \Omega. \quad (4.3)$$

With $\omega = 2\pi \cdot 50 \text{ Hz}$ and $C' = 400 \text{ nF/km}$, a lumped approximation gives

$$L = \frac{X_N + X_{\text{line}}}{\omega} \approx 6.9 \text{ mH}, \quad (4.4)$$

$$C = C' l = 2 \mu\text{F}, \quad (4.5)$$

$$f_r = \frac{1}{2\pi\sqrt{LC}} \approx 1.35 \text{ kHz}. \quad (4.6)$$

The cable is implemented as a lumped T-section. During the initial charging process, only the source-side half of its series inductance is effective in the relevant resonant loop. Therefore,

$$L_{\text{eff}} = \frac{X_N + X_{\text{line}}/2}{\omega} \approx 6.0 \text{ mH}, \quad (4.7)$$

$$f_{r,T} = \frac{1}{2\pi\sqrt{L_{\text{eff}}C}} \approx \boxed{1.45 \text{ kHz}}, \quad (4.8)$$

which agrees closely with the simulated 1.44 kHz.

The oscillation frequency can also be read directly in the waveform viewer: zoom into two adjacent transient peaks and use the time difference and frequency displayed in the lower-left status line.

4.3.2 Petersen-Coil Oscillation

The Petersen-coil voltage and current do not immediately reach steady state. A slow beat of approximately 1 Hz is visible because the compensated zero-sequence resonant frequency differs slightly from the network frequency. After the transient has decayed, the residual coil current and beat are nearly zero.

4.4 Energization of a Loaded Line

When the cable supplies the load, its voltage and current transients are more strongly damped. The active part of the load absorbs oscillatory energy and reduces both the amplitude and duration of the switching transient.

4.5 Energization of a Second Line

The first, upper line is energized in the same way as the unloaded line in ?? . At 400 ms, the second line is connected to the same busbar. The traces `Ix(Line3a:L1_1)` and `Ix(Line3b:L1_1)` initially show transients of similar magnitude in both lines.

Closer inspection shows that the high-frequency components have opposite signs. They are capacitive currents circulating through the busbar and the phase-to-earth capacitances of the two cables. For two identical 5 km cables, the approximate circular-current frequency is

Calculation 4.2 – (Ring-current and network-current frequencies)

$$L_{\text{ring}} = \frac{2 \cdot 0.11 \, \Omega/\text{km} \cdot 2.5 \, \text{km}}{2\pi \cdot 50 \, \text{Hz}} \approx 1.75 \, \text{mH}, \quad (4.9)$$

$$C_{\text{ring}} = \frac{400 \, \text{nF}}{2} = 200 \, \text{nF}, \quad (4.10)$$

$$f_{\text{ring}} = \frac{1}{2\pi \sqrt{L_{\text{ring}} C_{\text{ring}}}} \approx \boxed{3.8 \, \text{kHz}}. \quad (4.11)$$

The lower-frequency component drawn from the network sees the combined capacitance of both lines:

$$L_{\text{net}} = \frac{1.613 \, \Omega + 0.11 \, \Omega/\text{km} \cdot 2.5 \, \text{km}}{2\pi \cdot 50 \, \text{Hz}} \approx 6.0 \, \text{mH}, \quad (4.12)$$

$$C_{\text{net}} = 2 \cdot 400 \, \text{nF} = 800 \, \text{nF}, \quad (4.13)$$

$$f_{\text{net}} = \frac{1}{2\pi\sqrt{L_{\text{net}}C_{\text{net}}}} \approx \boxed{1.03 \, \text{kHz}}. \quad (4.14)$$

Because this network-current component has the lower frequency, its associated inductive voltage drop and busbar-voltage transient are also smaller. The reactive-power exchange of each cable can be viewed by holding ALT and right-clicking the respective line element. LTspice then displays the instantaneous product of element voltage and current.

4.6 Energization of a Transformer-Terminated Line

In the fourth circuit, the cable supplies a transformer initialized with unfavourable residual flux. The transient current is therefore a combination of capacitive cable-charging current and inductive transformer-inrush current.

In the phase closed at a voltage zero crossing, the capacitive contribution is small while the inductive inrush contribution is large. In the other phases, the capacitive component is initially dominant but decays rapidly; the inductive component subsequently prevails. The two components decay at different rates. Extend now the simulation to 15s and run. The voltages at the primary side of the transformer are at the first few seconds higher as the nominal voltages. Especially the phase C voltage is rather high. You can get this under control by running the Petersens slightly under- or overcompensated (out of resonance).

The residual-flux initialization and its coordination with switching time are described in Chapter 3.

4.7 Extended-Line Study: Charging Current Near Rated Current

Open file `Switching_lines_70km.asc` The cable length is increased until its steady-state charging current is close to the nominal current of approximately 900 A peak, or 600 A RMS. The simulation study uses a line length of 70 km.

For a phase-to-earth capacitance C' and line-to-line RMS voltage U_{LL} , the approximate charging current is

$$I_c = \omega C' l \frac{U_{LL}}{\sqrt{3}}. \quad (4.15)$$

With $C' = 400 \, \text{nF/km}$, the ideal length required for exactly 600 A RMS is about 75 km. The 70 km simulation case is therefore a practical approximate setting, with the exact result determined by the implemented line model.

At 70 km, the current transient reaches approximately 3.5 kA for phase B and C, while its dominant oscillation frequency falls to approximately 230 Hz. Despite the larger current, the voltage transient is smaller and the oscillation decays rapidly. The greater cable resistance provides stronger damping, and the lower oscillation frequency reduces the network impedance.

Calculation 4.3 – (Comparison of inductive voltage drops at net impedance)

For the 5 km case,

$$L_N = \frac{1.613 \Omega}{2\pi \cdot 50 \text{ Hz}} \approx 5.1 \text{ mH}, \quad (4.16)$$

$$X_L(1.44 \text{ kHz}) = 2\pi \cdot 1.44 \text{ kHz} \cdot L_N \approx 46.4 \Omega, \quad (4.17)$$

$$\hat{U}_L \approx 46.4 \Omega \cdot 1.5 \text{ kA} \approx 69.6 \text{ kV}. \quad (4.18)$$

For the 70 km case,

$$X_L(230 \text{ Hz}) = 2\pi \cdot 230 \text{ Hz} \cdot L_N \approx 7.4 \Omega, \quad (4.19)$$

$$\hat{U}_L \approx 7.4 \Omega \cdot 3.5 \text{ kA} \approx 25.9 \text{ kV}. \quad (4.20)$$

This explains why the 70 km case produces a smaller voltage transient even though its charging-current transient is larger. In LTspice, the voltage drop can be measured by right-clicking the source side of the phase-B of the impedance, choosing MARK REFERENCE, and selecting the switcher side of the impedance as the second measurement point. The observed drop is approximately 25 kV, compared with approximately 70 kV in the 5 km case. This is because the dominant frequency is much smaller and therefore the impedance is much smaller. HINT: Look at the Petersen current in the 70 km cable network. It is about 90A peak.

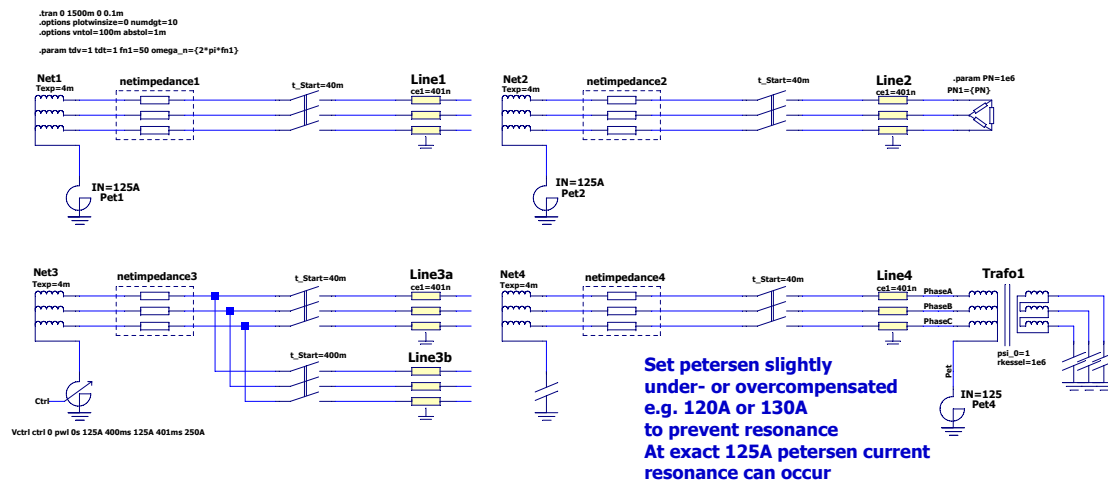


Figure 4.1: Switching lines - schematic

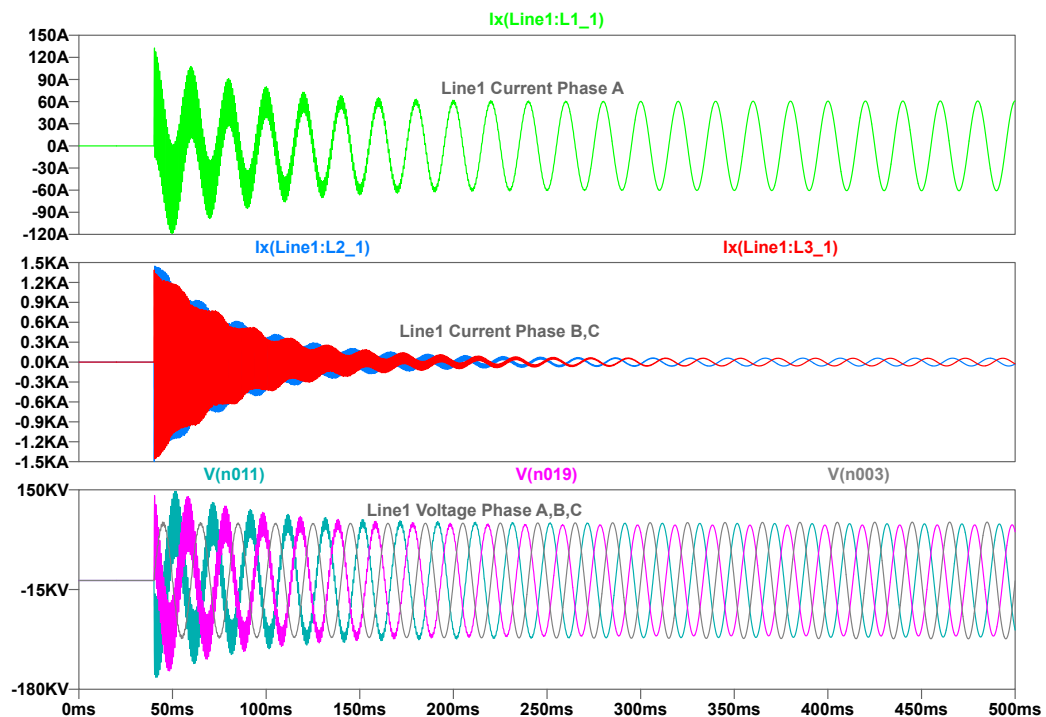


Figure 4.2: Switching lines1 - waveform

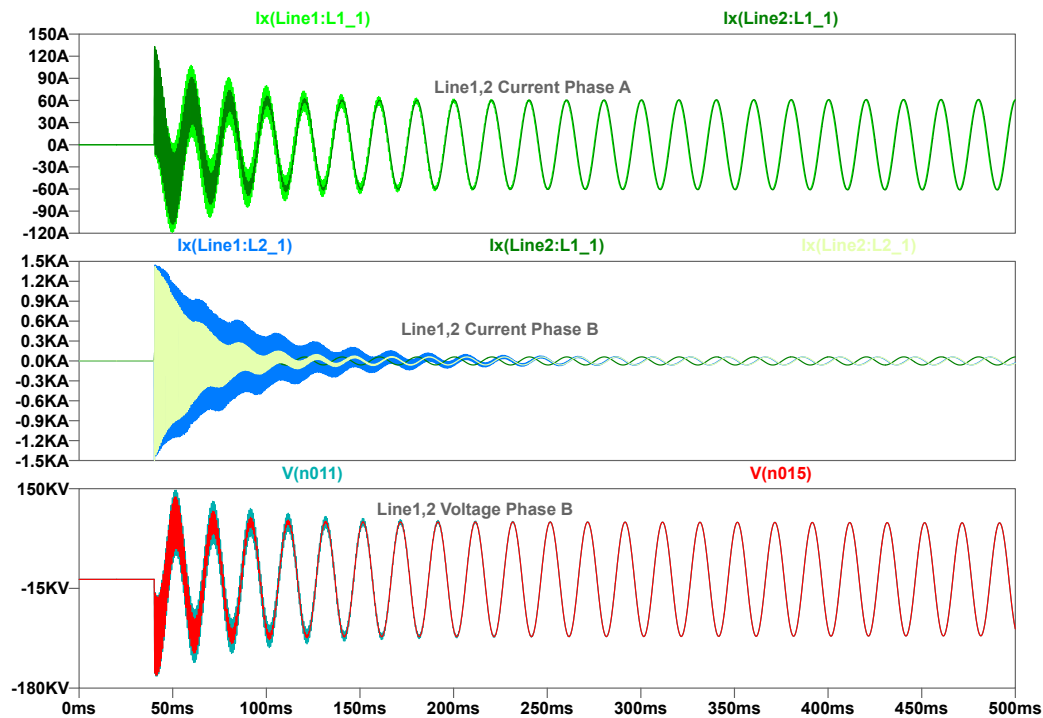


Figure 4.3: Switching lines2 - waveform

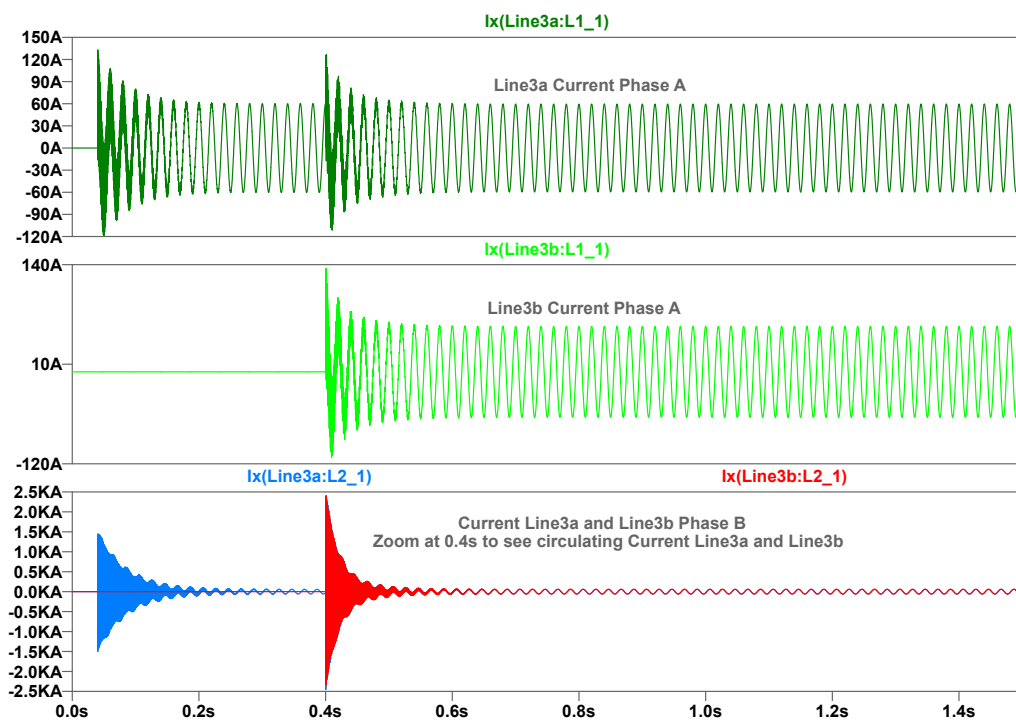


Figure 4.4: Switching lines3ab - waveform

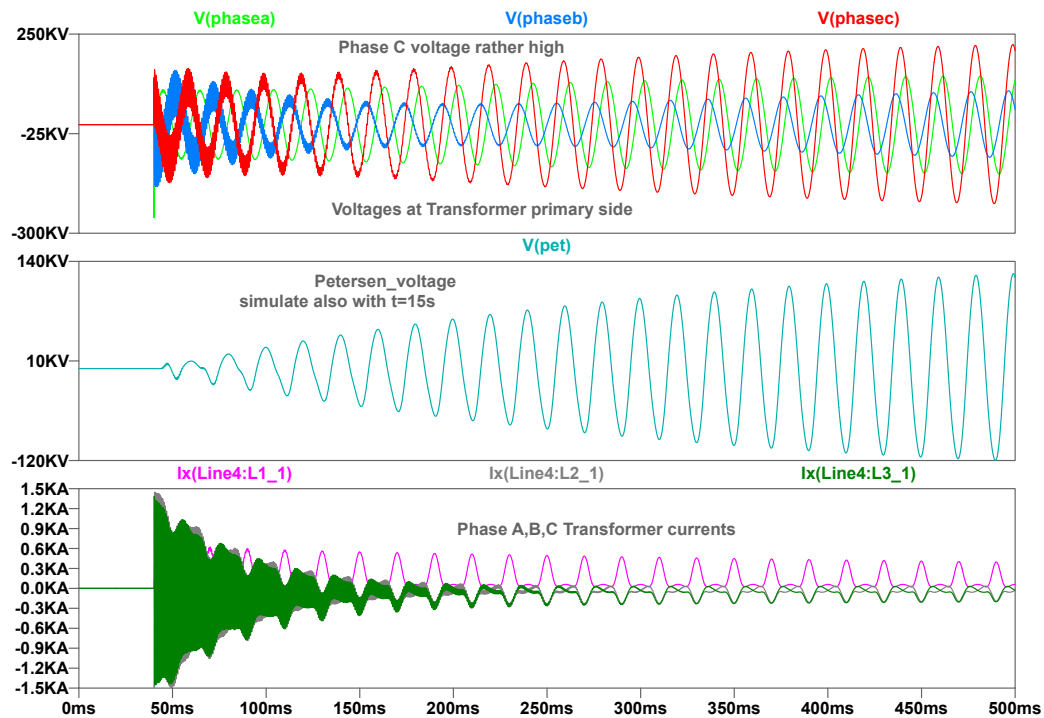


Figure 4.5: Switching lines4 - waveform

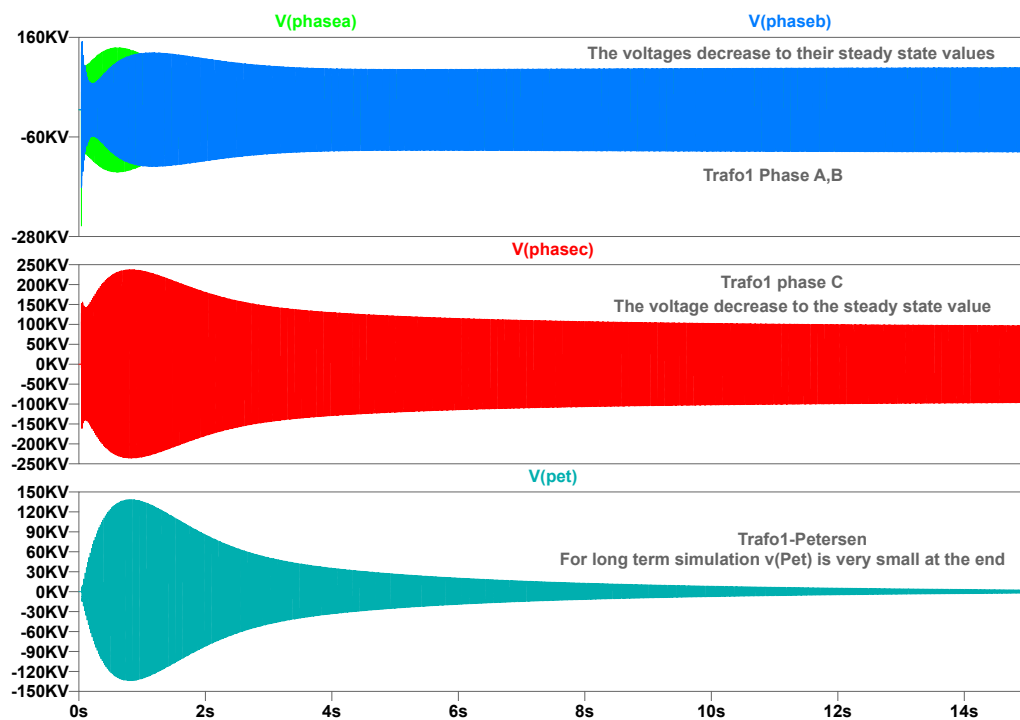


Figure 4.6: Switching lines 15s - waveform

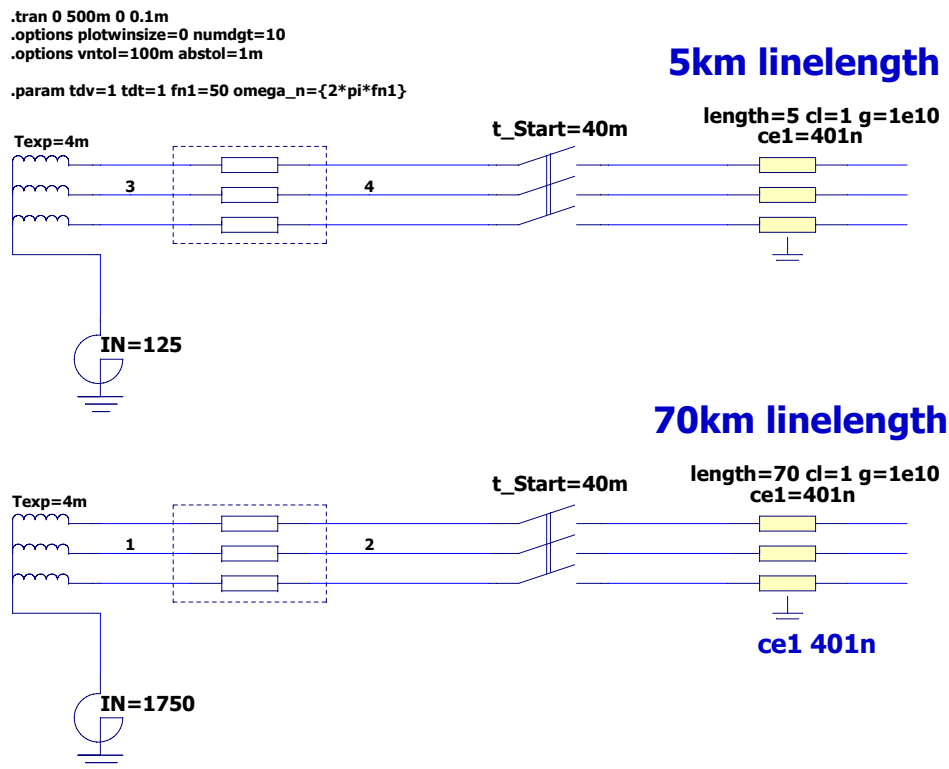


Figure 4.7: Switching lines 70km - schematic

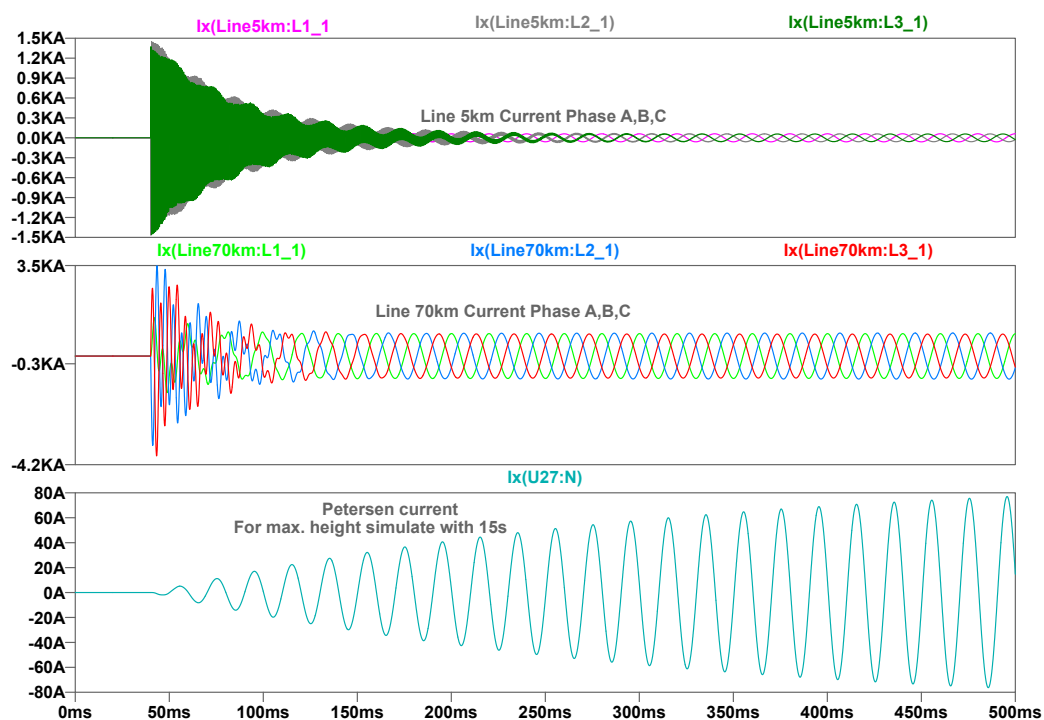


Figure 4.8: Switching lines 70km - waveform1

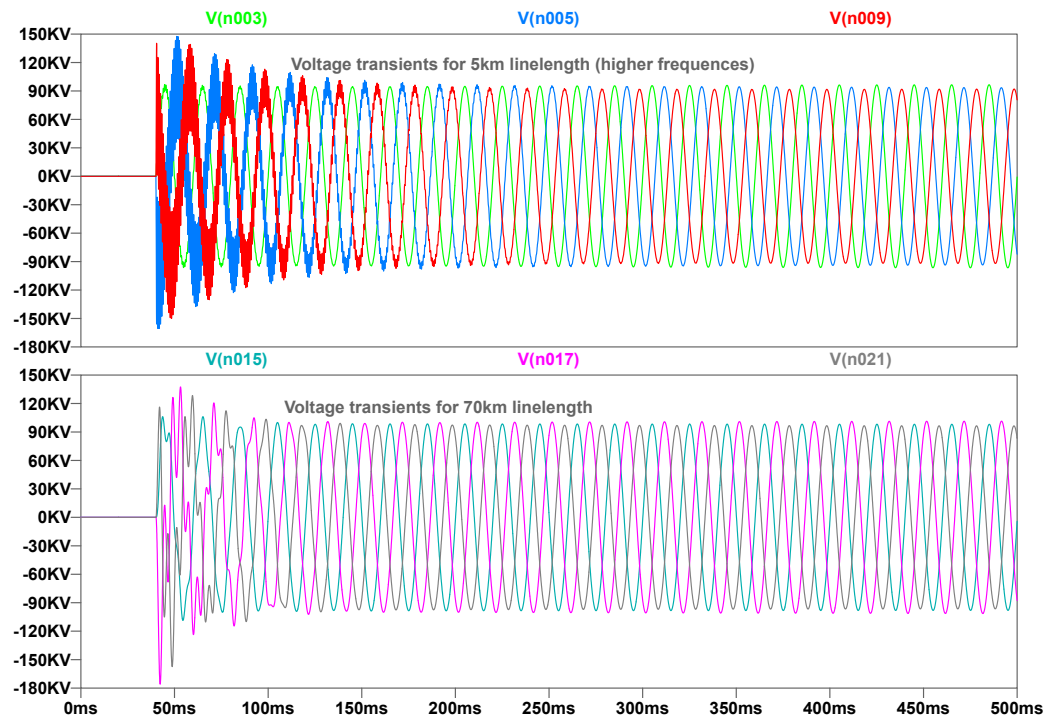


Figure 4.9: Switching lines 70km - waveform2

Chapter Summary

Cable energization produces high-frequency oscillations determined mainly by network inductance and cable capacitance. The switching instant controls the initial phase currents and overvoltages, while a connected load increases damping. Energizing a second cable creates both high-frequency circulating currents and a lower-frequency network-current component. When a cable supplies a transformer, capacitive charging and inductive inrush currents are superimposed. Increasing the cable length raises the charging current but also lowers the resonant frequency and increases resistive damping; the resulting voltage transient can therefore become smaller even when the current transient is larger. As can be seen in the example with the transformer, operating the Petersen transformer exactly at the resonance point can cause very high voltages. For this reason, in practice, the Petersen transformer is operated with either slight overcompensation or undercompensation. As can be seen in the network with the 70-kilometer-long cable, the residual current in very large cable networks becomes quite high. The network is therefore usually divided into smaller subnetworks.

5 Earth Faults in 110 kV and 10 kV Power Grids

5.1 General

A Petersen coil is an intelligent protection and stabilization element in medium-voltage networks and, in some cases, also in high-voltage networks. It ensures that single-pole ground faults can be controlled safely and without immediate shutdown. This makes it an indispensable component of modern power supply systems. The Petersen coil is an inductive coil that is connected to the neutral point of the transformer. In a three-phase AC network, capacitive currents flow between conductors and earth. If a ground fault occurs, a capacitive fault current flows through the fault location – this can be dangerously high. In the event of a fault, the Petersen coil generates an inductive current that is opposite to the capacitive fault current and, in the ideal case, compensates for it at the fault location.

5.2 Circuit design

This chapter investigates earth faults in small cable networks with resonant neutral grounding. The principal 110 kV example is designed for a nominal earth-fault compensation current of 300 A. In normal operation, network asymmetry produces only a small neutral displacement voltage and therefore a small Petersen-coil current. During a solid earth fault, approximately the full phase-to-earth voltage appears between the transformer neutral and earth, and the coil supplies approximately its rated current.

Unless stated otherwise, the transformer is unloaded. The earth fault is applied at 205 ms. The voltage-source parameter `texp` is used to establish steady state rapidly before the fault. The model contains a Yd5 transformer whose parameters are defined in the ltspice file `Transformer_110k_10k.asc`

5.3 Compensated 110 kV Network Without a Fault

5.3.1 Adjustment of the Petersen Coil

The simulation file is `Petersen_without_Fault_TRAN.asc` (see figure 5.1). The network has a phase-to-earth capacitance of 5 012 nF per phase. At 50 Hz, its capacitive reactance is

Calculation 5.1 – (Petersen-coil rating from the network capacitance)

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \cdot 50 \text{ Hz} \cdot 5\,012 \text{ nF}} \approx 635.1 \, \Omega, \quad (5.1)$$

$$I_C = \frac{U_{LL}/\sqrt{3}}{X_C} = \frac{110 \text{ kV}/\sqrt{3}}{635.1 \, \Omega} \approx 100 \text{ A RMS}. \quad (5.2)$$

For a single-phase earth fault, the total capacitive earth-fault current is approximately three times the phase charging current. Resonant compensation therefore requires

$$I_P \approx 3I_C = 300 \text{ A}, \quad (5.3)$$

$$X_{L,P} = \frac{X_C}{3} \approx \boxed{211.7 \Omega}. \quad (5.4)$$

The Petersen-coil model accepts the nominal line-to-line voltage and compensation current directly; set these to 110 kV and 300 A.

5.3.2 Neutral Displacement Voltage in the Transient Analysis

Even without a fault, unequal phase-to-earth capacitances produce a neutral displacement voltage across the Petersen coil. In this example, its peak is approximately 1.2 kV peak, much smaller than the rated phase voltage. The greater the difference between the phase capacitances, represented in the model by CE+CE1 and CE, the higher this voltage becomes.

The displacement voltage rises slowly and shows a beat frequency of approximately 1.2 Hz. This indicates that the resonant frequency is not exactly 50 Hz. In the LTspice waveform viewer, the beat frequency can be read by drawing a zoom window between two adjacent maxima and observing the frequency in the status line. (See figure 5.2)

5.3.3 Corrected Petersen-Coil Setting

The capacitance-only calculation in calculation 5.1 is correct for an ideal transformer, but the complete resonant circuit is not optimally compensated with a 300 A coil. The transformer short-circuit reactance on the primary side, $X_{1s} = 30.25 \Omega$ (see Transformer_110k_10k.asc), reduces the neutral voltage available across the coil to 48.8 Hz. The coil nominal current must therefore be increased to approximately 315 A to get again 50 Hz. This can be verified by simulating with Petersen_without_Fault_AC.asc. (See figure 5.3)

Now we set the initially chosen value of 1E20 for the magnetic reluctance of the tank to a reasonable value of 1e6. After simulation we see that the resonant point is again lower than 50 Hz

We choose now 328 A for the Petersen coil. We restart the simulation. Now we see that the resonant point is again at about 50 Hertz. We have seen now that the sum of all cable capacities is not the sum of all Petersen current values because of the inner resistances of the transformer. We have to add about 10% for the Petersen current value to compensate for the voltage drop at the starpoint.

Remark 5.1 – (Phase information in AC analysis)

In practice: The automatic Petersen is usually operated with very slight over- or under-compensation to prevent resonant effects Also the Petersen automatic is switched off if an earth fault occur

5.3.4 Reason about the reduction of the starpoint voltage

The reason for the reduced neutral-point voltage when adding the magnetic reluctance of the transformer tank lies in the additional secondary leakage flux and the corresponding voltage drop across the leakage reactance. This further decreases the effective neutral-point voltage. You can

clearly see this in the file `Petersen_with_fault_hierarchical_model_AC.asc`. Click on the transformer symbol and then on the symbol for the primary winding. Then measure the current through RPhis. This gives approximately 9 mA. Perform the same measurement for the secondary winding. The current there is 7 mA increasing now the sum of all leakage fluxes. The Resonant frequency is about 47.9Hz. (See figure 5.4)

5.3.5 Resonant Frequency at about 50Hz

This is the resonance of all three phase capacitances with the Petersen-coil inductance and the effective transformer leakage inductance in the zero-sequence path. The coil reactance and inductance are

$$X_P = \frac{U_{LL}}{\sqrt{3}I_P} = \frac{110 \text{ kV}}{\sqrt{3} \cdot 300 \text{ A}} \approx 211.7 \, \Omega, \quad (5.5)$$

$$L_P = \frac{X_P}{2\pi \cdot 50 \text{ Hz}} \approx 0.674 \text{ H}. \quad (5.6)$$

The transformer leakage reactance gives

$$L_{1s} = \frac{30.25 \, \Omega}{2\pi \cdot 50 \text{ Hz}} \approx 0.096 \text{ H}. \quad (5.7)$$

Since the three phase capacitances act in parallel and the three transformer phase inductances contribute as $L_{1s}/3$

Calculation 5.2 – (Resonanz at 50Hz without leakage inductance)

$$C_0 = 3 \cdot 5 \, 012 \text{ nF}, \quad (5.8)$$

$$L_0 = L_P + \frac{L_{1s}}{3} = 0.674 \text{ H}, \quad (5.9)$$

$$f_{r,0} = \frac{1}{2\pi\sqrt{L_0 C_0}} \approx \boxed{50 \text{ Hz}}. \quad (5.10)$$

Calculation 5.3 – (Resonanz at 48.8Hz with primary leakage inductance)

$$C_0 = 3 \cdot 5 \, 012 \text{ nF}, \quad (5.11)$$

$$L_0 = L_P + \frac{L_{1s}}{3} = 0.674 \text{ H} + \frac{0.096 \text{ H}}{3}, \quad (5.12)$$

$$f_{r,0} = \frac{1}{2\pi\sqrt{L_0 C_0}} \approx \boxed{48.8 \text{ Hz}}. \quad (5.13)$$

Calculation 5.4 – (Resonanz at 47.9Hz also with secondary leakage inductance)

$$C_0 = 3 \cdot 5\,012 \text{ nF}, \quad (5.14)$$

$$L_0 = L_P + \frac{L_{1s}}{3} + \frac{L_{1s} * 7}{9} = 0.674 \text{ H} + \frac{0.096 \text{ H}}{3} + \frac{0.096 \text{ H} * 7}{9}, \quad (5.15)$$

$$f_{r,0} = \frac{1}{2\pi\sqrt{L_0 C_0}} \approx \boxed{47.95 \text{ Hz}}. \quad (5.16)$$

The resonant peaks for 48.8Hz and 47.95Hz can also be observed in the file `Petersen_without_fault_AC.asc`, by setting `rkessel` to `1e6` or `1e20`. For the calculation of the resonant frequencies see also the file `Petersen.asc`

5.4 Low-Resistance Earth Fault in the 110 kV Network

5.4.1 Network Designed for 300 A Earth-Fault Current

The transient simulation is contained in `Petersen_with_fault_TRAN.asc` (see figure 5.6). At fault inception, the phase-R voltage rapidly collapses to zero. The voltages of the two healthy phases rise toward the line-to-line voltage. This transition is accompanied by high-frequency overvoltages and currents. An FFT shows a mixture of dominant components near 260 Hz and 1.2 kHz. (see figure 5.19) .

At this higher frequency, the capacitive reactance decreases and the inductive reactance of the line impedance increases. The capacitive current through the inductive impedance therefore produces an additional voltage rise. The currents flowing toward the transformer are predominantly inductive and approximately in phase with one another. Their inductive character can be recognized because the current maximum lags the corresponding voltage maximum. You can also see that the remaining voltages have a phase difference going from 120 degrees to 60degrees (see figure 5.5)

The current at the fault location initially reaches approximately 4.2kA peak (see figure 5.7). It decays rapidly and approaches approximately the longtime value of about 4 A peak. Its minimum also depends on the ohmic resistance of the Petersen coil, set by `r_x`. In `Petersen_with_Fault_AC.asc`, the minimum fault current is approximately 3 A RMS near 50 Hz (see figure 5.8). Set the vertical axis to linear scaling to read this minimum accurately. You can also see that the voltage magnitude of phase A is zero, and that Phase B and Phase C are at 110kV, which is the phase-to-phase voltage. Additionally, the phase of Phase B is -150 degrees and Phase C is +150 degrees. The difference is $-150 - 150 = -300 = +60$ degrees, just as we observed earlier. (see figure 5.5)

The prefault capacitive reactive power is approximately -6.4 Mvar per phase, or -20 Mvar in total (see figure 5.7). Immediately after the phase A fault, the high-frequency recharging process briefly drives the phase B and phase C values to approximately -40 Mvar. However, immediately after the fault, the capacitive reactive power is superimposed by the inductive reactive power of the short-circuit current. The reason for the doubling of the capacitive reactive power is that the two capacitances of the healthy phases are suddenly subjected to a voltage that is the square root of three times the normal voltage. At the end of the transient processes, the additional capacitive reactive power is again compensated by the Petersen reactor. In addition, the inductive reactive power decays to zero. In the end, the reactive power is exactly the same as it was at the

beginning.(see figure 5.7 and 5.8)

Remark 5.2 – (Phase information in AC analysis)

The relative phase angles of voltages and currents are most accurately examined in the AC-analysis files, where the fundamental-frequency phasors are not obscured by the switching transient.

5.4.2 Reactive Power detailed

The capacitive reactive power of the network is approximately

$$Q_C = \sqrt{3} U_{LL} I_C = \sqrt{3} \cdot 110 \text{ kV} \cdot 100 \text{ A} \approx 19 \text{ Mvar.} \quad (5.17)$$

It can be measured with the `qmeter_uvw` element. Each phase contributes approximately –6.3 Mvar, with small differences caused by the unequal capacitances and the resulting unequal phase voltages (This is the reason for the starpoint voltage). The waveform viewer shows approximately 110 kV, 111.7 kV, and 110.7 kV after the model's display scaling by $\sqrt{3}/\sqrt{2}$. Their mean is slightly above 110 kV because the capacitive current produces a voltage rise across the inductive line impedance.

Remark 5.3 – (Waveform-viewer units and scaling)

Multiplying a power trace by 1W/1V can be used to change the displayed unit prefix in the waveform viewer. If `sfactor=3` is selected in `qmeter_uvw`, the measured values are multiplied internally by three, which may simplify comparison with the total three-phase power.

5.4.3 Reactive-Power Increase at Fault Inception

During the earth fault, the two healthy phase-to-earth capacitances are charged to approximately the line-to-line voltage, while the capacitance of the faulted phase is discharged. Since capacitive reactive power is proportional to voltage squared, the total capacitive reactive power of the healthy phases is ideally twice the prefault three-phase value. The source current therefore also rises correspondingly.

After the transient, one part of this increased capacitive earth-fault current is compensated by the Petersen coil. The ordinary positive-sequence charging current remains supplied by the source.

5.4.4 Additional Transformer Loading with Petersen current

The Petersen-coil current flows through the transformer windings and therefore adds to the transformer loading. In the example, its equivalent contribution is approximately 100 A per phase, while the rated primary current is approximately 200 A. Because this current is predominantly inductive, it must be added vectorial to the load current. For the assumed load, whose reactive component is about one fifth of its active component, approximately 75 % of the original load capability remains. In addition, we must take into account the high secondary-side circulating current resulting from the inclusion of the oil tank to our simulation. This can be seen best in the file `Petersen_without_fault_hierarchical_model_TRAN/AC.asc`. Here you have

to right click on the transformer symbol, then choose open-schematic. Now (after simulation run) you can measure the secondary current at the secondary winding of the transformer.

5.4.5 Loaded and Unloaded Transformer

Changing the load parameter from $20\text{e-}6$ to $40\text{e}6$ reduces both the phase voltages and the transformer neutral voltage. Since the voltage across the cable capacitances decreases at the same time, the compensation tuning remains almost unchanged. The comparison is implemented in `Petersen_with_fault_with_load_vs_without_load_AC.asc`. (see figure 5.9 and 5.10)

5.5 High-Resistance Earth Fault

The AC-analysis file `Petersen_with_fault_highohmic_AC.asc` compares the earth-fault resistances $50\ \Omega$, $100\ \Omega$, $500\ \Omega$, and $1\ 000\ \Omega$. At the resonance point, all current curves approach approximately 3 A, representing the residual ohmic component of the compensated earth-fault current. (see figure 5.11 and 5.12)

5.6 Comparison of coupled and uncoupled line impedance

We now load the file `Petersen_fault_coupled_uncoupled.asc`. After simulation we see that the short circuit current peak in the coupled case is smaller than in the uncoupled case. The difference is about 1 kA. The steady state current at the end of the simulation is the same for the two cases. This shows that simulating a asymmetric fault the coupling of the lines has to be considered. For computing of the coupled impedance values see also the wxmaxima file `Petersen.asc` (see figure 5.13 and 5.14)

Important 5.1 – (Asymmetric faults)

It is important by simulating asymmetric faults always to use coupled line models.

5.7 Compensated 10 kV Network with a grounding Transformer

A Yd transformer does not provide an accessible neutral on its delta-connected side. An external neutral-forming transformer, represented by `Trafo_gnd`, creates a neutral point in the medium-voltage network so that a Petersen coil can be connected. The corresponding simulation files are

- `Petersen_Trafo_gnd_TRAN.asc`,
- `Petersen_Trafo_gnd_AC_fault.asc`,
- `Petersen_Trafo_gnd_AC_no_fault.asc`.

We now see a 10 kV compensated network with external star point builder transformer. You see a Petersen in a medium voltage network. Due to the star point builder, a YD transformer can establish a star point at the secondary side for connecting a Petersen coil. Now Some words to Petersen on a YY transformer with three leg core. Since the YY transformer has no low ohmic return path for flux in the core of the transformer, the flux have to go through tank and oil. This

is not the goal. Therefore, the star point of a wye/wye transformer should only be loaded by maximum of ten percent of the transformer nominal current. (see figure 5.15 and 5.16) for TRAN analysis and (see figure 5.17 and 5.18) for AC analysis

5.8 Solid starpoint earthing and transformer with fiveleg magnetic core

Open File `FiveLegCore_without_third_winding.asc` If the Y/Y transformer has a five leg core, the star point cannot deliver any current if the second star point is isolated. This is because the low reluctance of the outer legs short the magnetic core for same phased fluxes. If the second star point is also connected, current can flow from one into the other star points, but current should not be exchanged between the two star points. In short, the two star points of a five leg Y/Y transformer should be isolated. Now open file `FiveLegCore_with_third_winding.asc`. Now to star point loading on a Y/Y transformer with five leg core with compensating third winding. The transformer can deliver full current at the star points. There is also no current transfer from one to the other star point.

5.9 Characteristic Resonance Frequencies

Several natural frequencies occur after fault inception. The highest is associated with the discharging capacitance of the faulted phase. A lower frequency appears in the healthy-phase voltages and capacitance currents.

5.9.1 Resonance at 1.2 kHz

This resonant path contains the cable series inductance and the faulted phase capacitance. It is driven mainly through the capacity C12 and the fault position. With $L = 3.5 \text{ mH}$ and $C = 5\,022 \text{ nF}$ follows ..

$$f_r = \frac{1}{2\pi\sqrt{LC}} \approx \boxed{1.2 \text{ kHz}}. \quad (5.18)$$

5.9.2 Resonance at 260 Hz


This is the frequency of the current through the netimpedance and the capacities C10 and C11. With $L = 25 \text{ mH}$ and $C = 5\,012 \text{ nF} \cdot 3$

$$f_r = \frac{1}{2\pi\sqrt{LC}} \approx \boxed{260 \text{ Hz}}. \quad (5.19)$$

For the frequencies see figure 5.19

Middle voltage transformer with petersen 300A (TRAN analysis) wo fault
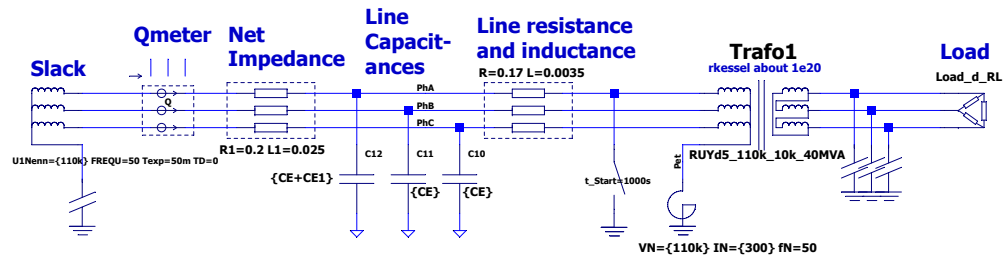
```
.param last=20e6
.param last=20e-6
.param tdtv=1 tdt=1 ce=5012n ce1=10n fn1=50
.options vntol=1m abstol=1m
.tran 0 5s 0 0.1m
.ac lin 1000 40 52
```



$$XC = 1/\omega/C = 1/314.159/5012e-9 = 635.10\Omega$$

$$I_0 = UN/1.73205/635.10\Omega = 100A$$

$$I_E = 3 \cdot I_0 = 300A \text{ (only for cables)}$$

Figure 5.1: Petersen without fault - schematic

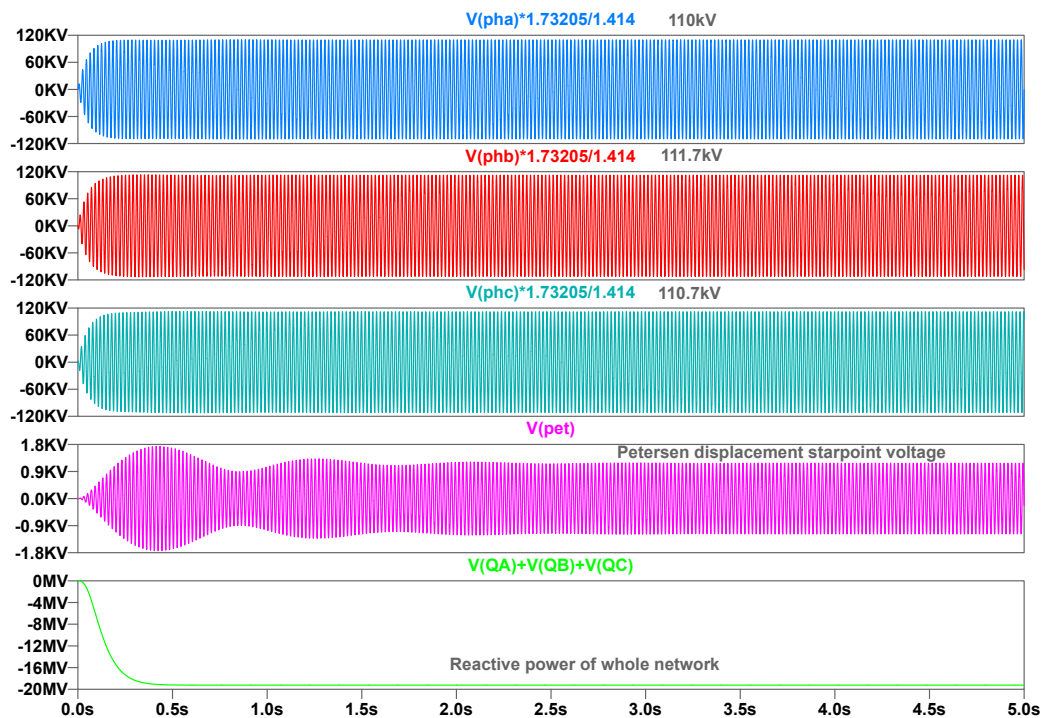


Figure 5.2: Petersen without fault TRAN - waveform

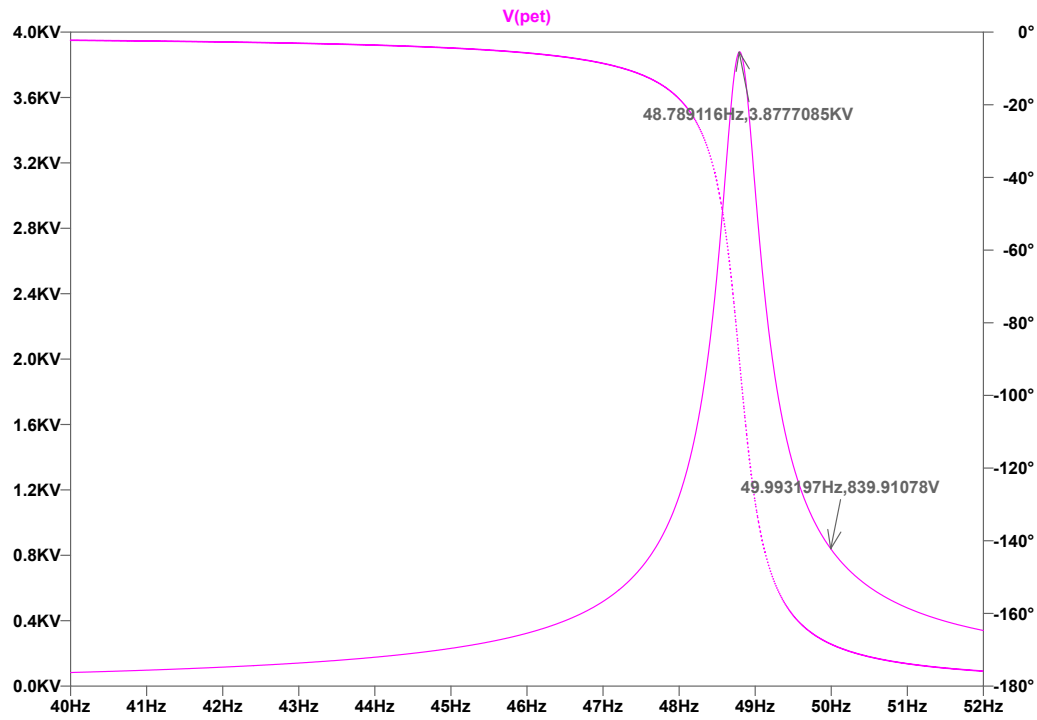


Figure 5.3: Petersen without fault AC starpoint (Petersen) voltage - waveform

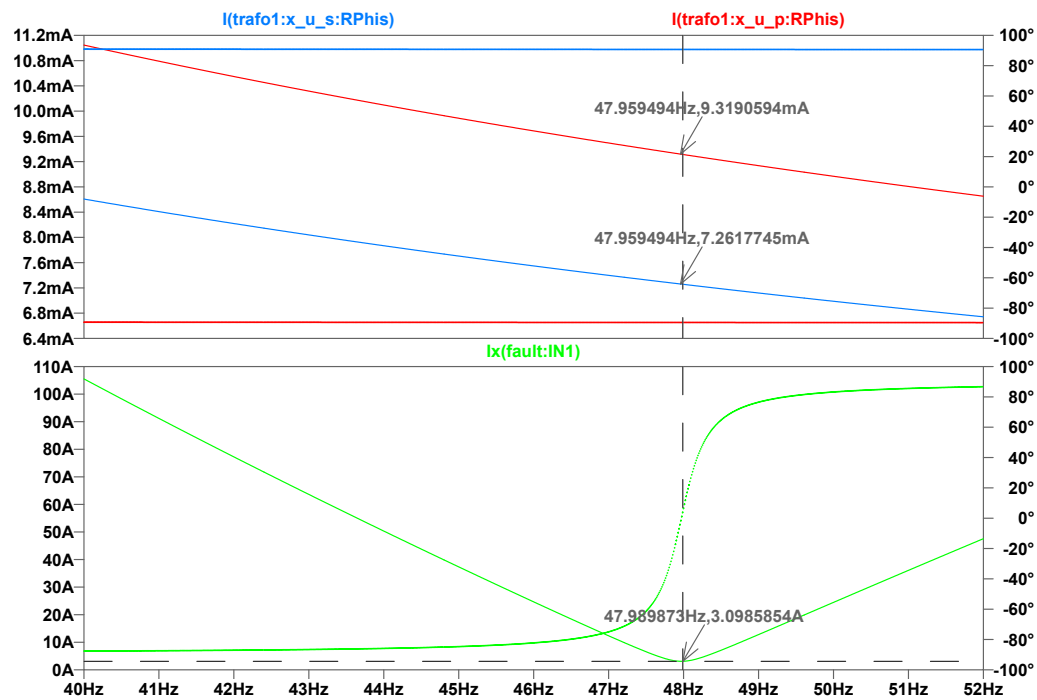


Figure 5.4: Petersen with fault AC hierarchical model - waveform


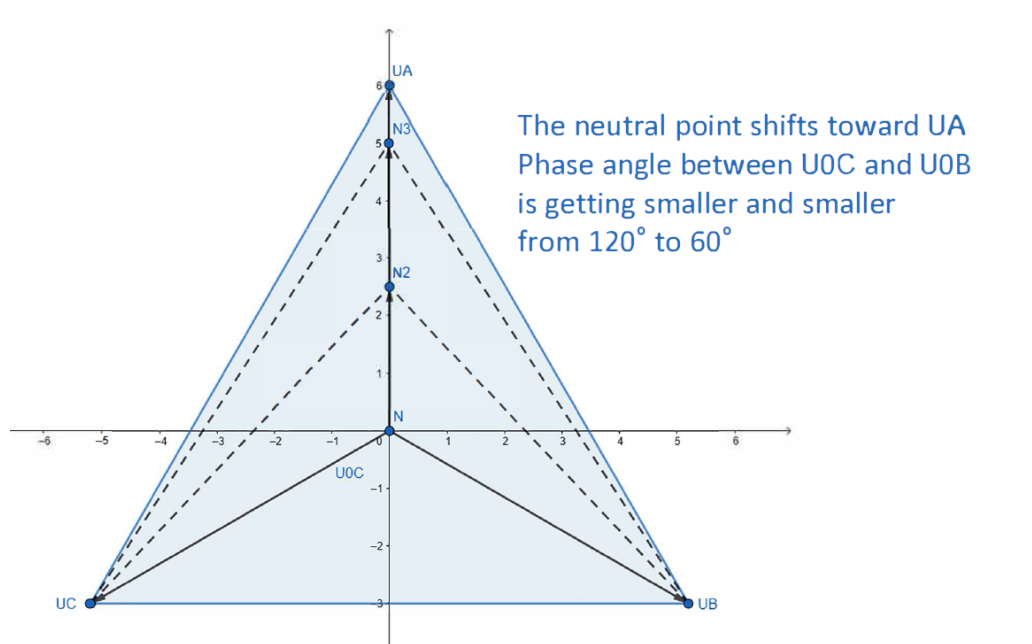


Figure 5.5: Phasedifference of the phase voltages UOB,UOC drawn with GeoGebra

Middle voltage transformer with petersen IN=328A (TRAN analysis)
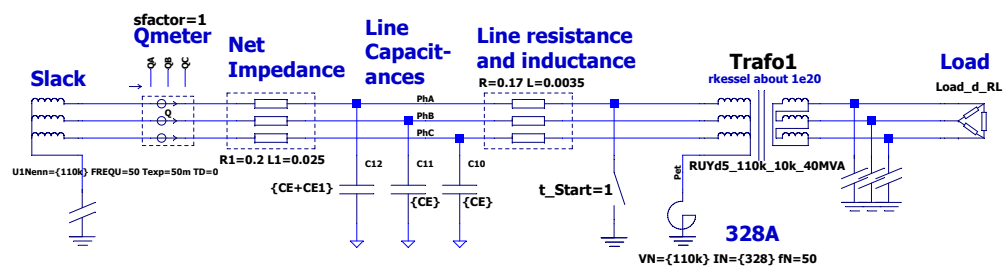
```
.param last=20e6
.param last=20e-6
.param tdtv=1 tdt=1 ce=5012n ce1=10n fn1=50
.options vntol=1m abstol=1u
.tran 0 5s 0 0.1m
.ac lin 1000 40 52
```



$$XC = 1 / \omega C = 1 / 314.159 / 5012e-9 = 635.10 \Omega$$

$$I_0 = U_N / 1.73205 / 635.10 \Omega = 100 \text{ A}$$

$$I_E = 3 * I_0 = 300 \text{ A (only for cables)}$$

Figure 5.6: Petersen with fault TRAN - schematic

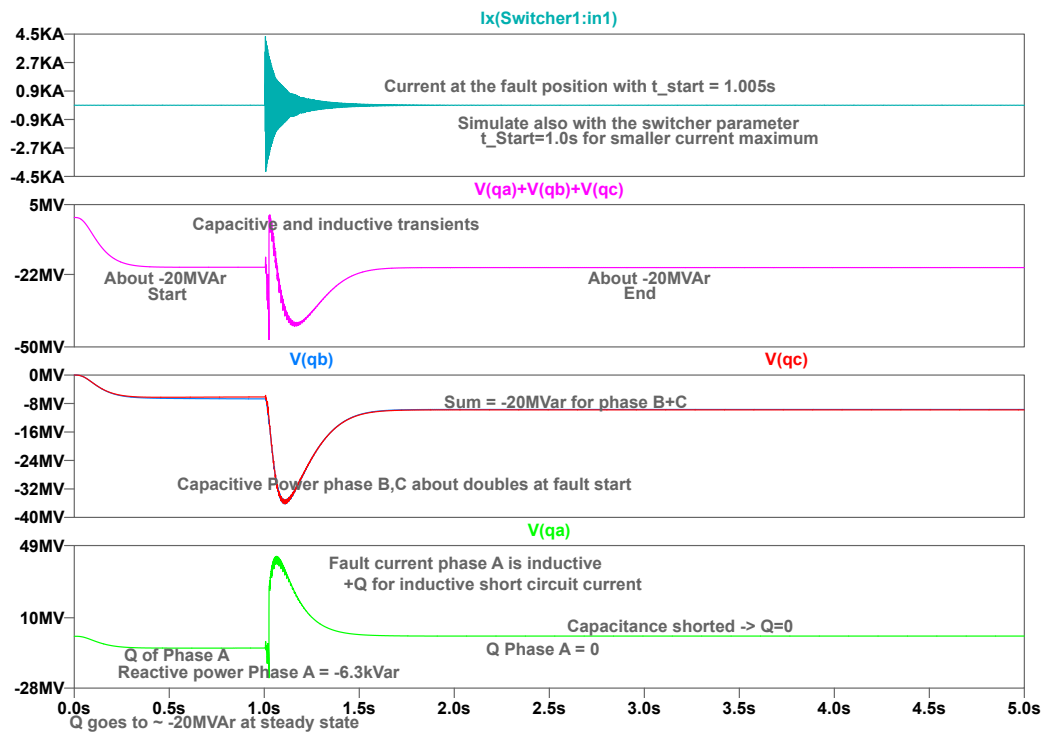


Figure 5.7: Petersen with fault TRAN - waveform

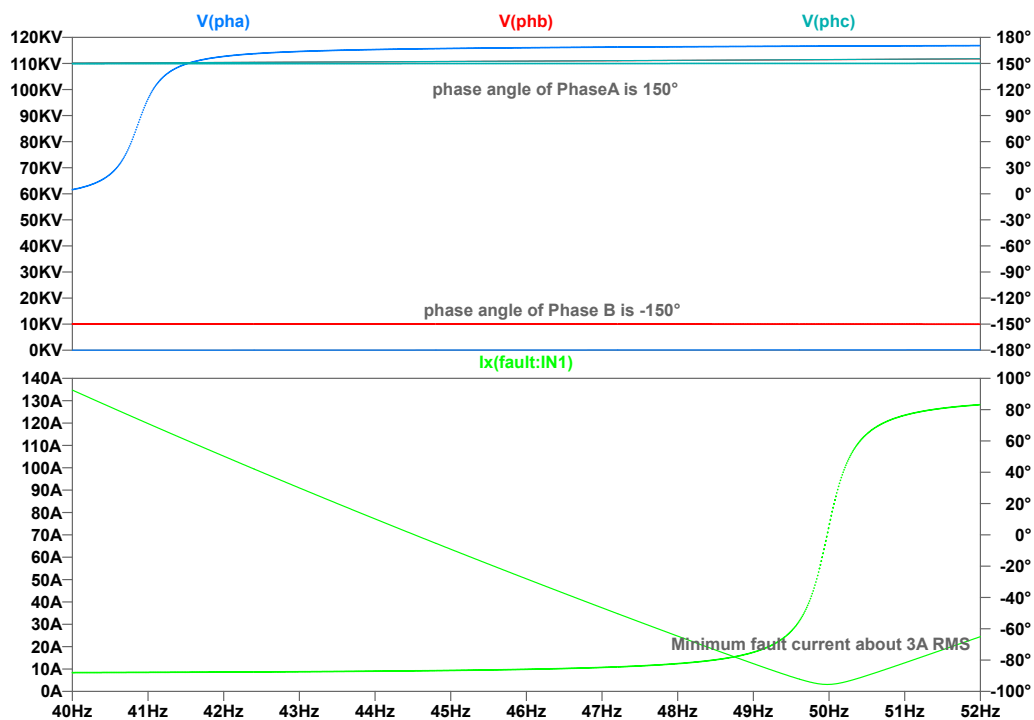


Figure 5.8: Petersen with fault AC - waveform

Petersen with fault loaded vs unloaded (AC-analysis)

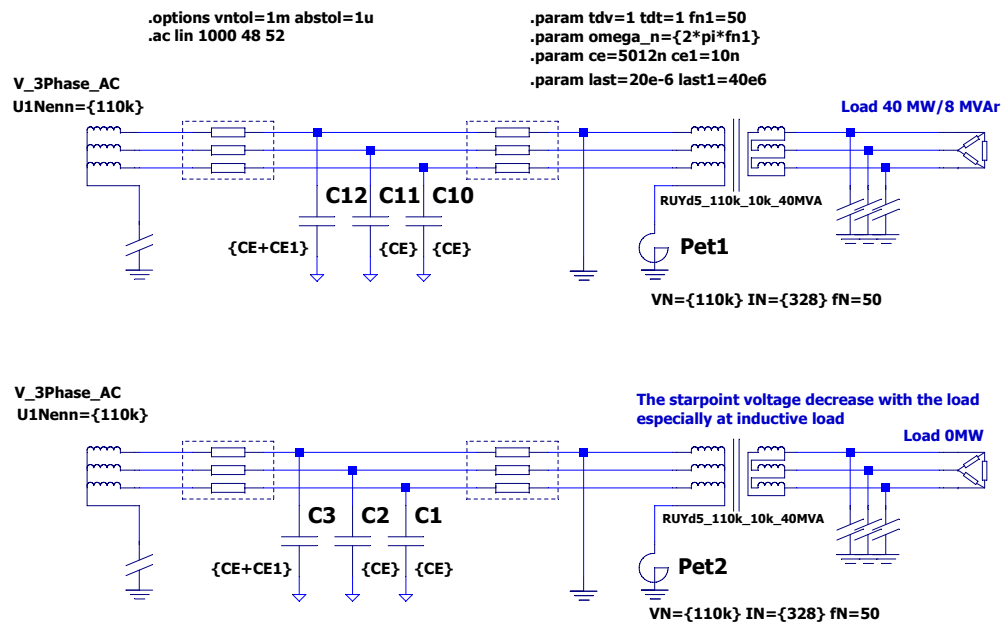


Figure 5.9: Petersen with fault and load AC - schematic

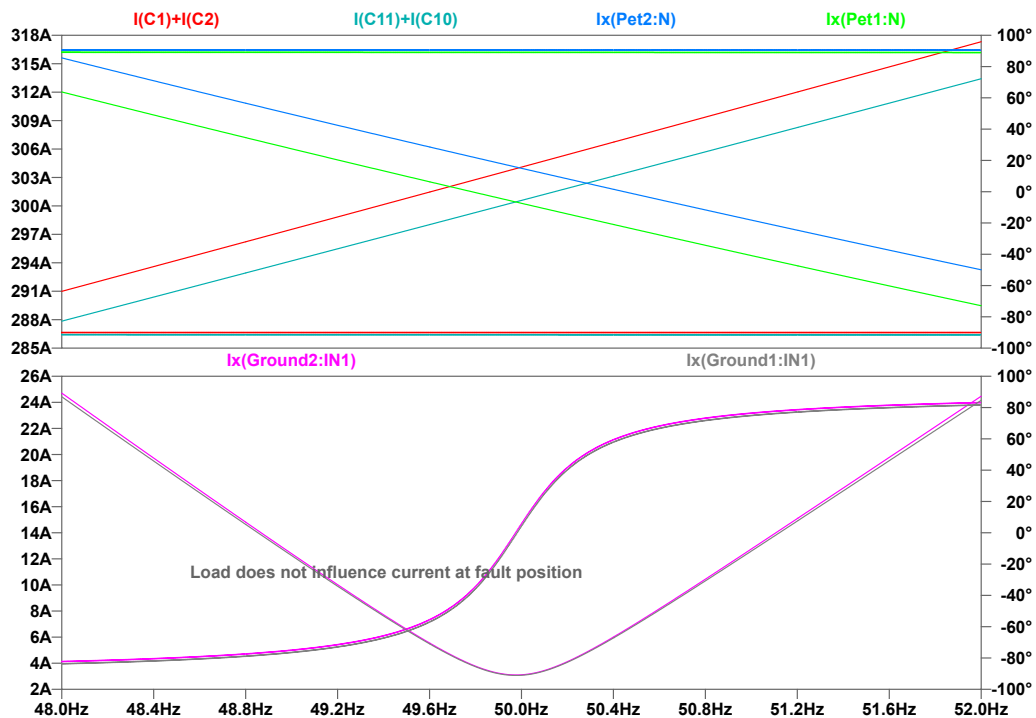


Figure 5.10: Petersen with fault and load AC - waveform

Middle voltage transformer with petersen 328A (AC analysis) with highohmic fault

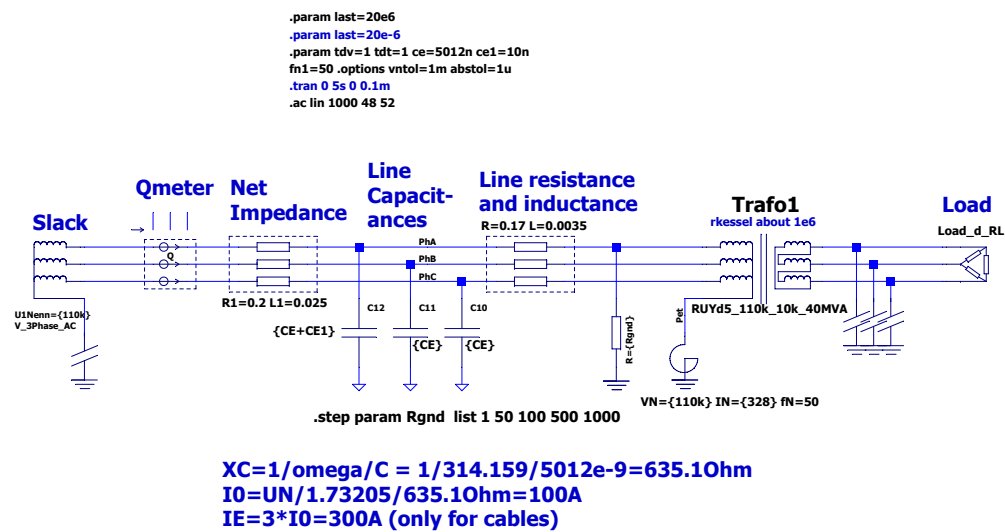


Figure 5.11: Petersen with highohmic fault AC - schematic

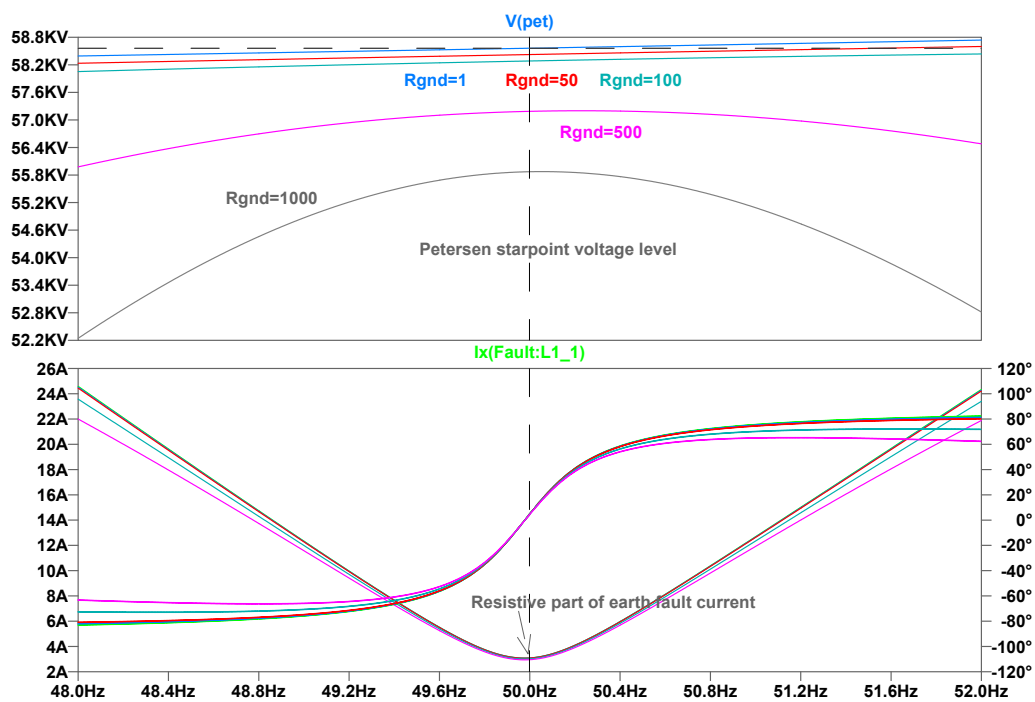


Figure 5.12: Petersen with highohmic fault AC - waveform

You can see that the maximal short circuit current at the fault position is smaller than in the uncoupled case !!!!
HINT: For asymmetric cases always use the coupled lines, impedance models
Comparison of coupled and uncoupled line impedance

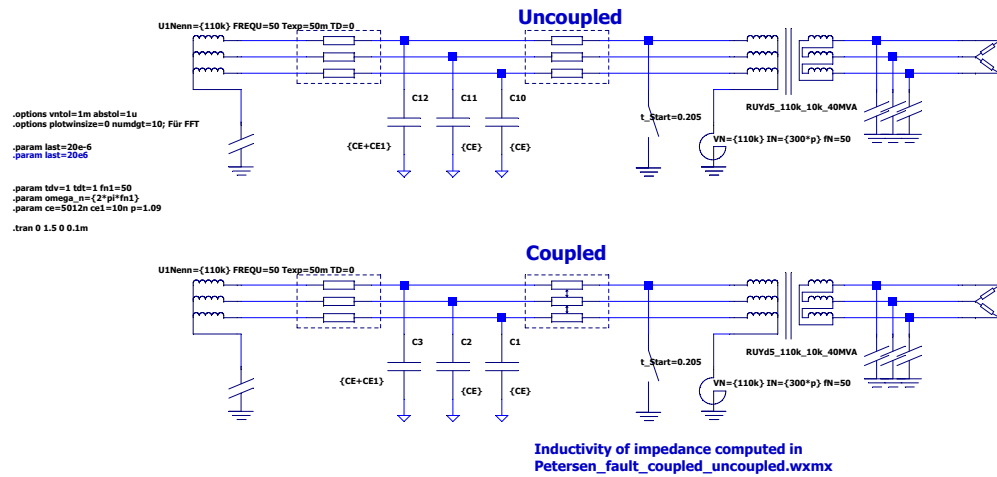


Figure 5.13: Petersen with fault and load AC - schematic

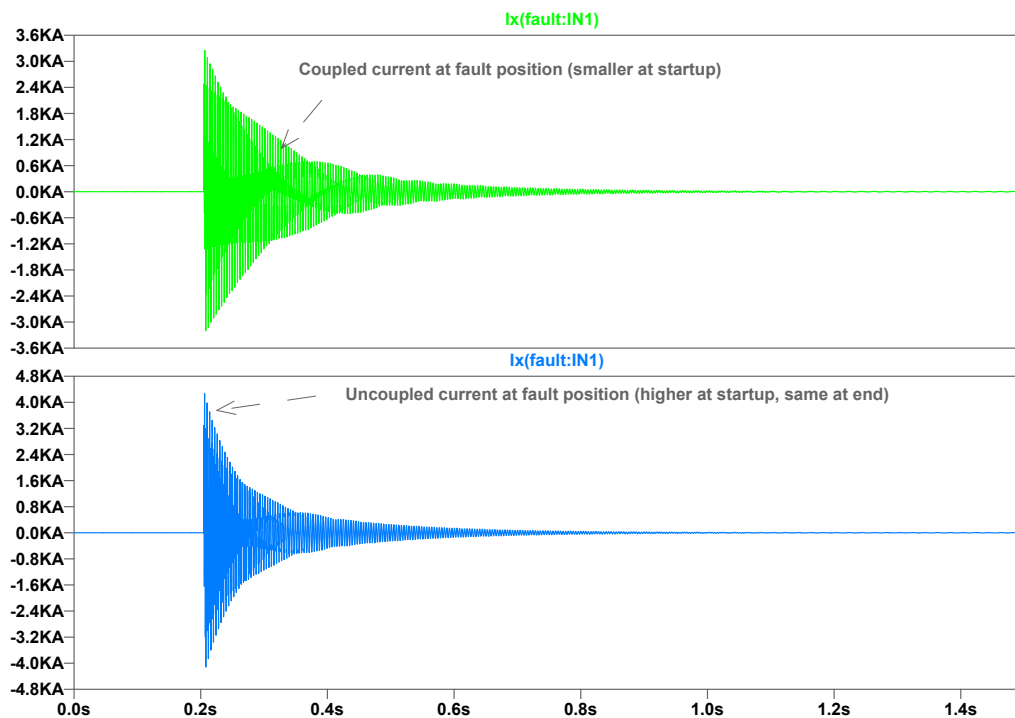


Figure 5.14: Petersen with fault and load AC - waveform

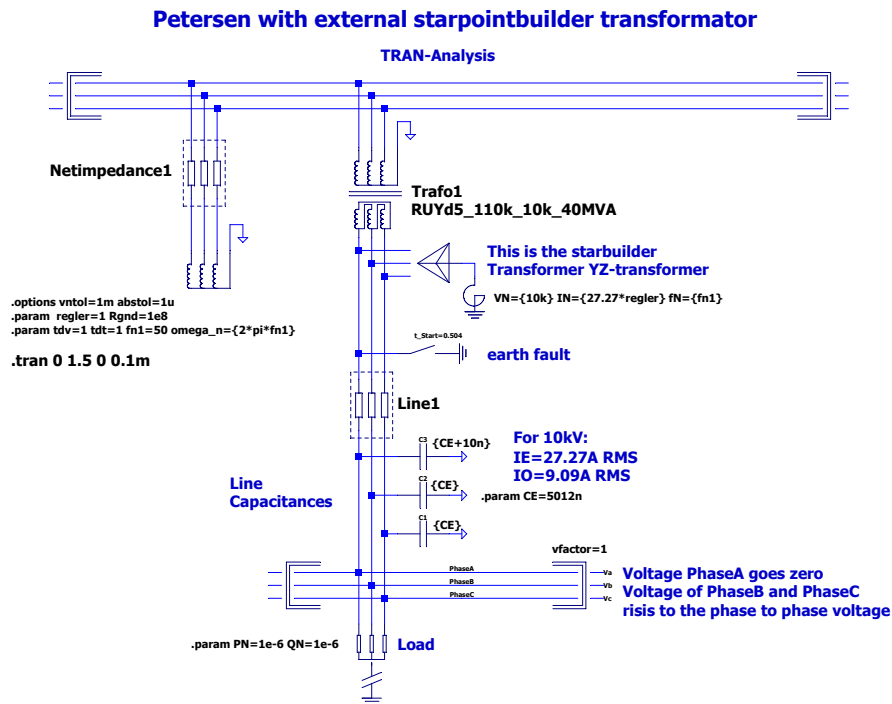


Figure 5.15: Petersen without fault and external petersen starpoint TRAN - schematic

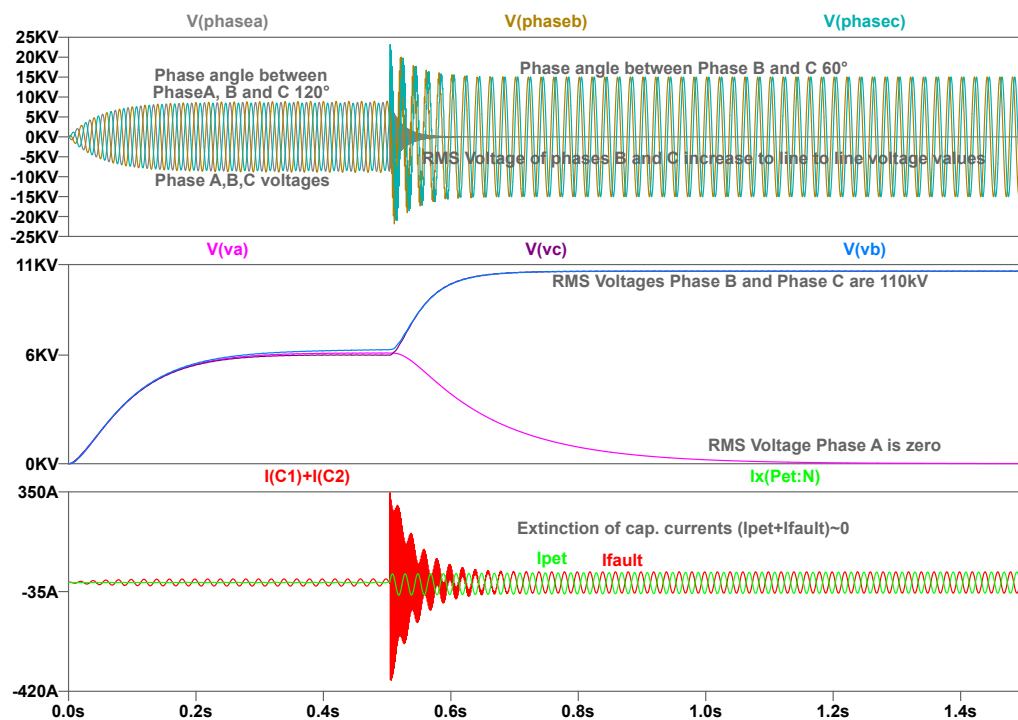


Figure 5.16: Petersen without fault and external petersen starpoint TRAN - waveform

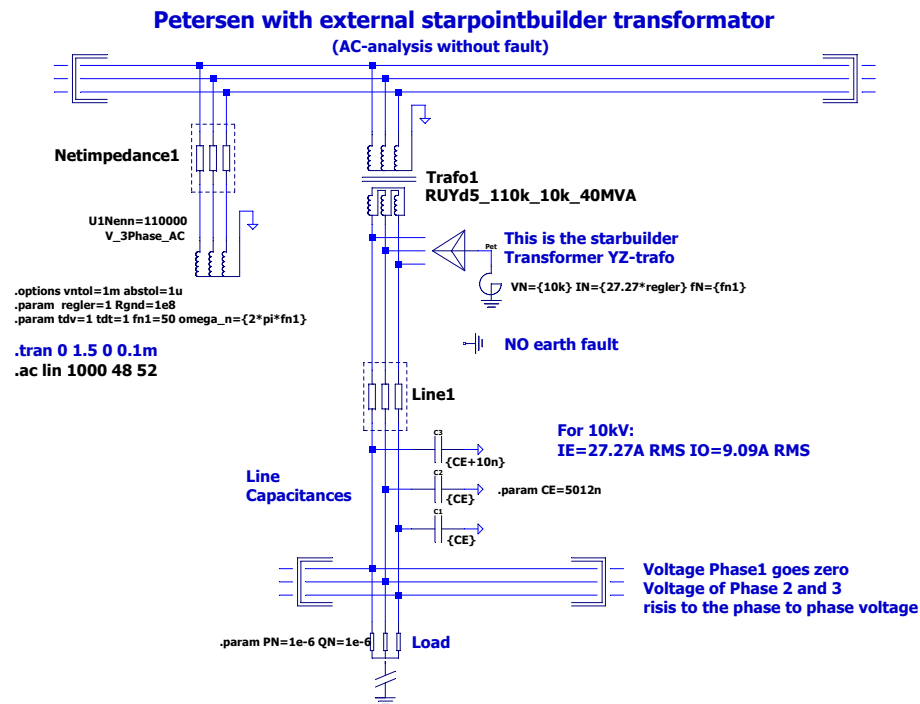


Figure 5.17: Petersen without fault and external petersen starpoint AC - schematic

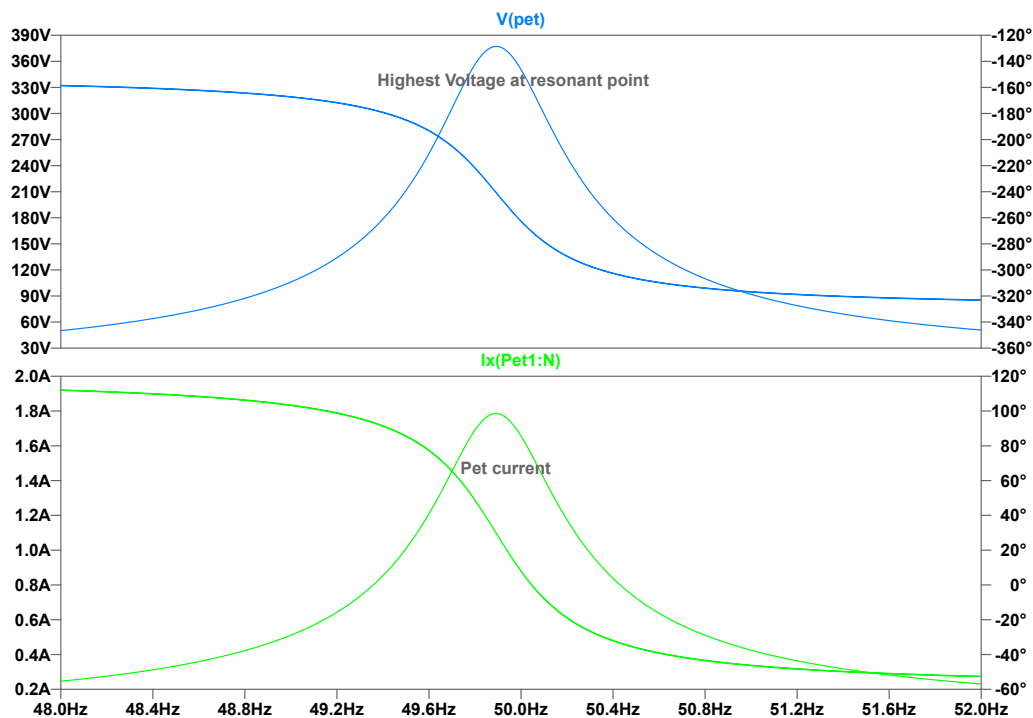


Figure 5.18: Petersen without fault and external petersen starpoint AC - waveform

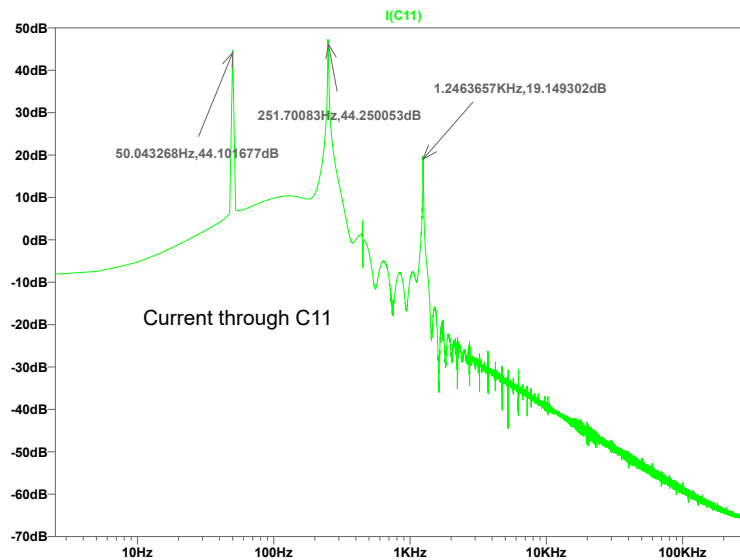


Figure 5.19: FFT of current through capacitor C11

Chapter Summary

In a resonant-grounded cable network, the Petersen coil compensates the zero-sequence capacitive earth-fault current. Network asymmetry creates a small neutral displacement voltage even without a fault. During a solid earth fault (currents like at a shorted circuit at startup), the healthy phases rise toward line-to-line voltage and the capacitive reactive power approximately doubles for the first instant. The complete tuning must include transformer and source impedances, not only the cable capacitance. Fault inception excites several natural frequencies determined by different inductive and capacitive paths. For networks without an accessible neutral, a neutral-forming transformer permits connection of the Petersen coil. High currents are present due to capacitive recharging processes. The capacitor at the faulty phase is shorted. The other two capacitors have now a $\sqrt{3}$ higher voltage. Through the higher frequencies the capacitive resistance is now much smaller $\rightarrow$ high currents flow at the begin. Voltage distortion is present due to higher inductive resistance (higher frequency of about 250Hz or 1.2kHz). At transient processes always higher frequencies are present (resonant frequencies) and therefore the frequency dependent C's and L's changes in height and so does the current level and the voltage drop level. At earth fault the capacitive reactive power of the net is suddenly doubled. This is why now two phases have a phase/phase level voltage and so the reactive power is 2 times the value before fault. This additional reactive power burdens the voltage source only for a short time (also take into account the inductive short circuit current in the faulty phase). At the time rises this additional power is compensated by the Petersen and at the end the same reactive power is reached as at startup. NOTE: In this example the inductances (impedance model) of the line are not assumed coupled. Due to coupling the impedance rise in the faulty phase. Therefore the short circuit current at the begin will be a bit smaller as computed.

6 Switching Whole Networks

6.1 General

This chapter examines the transients that occur when an entire network (grid zone) is energized. This situation can occur during grid restoration following a blackout. The following cases are examined in detail:

- Connecting at minimum voltage in phase R,
- Connecting the grid zone with phase R at maximum voltage,
- Connecting at minimum voltage and full remanent flux,
- Connecting with the main transformer set to minimum voltage,
- Connecting a larger grid zone,
- Connecting under load.
- Connecting with skin effect in the grid impedance,
- Connecting with a weak feed-in,
- Slowly ramping up the voltage instead of a switching operation.

6.2 Circuit Design

The example is a 110 kV network with five substations. Three substations are loaded; two are unloaded or have loads that are not yet connected. The network is supplied through a 220 kV/110 kV transformer rated 200 MV A.

The main transformer is represented by a linear magnetizing characteristic using $m=1$. Its voltage source initially rises exponentially so that the transformer reaches steady state before the network switch closes. The network contains three cable sections and two overhead-line sections. The cables have a total length of 10 km and generate approximately 15 Mvar of capacitive reactive power. A 40 Mvar shunt reactor with 15 Mvar overcompensates this power, leaving a net inductive demand of approximately 25 Mvar. The energized network therefore tends to reduce rather than raise the voltage (valid for steady state)

The cable phase-to-earth capacitances are compensated by a Petersen coil at substation 1. A small capacitance asymmetry is required to create a measurable neutral displacement voltage. In the model, this is introduced with the parameter *cuf* in phase 1 of line 2.

6.3 Petersen-Coil Setting

The cable capacitance is 400 nF/km per phase. For a total cable length of 10 km, the phase capacitance is 4 000 nF.

Calculation 6.1 – (Compensation current for the complete cable network)

At 50 Hz,

$$C = 400 \text{ nF/km} \cdot 10 \text{ km} = 4\,000 \text{ nF}, \quad (6.1)$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \cdot 50 \text{ Hz} \cdot 4\,000 \text{ nF}} \approx 796 \, \Omega, \quad (6.2)$$

$$Q_C = \frac{U_{LL}^2}{X_C} = \frac{(110 \text{ kV})^2}{796 \, \Omega} \approx 15.2 \text{ Mvar}. \quad (6.3)$$

For resonant earth-fault compensation,

$$X_{L,P} = \frac{X_C}{3} \approx 265 \, \Omega, \quad (6.4)$$

$$I_P = \frac{U_{LL}/\sqrt{3}}{X_{L,P}} \approx \boxed{239.7 \text{ A}}. \quad (6.5)$$

The model uses a rounded setting of 250 A. An increase of roughly 5 % is useful because internal transformer reactance reduces the neutral voltage and prevents the ideal coil current from being reached during an earth fault. This effect was discussed in detail in [Chapter 5](#).

6.4 Calculation of the Network Resonance

The inductances specified on the 220 kV side must be referred to the 110 kV side. With a voltage ratio of 2, impedance and inductance are divided by $2^2 = 4$ when referred from the 220 kV side to the 110 kV side. The source and transformer inductances are $L_{\text{net}} = 0.0077 \text{ H}$ and $L_{\text{Tr}} = 0.154 \text{ H}$. The transformer value is obtained from `xkos/omega` in `Trafo_YY0_220k_110k_200MVA_Daten.asc`. Thus, ..

Calculation 6.2 – (Dominant cable-network resonance)

$$L_{\text{eq}} = \frac{L_{\text{net}}}{4} + \frac{L_{\text{Tr}}}{4} = \frac{0.0077 \text{ H} + 0.154 \text{ H}}{4} = 0.04 \text{ H}, \quad (6.6)$$

$$C = 4\,000 \text{ nF}, \quad (6.7)$$

$$f_r = \frac{1}{2\pi\sqrt{L_{\text{eq}}C}} \approx \boxed{395.8 \text{ Hz}}. \quad (6.8)$$

This result agrees with the approximately 400 Hz peak which can be best observed in the FFT of the main transformer current of phase B,C of the simulation of case1 zooming from 40ms to 100ms and choose view/FFT (current zoom extent) Some other harmonics due to nonlinear transformer currents can best be seen in Phase A with 100Hz,150Hz,200Hz and 250Hz

6.5 Rated current of the main transformer

The rated RMS current on the 220 kV side of the main transformer is

$$I_N = \frac{S_N}{\sqrt{3}U_N} = \frac{200 \text{ MVA}}{\sqrt{3} \cdot 220 \text{ kV}} \approx \boxed{525 \text{ A}}. \quad (6.9)$$

For further values of transformer parameters see:

Transformer_110kV_10KV.asc and

Transformer_220kV_110KV.asc

6.6 Case 1: Closing at the Phase-R Voltage Zero

Set $t_0=0$. The network switch closes at 40 ms, when the phase-R voltage crosses zero. The primary phase-R current of the main transformer is then dominated by the magnetizing inrush currents of the medium-voltage transformers. Closing at voltage zero produces the largest unidirectional flux offset. Even without residual flux, the transient flux can approach twice its steady-state peak starting from zero to about 0.58 Wb.

At the same instant, the phase-R (U) capacitive charging current is comparatively small because the applied voltage is close to zero. In phases S (V) and T (W), the opposite situation occurs: the instantaneous voltages are high, their medium voltage transformer flux offsets are smaller, and their initial cable-charging currents are large. The principal currents decay over approximately 500 ms. The overvoltages depend strongly on the switching instant.

All three phase currents contain high-frequency components caused by resonances between the cable capacitances and the source and transformer inductances. An FFT of a phase A medium-voltage-transformer current also contains many harmonics (100Hz,150Hz,200Hz,250Hz) of the power frequency because of the nonlinear transformer magnetizing curves. In phases S and T, a distinct network resonance appears at approximately 400 Hz.

All three medium voltage transformer currents exhibit similar but also slightly different behavior. Since a Petersen coil is connected to the neutral point of Transformer 1, the inrush current runs partially below the zero line. For Transformer 2, a faster decay of the inrush current can be observed. This can be explained by the additional voltage drop caused by the shunt reactor current on Line 2. In Phase A, the shunt reactor carries a current that runs entirely above the zero line (in phase with the transformer). This current causes a greater voltage drop across Line 2 and thus a lower voltage across the transformer. Since the flux of the transformer depends directly on the integral of the voltage, both the flux and the current of the transformer decrease. NOTE: The behavior described above occurs only if the shunt reactor is turned on simultaneously with the transformer. If the shunt reactor is turned on 10 ms later, its current is out of phase with the transformer current, and the inrush current of the transformer will now decrease more slowly or even rise slightly at first. Try it out by inserting a switch with a switching time of 50 ms before the shunt reactor.

Line 4 is a overhead line (so line3) and the cap. inrush is very small compared to the cables. For Schematic and waveforms see figures 6.1 till figures 6.6. For Measurement values and signal ranges see table: 6.1.

Case1 : Closing at Phase-R Voltage Zero

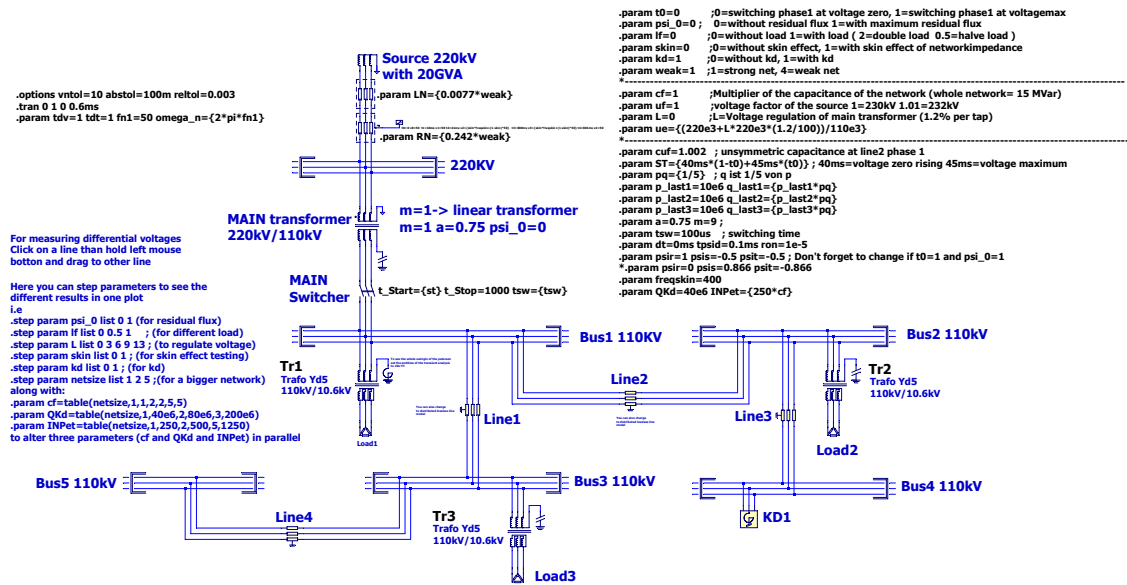


Figure 6.1: Switching on networks schematic

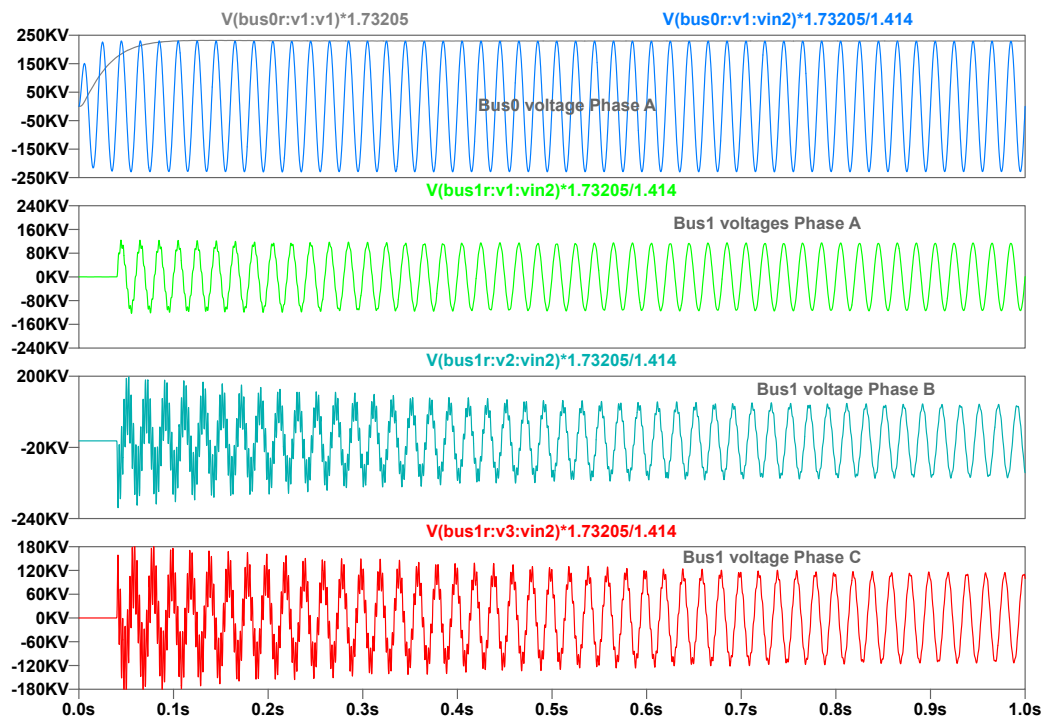


Figure 6.2: Switching on networks voltages - case1

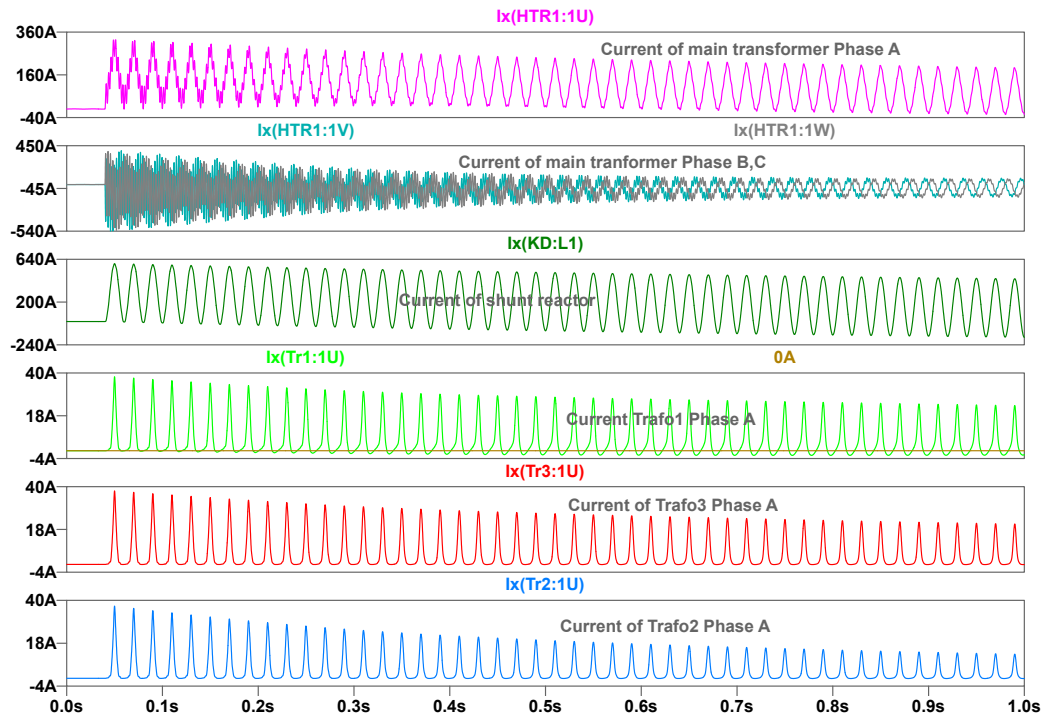


Figure 6.3: Switching on networks currents - case1

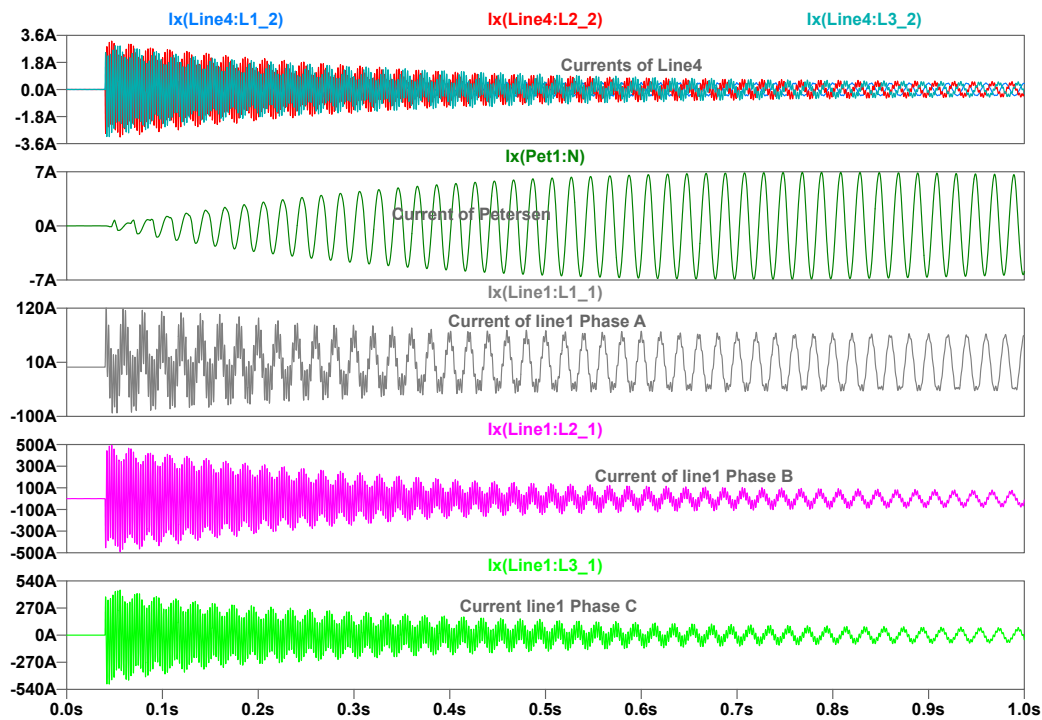


Figure 6.4: Switching on networks currents line1, line4 - case1

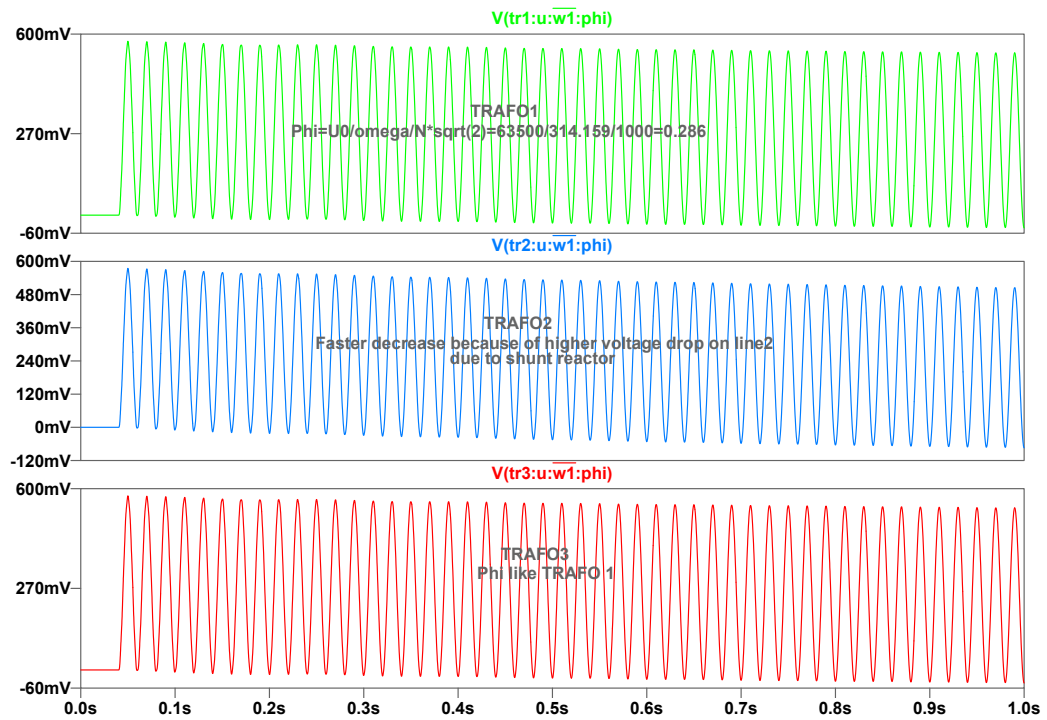


Figure 6.5: Switching on networks fluxes - case1

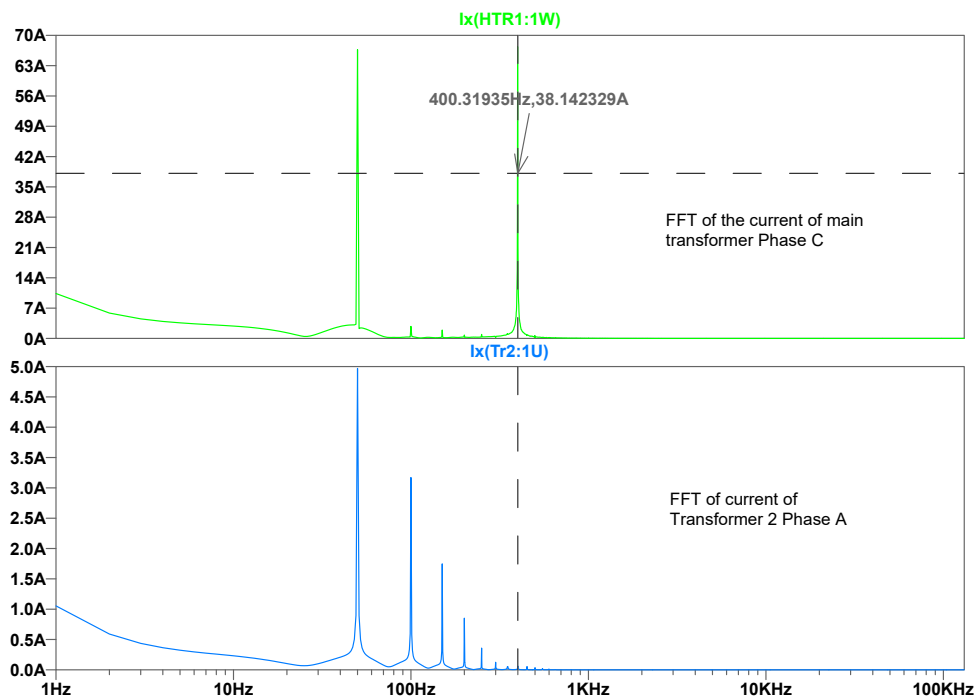


Figure 6.6: Switching on networks FFT - case1

Table 6.1: signal values case1, min-max values are all peak values, but Bus0-Bus1 values are RMS values

Meas.	Grid element	Phase	Voltage level	Min.	Max.	Notes
V	Bus0	Ph A	220 kV	-229 kV	229 kV	-
V	Bus1	Ph A	110 kV	-100 kV	100 kV	-
V	Bus1	Ph B, C	110 kV	-200 kV	200 kV	-
I	HTr1	Ph A	220 kV	0 A	330 A	-
I	HTr1	Ph B, C	220 kV	-540 A	360 A	-
I	KD1	Ph A	110 kV	0 A	600 A	Steady state: 300 A
I	Tr1	Ph A	110 kV	-2 A	38 A	Due to Petersen values under zero line
I	Tr2	Ph A	110 kV	0 A	37 A	Due to KD1: faster decrease of current
I	Tr3	Ph A	110 kV	0 A	37 A	-
I	Line4	Ph B, C	110 kV	-3 A	3 A	Small capacitive inrush current due to overhead line
I	Line1	Ph B, C	110 kV	-500 A	500 A	High capacitive inrush current due to cable
I	Line1	Ph A	110 kV	-100 A	120 A	-
I	Pet1	Ph N	110 kV	-7 A	7 A	Longtime value very small
V	Pet1	Ph N	110 kV	-1.8 kV	1.6 kV	Longtime value very small
Φ	Tr1	Ph A	110 kV	0 Wb	0.576 Wb	Nominal flux: 0.288 Wb
FFT	HTr1	Ph C	220 kV	50 Hz	400 Hz	Only 50 Hz and 400 Hz
FFT	Tr2	Ph A	110 kV	50 Hz	250 Hz	50 Hz, 100 Hz, 150 Hz, 200 Hz, and 250 Hz

6.7 Case 2: Closing at the Phase-R Voltage Maximum

Set $t_0=1$. Phase R now closes near its voltage maximum. Its initial capacitive charging current measured at the main transformer primary side is maximal, while its transformer 1,2,3 magnetizing inrush is minimal because the corresponding flux begins close to its natural steady-state trajectory. Phases S and T contain mixtures of cable-charging and transformer-magnetizing currents. The currents of the main transformer decay toward steady state within approximately 500 ms. The largest voltage peak occurs in phase R, while phases S and T show similar, smaller peaks.

The primary currents of the main transformer remain approximately at the level of Case 1. The inrush currents of medium-voltage transformers 1, 2, and 3 are now minimal in Phase A and higher and roughly equal in Phases B and C for transformers 2 and 3, but remain smaller than the inrush currents in Phase A at the switching time $t_0 = 0$. Since the Petersen current of Transformer 1 becomes quite high at approximately 16 A when $t_0 = 1$, the currents in phases B and C of Transformer 1 differ. The current through the shunt reactor is now symmetrical to the neutral line from the start and is approximately 300 A. The current in Line 1 Phase A is approximately 500 A, and that in Phases B and C is approximately 300 A. The flow in Phases B and C is now at its highest, but not as high as it was in Phase A in Case 1. Therefore the inrush currents of Phase B and C are smaller as in phase A Case1. NOTE: Due to the highly nonlinear magnetic characteristic curve, small changes in the flux values cause large changes in the magnetization currents. For Waveforms see figures 6.7 till figures 6.10. For Measurement values and signal ranges see table: 6.2.

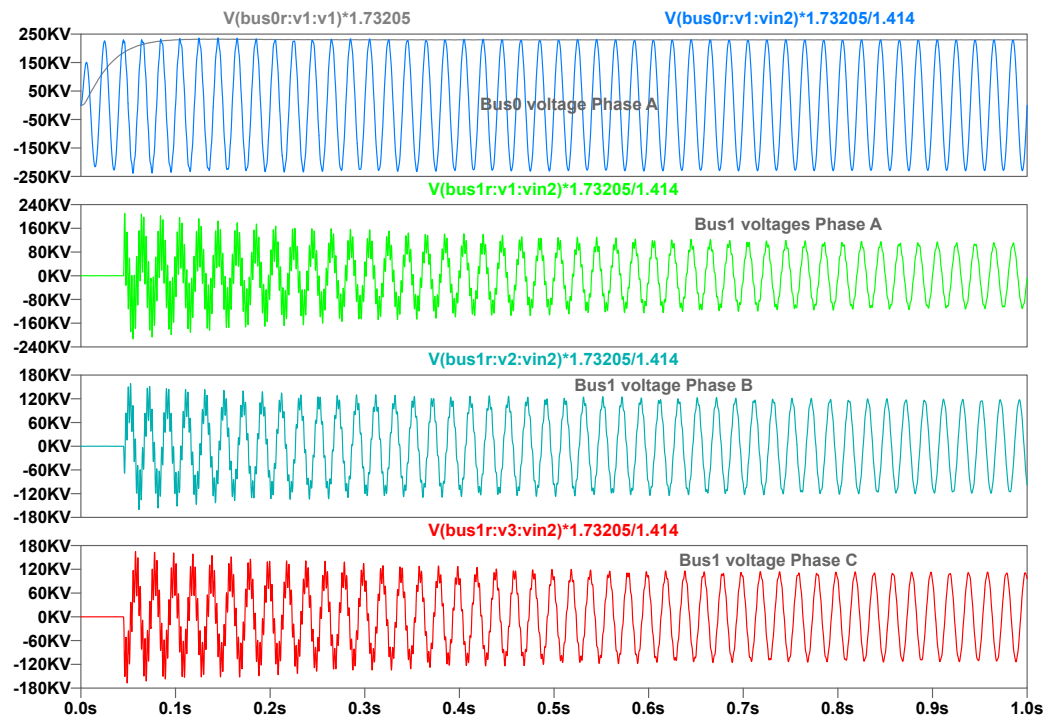


Figure 6.7: Switching on networks voltages - case2

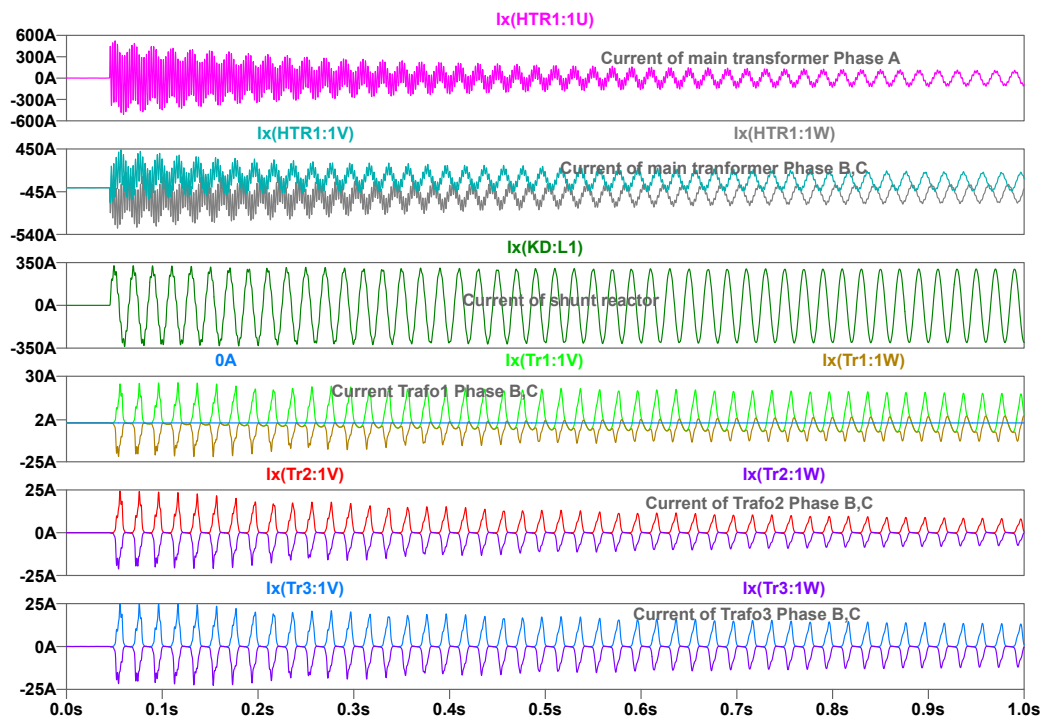


Figure 6.8: Switching on networks currents - case2

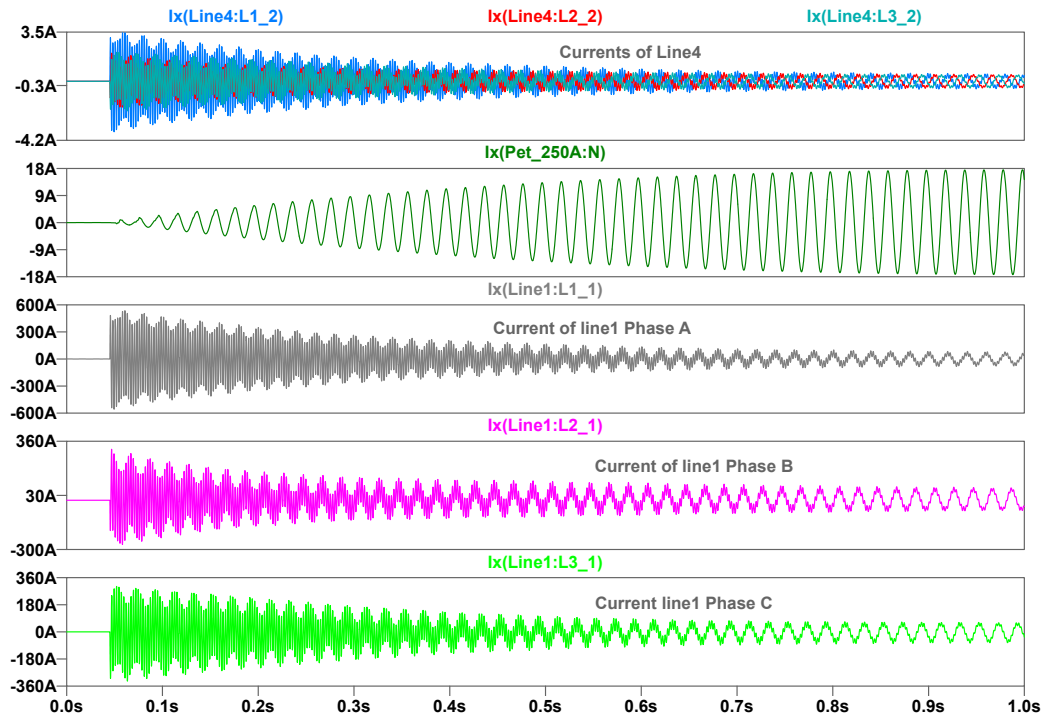


Figure 6.9: Switching on networks currents line1, line4 - case2

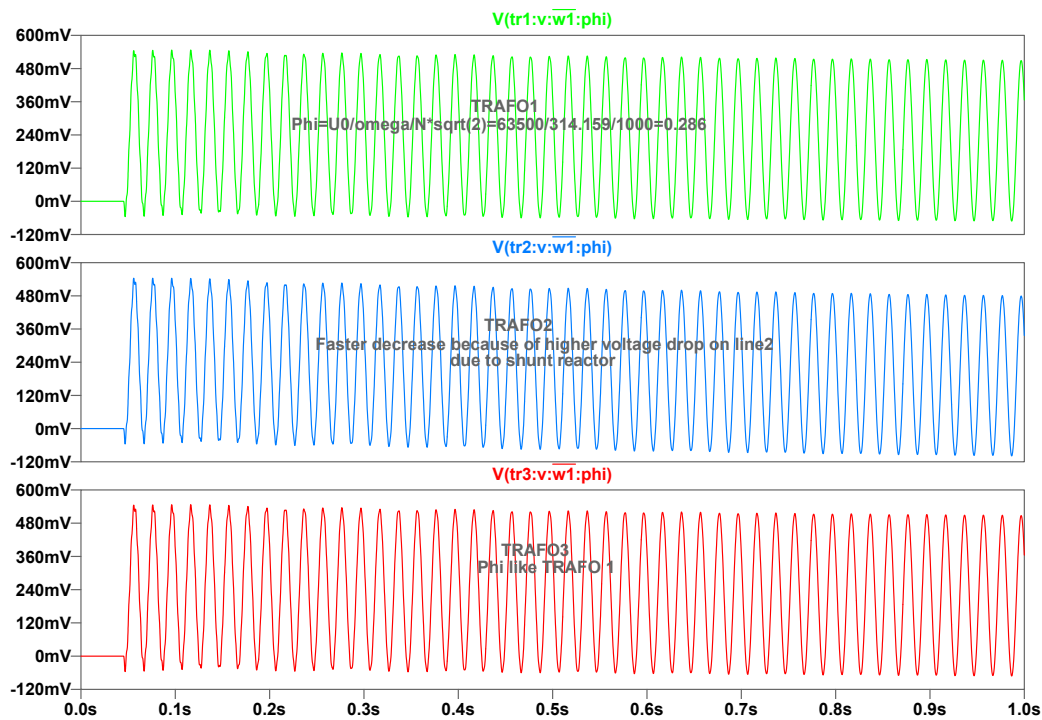


Figure 6.10: Switching on networks fluxes - case2

Table 6.2: signal values case2, min-max values are all peak values, but Bus0-Bus1 values are RMS values

Meas.	Grid element	Phase	Voltage level	Min.	Max.	Notes
V	Bus0	Ph A	220 kV	-229 kV	229 kV	-
V	Bus1	Ph A, B, C	110 kV	-200 kV	200 kV	-
I	HTr1	Ph A	220 kV	-520 A	510 A	-
I	HTr1	Ph B	220 kV	-170 A	460 A	-
I	HTr1	Ph C	220 kV	-470 A	180 A	-
I	KD1	Ph A	110 kV	-300 A	300 A	Steady state: 300 A
I	Tr1	Ph B	110 kV	-4 A	26 A	Due to Petersen values under zero line
I	Tr2	Ph B	110 kV	0 A	25 A	Due to KD: faster decrease of current
I	Tr3	Ph A	110 kV	0 A	25 A	-
I	Line4	Ph A	110 kV	-3.5 A	3.5 A	Small capacitive inrush current due to overhead line
I	Line1	Ph A	110 kV	-500 A	500 A	High capacitive inrush current due to cable
I	Line1	Ph B, C	110 kV	-300 A	300 A	High capacitive inrush current due to cable
I	Pet1	Ph N	110 kV	-18 A	18 A	Longtime value very small
V	Pet1	Ph N	110 kV	-4.5 kV	4.5 kV	Longtime value very small
Φ	Tr1	Ph B, C	110 kV	0 Wb	0.54 Wb	Nominal flux: 0.288 Wb

6.8 Case 3: Closing at Voltage Zero with Full Residual Flux

Set $\psi_{i0}=1$. Phase R then carries a very large combined magnetizing current from the medium-voltage transformers. Measured on the 220 kV side of the main transformer, the peak is approximately 920 A. This exceeds the rated peak current of approximately $\sqrt{2} \cdot 525 \text{ A} = 742 \text{ A}$.

With unfavourable full residual flux, the phase-R flux can approach theoretically three times its normal peak. The theoretical peak could be so about 8.66 Wb. This theoretical peak cannot be achieved in practice. The reason is, on the one hand, the reduced voltage caused by the high current and external and internal voltage drops on the other hand, the reactive secondary circuit current and the leakage flux create additional factors that reduce the voltage. The fast decrease of the currents is due to the nonlinear characteristic of the magnetizing curve

The Petersen-coil of transformer1 neutral voltage initially rises to a high value (about nominal voltage) and then decays slowly. The cause is the large asymmetry of the phase magnetizing currents, which also makes the phase-to-earth voltages asymmetric. The line-to-line voltages are much less affected. If the simulation is extended to 60 s, the magnetizing currents approach their small steady-state values and the Petersen-coil voltage settles to approximately 1 kV to 2 kV.

The very high displacement voltage (reaches nominal voltage), which also slowly builds up at the neutral point of the main transformer, causes a highly asymmetrical voltage in Phase B of the grid. This voltage first rises, then drops to nearly half the rated voltage, and then rises again.

For Waveforms see figures 6.11 till figures 6.14. For Measurement values and signal ranges see table: 6.3.

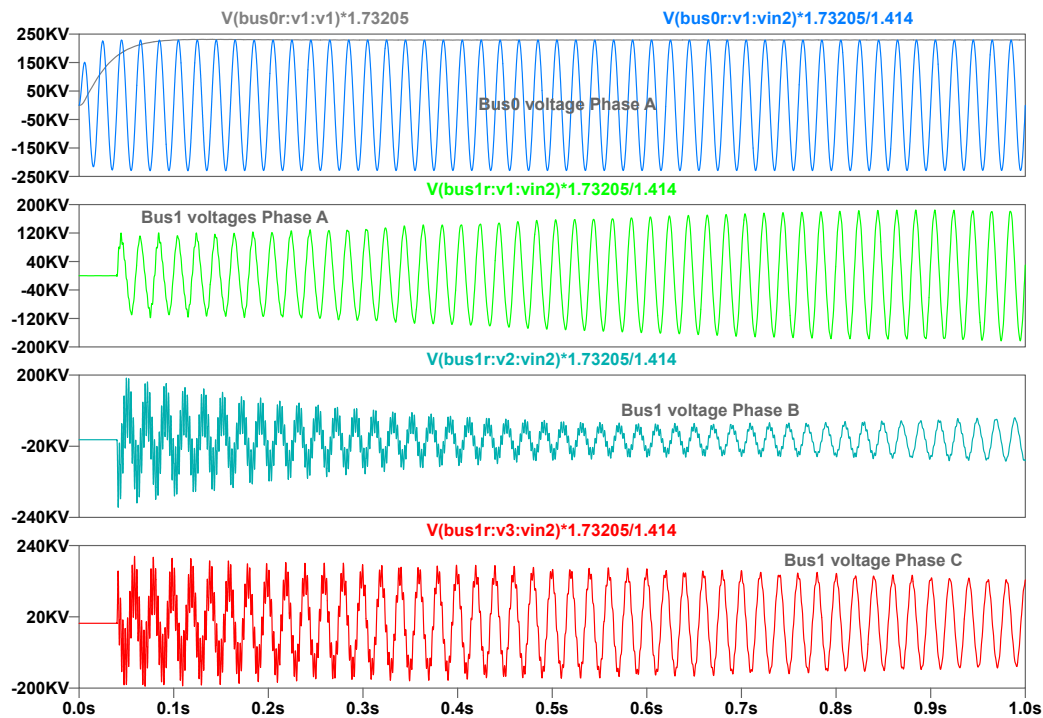


Figure 6.11: Switching on networks voltages - case3

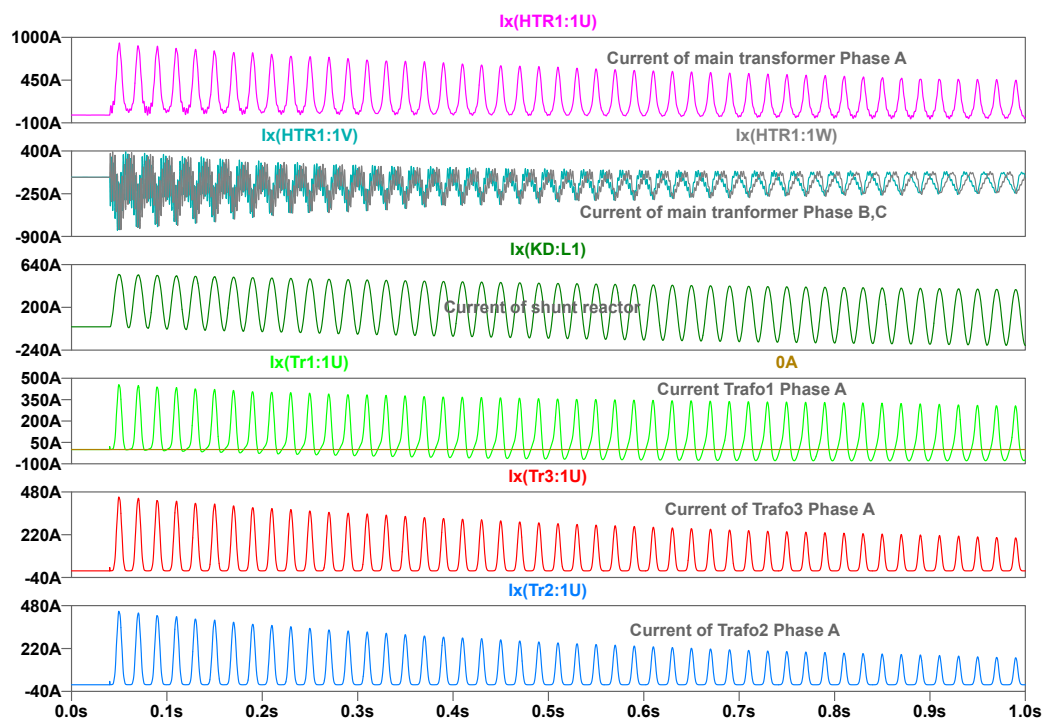


Figure 6.12: Switching on networks currents - case3

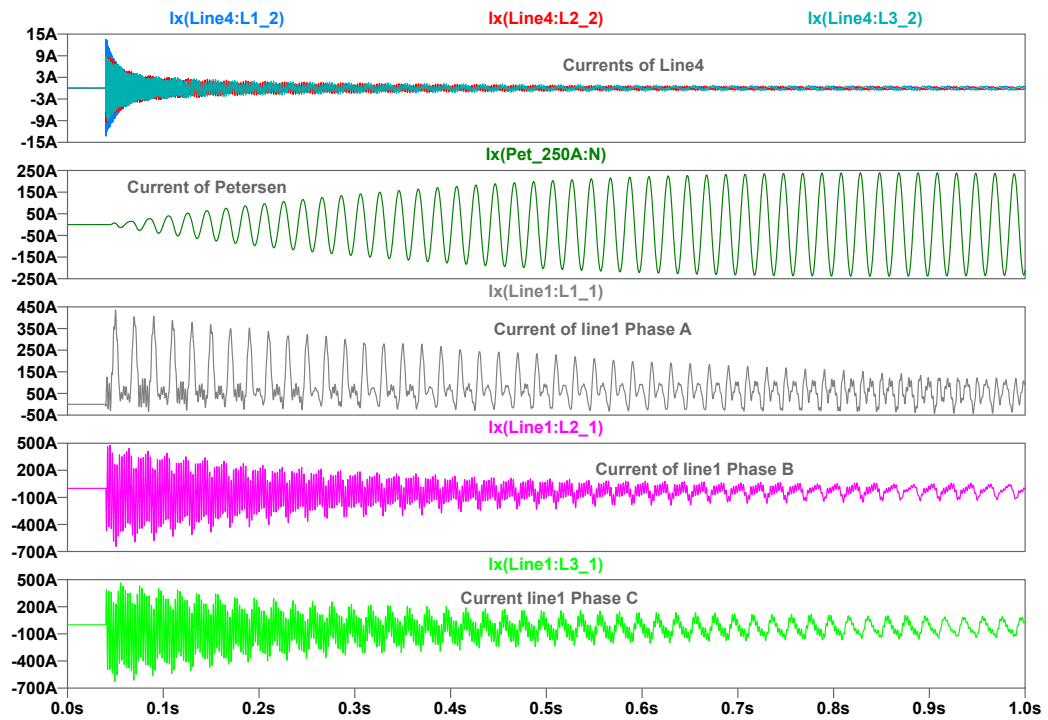


Figure 6.13: Switching on networks currents line1, line4 - case3

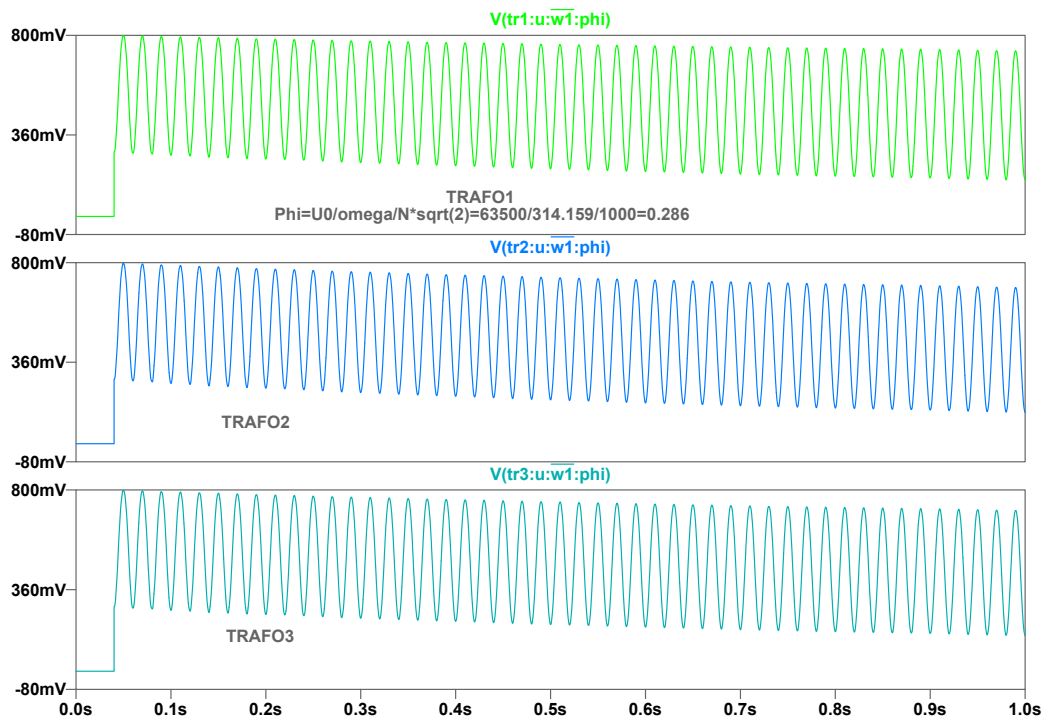


Figure 6.14: Switching on networks fluxes - case3

Table 6.3: signal values case3, min-max values are all peak values, but Bus0-Bus1 values are RMS values

Meas.	Grid element	Phase	Voltage level	Min.	Max.	Notes
V	Bus0	Ph A	220 kV	−229 kV	229 kV	–
V	Bus1	Ph A,	110 kV	−120 kV	120 kV	Startup values low and later higher
V	Bus1	Ph B	110 kV	−200 kV	200 kV	Startup values high and later much smaller than higher again, Steady state: 114 kV
V	Bus1	Ph C	110 kV	−200 kV	200 kV	Steady state: 114 kV RMS
I	HTr1	Ph A	220 kV	0 A	920 A	–
I	HTr1	Ph B	220 kV	−800 A	400 A	–
I	HTr1	Ph C	220 kV	−800 A	400 A	–
I	KD1	Ph A	110 kV	0 A	540 A	Steady state: 300 A
I	Tr1	Ph A	110 kV	−80 A	450 A	Due to Petersen values under zero line
I	Tr2	Ph A	110 kV	0 A	450 A	Due to KD1: faster decrease of current
I	Tr3	Ph A	110 kV	0 A	450 A	–
I	Line4	Ph A	110 kV	−13 A	13 A	Small capacitive inrush current
I	Line1	Ph A	110 kV	−20 A	440 A	High capacitive inrush current due to cable
I	Line1	Ph B, C	110 kV	−500 A	500 A	High capacitive inrush current due to cable
I	Pet1	Ph N	110 kV	−240 A	240 A	Longtime value very small
V	Pet1	Ph N	110 kV	−60 kV	60 kV	Longtime value very small
Φ	Tr1	Ph A, B, C	110 kV	0 Wb	0.8 Wb	Nominal flux: 0.288 Wb

6.9 Case 4: Main-Transformer Tap Position L+13

Set L=13. The altered tap position reduces the secondary voltage of the main transformer. The currents are also lower than in Section 6.6. The maximum flux values are at 500mV also smaller than in case0. The bus1 voltage phase A is about 100kV peak and has practically no 400Hz cap. inrush components. The voltages due to cap inrush of bus1 phase B and C have smaller values (180kV). The current of the petersen are smaller (2.5A) as in case0. The current of line4 is similar to case0. The currents of line1 Phase B,C are at max. 500A The current of phase A of line1 is max. 100A The transformer inrush currents are about max. 11.5A and much smaller compared to case0 since the maximum flux values are also reduced to 500mV (see above).

An FFT shows that the dominant resonance shifts from approximately 400 Hz to 450 Hz. With voltage ratio = 220kV/97kV=2.268 and $t=2.268 \cdot 2.268=5.14$. Compared to calculation: 6.2 the resonant frequency is

Calculation 6.3 – (Dominant cable-network resonance)

$$L_{eq} = \frac{L_{net}}{5.14} + \frac{L_{Tr}}{5.14} = \frac{0.0077 \text{ H} + 0.154 \text{ H}}{5.14} = 0.0314 \text{ H}, \quad (6.10)$$

$$C = 4000 \text{ nF}, \quad (6.11)$$

$$f_r = \frac{1}{2\pi\sqrt{L_{eq}C}} \approx \boxed{448.8 \text{ Hz}}. \quad (6.12)$$

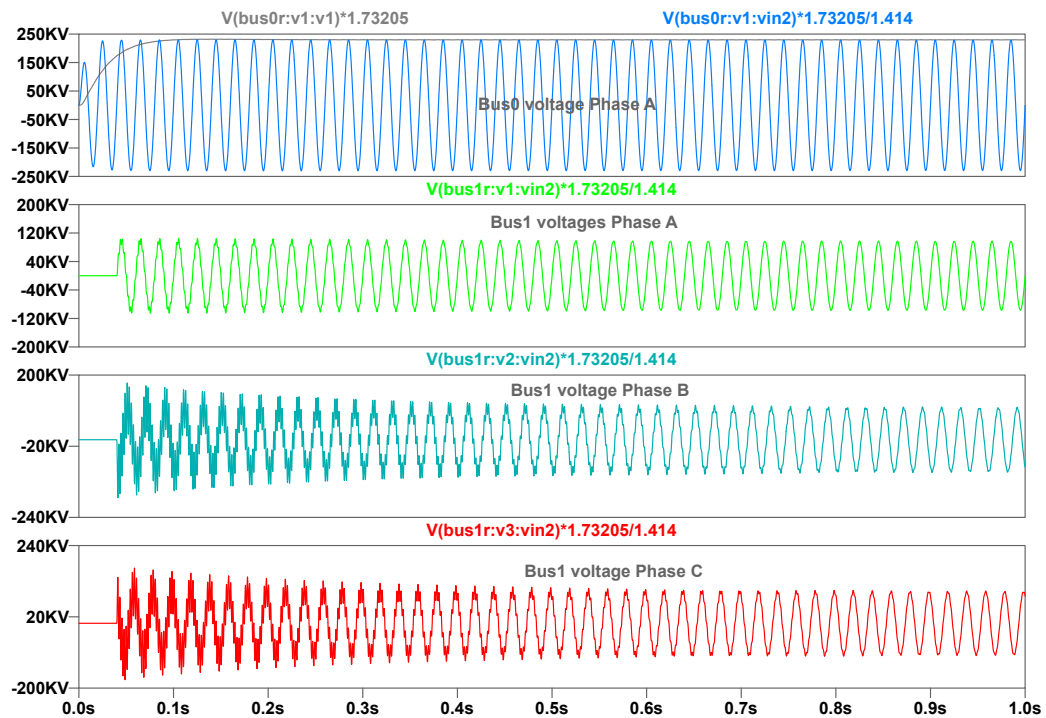


Figure 6.15: Switching on networks voltages - case4

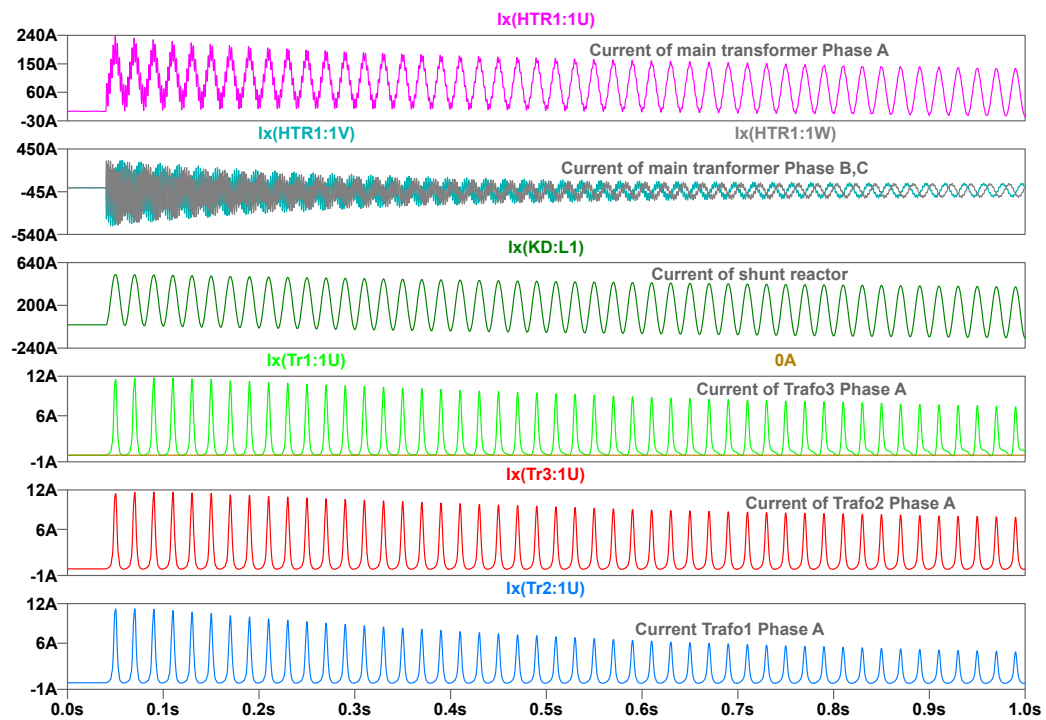


Figure 6.16: Switching on networks currents - case4

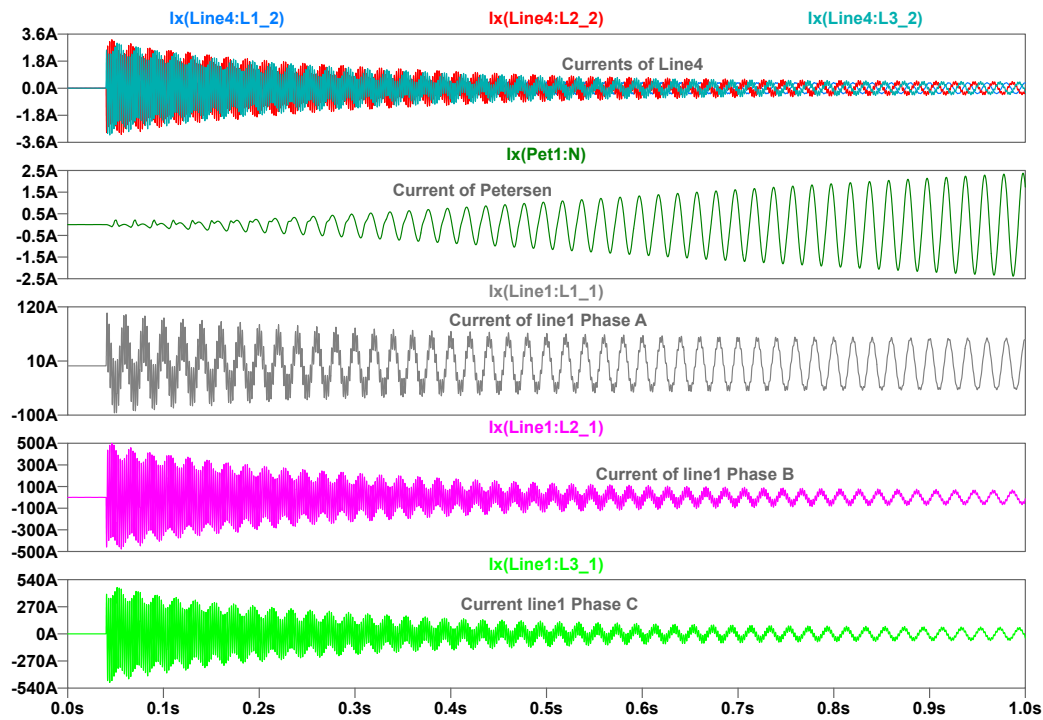


Figure 6.17: Switching on networks currents line1, line4 - case4

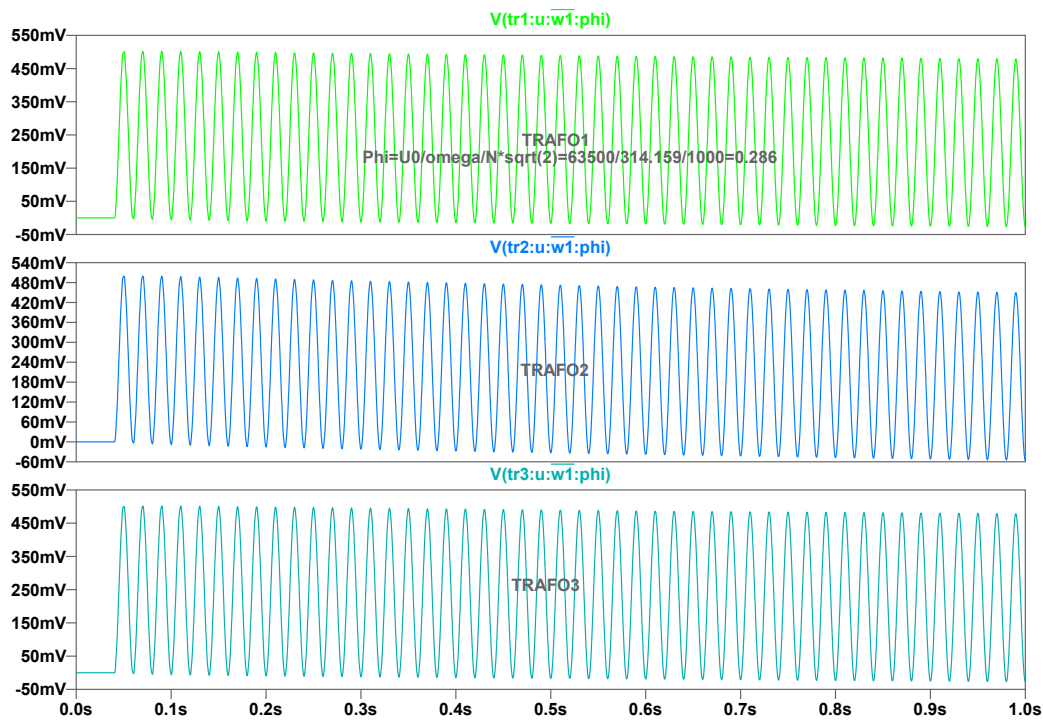


Figure 6.18: Switching on networks fluxes - case4

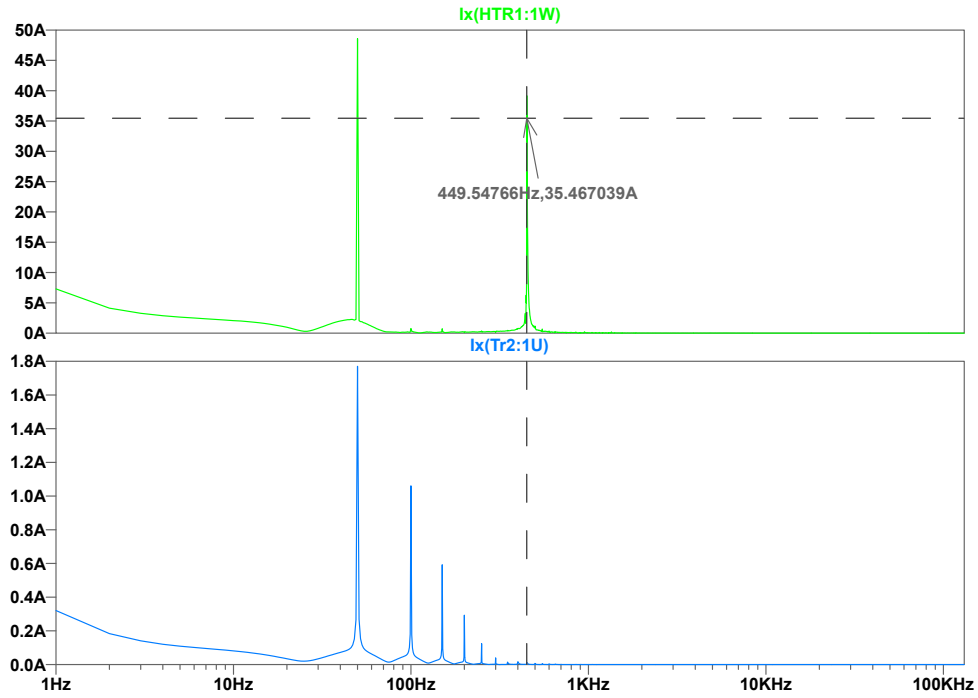


Figure 6.19: Switching on networks FFT - case4

Table 6.4: signal values case4, min-max values are all peak values, but Bus0-Bus1 values are RMS values

Meas.	Grid element	Phase	Voltage level	Min.	Max.	Notes
V	Bus0	Ph A	220 kV	-229 kV	229 kV	-
V	Bus1	Ph A,	110 kV	-100 kV	100 kV	-
V	Bus1	Ph B,C	110 kV	-180 kV	180 kV	-
I	HTr1	Ph A	220 kV	0 A	230 A	-
I	HTr1	Ph B, C	220 kV	-350 A	300 A	-
I	KD1	Ph A	110 kV	0 A	520 A	Steady state: 300 A
I	Tr1	Ph A	110 kV	0 A	11 A	
I	Tr2	Ph A	110 kV	0 A	11 A	Due to KD1: faster decrease of current
I	Tr3	Ph A	110 kV	0 A	11 A	-
I	Line4	Ph A	110 kV	-3 A	3 A	Small capacitive inrush current
I	Line1	Ph A	110 kV	-100 A	100 A	High capacitive inrush current due to cable
I	Line1	Ph B, C	110 kV	-500 A	500 A	High capacitive inrush current due to cable
I	Pet1	Ph N	110 kV	-2.5 A	2.5 A	Longtime value very small
V	Pet1	Ph N	110 kV	-600 V	600 V	Longtime value very small
Φ	Tr1	Ph A, B, C	110 kV	0 Wb	0.5 Wb	Nominal flux: 0.288 Wb
FFT	HTr1	Ph C	220 kV	50 Hz	450 Hz	Only 50 Hz and 450 Hz
FFT	Tr2	Ph A	110 kV	50 Hz	250 Hz	50 Hz, 100 Hz, 150 Hz, 200 Hz, and 250 Hz

6.10 Case 5: Energizing a Larger Network

Set $cf=5$ to multiply the cable-network capacitance by five. The capacitive currents are approximately twice, rather than five times, those of Section 6.6. The larger capacitance lowers the dominant resonance from approximately 400 Hz to approx. 180 Hz.

As can be seen from the low bias voltage and the low Petersen current, the Petersen circuit is not yet optimally tuned. If we look at the AC analysis, we can see that the resonance point is at approximately 45 Hz. You can see this by determining the beat frequency in the transient analysis. So the Petersen circuit's tuning still needs to be adjusted (see `Switching_Networks_AC.asc`). NOTE: At 1250 A, the Petersen current is, of course, much too high and would place too heavy load on the transformer. The transformer current of Transformer 1 starts at approximately 50 A and then fluctuates up and down. This is due to the 180Hz+50Hz voltage, which also fluctuates up and down at the beginning and, consequently, the integral of the voltage which gives the flux (see file `inrush.asc`). The voltage of the 110 kV Phase A starts at 120 kV, while the voltage of the other phases starts at 180 kV till 200 kV. The current through the main transformer in Phase A is approximately 540 A to -170 A, while the current in Phases B and C is approximately 1 kA. These currents are primarily caused by capacitive inrush currents and are due to the now larger capacitive network. The current through the KD ranges from 0 A to 620 A and decreases rapidly. The current in Line 1 is approximately 600 A in Phase A and approximately 1.2 kA in the other two phases, which is much higher than in Case 1. The current in Line 4 is very low, at 1 A to 2 A, since the charging current of an overhead line is very small. The FFT of the current in phase C on the primary side of the main transformer shows a peak at approximately 180 Hz, as already shown in the calculation below. Here, the 180 Hz component is even higher than the 50 Hz component. The maximum flux of the medium-voltage transformers is initially about 600 mWb Weber, which is slightly higher than in Case 1.

For calculation of the dominant frequency of the circuit like in calculation 6.2 the inductances specified on the 220 kV side must be referred to the 110 kV side. With a voltage ratio of 2, impedance and inductance are divided by $2^2 = 4$ when referred from the 220 kV side to the 110 kV side. The source and transformer inductances are $L_{\text{net}} = 0.0077 \text{ H}$ and $L_{\text{Tr}} = 0.154 \text{ H}$. The sum of capacitance is now $5 \cdot 4000 \text{ nF} = 20000 \text{ nF}$.

The transformer inductive values are obtained from `Trafo_YY0_220k_110k_200MVA_Daten.asc`.

Calculation 6.4 – (Dominant cable-network resonance)

$$L_{\text{eq}} = \frac{L_{\text{net}}}{4} + \frac{L_{\text{Tr}}}{4} = \frac{0.0077 \text{ H} + 0.154 \text{ H}}{4} = 0.04 \text{ H}, \quad (6.13)$$

$$C = 20000 \text{ nF}, \quad (6.14)$$

$$f_r = \frac{1}{2\pi\sqrt{L_{\text{eq}}C}} \approx \boxed{178 \text{ Hz}}. \quad (6.15)$$

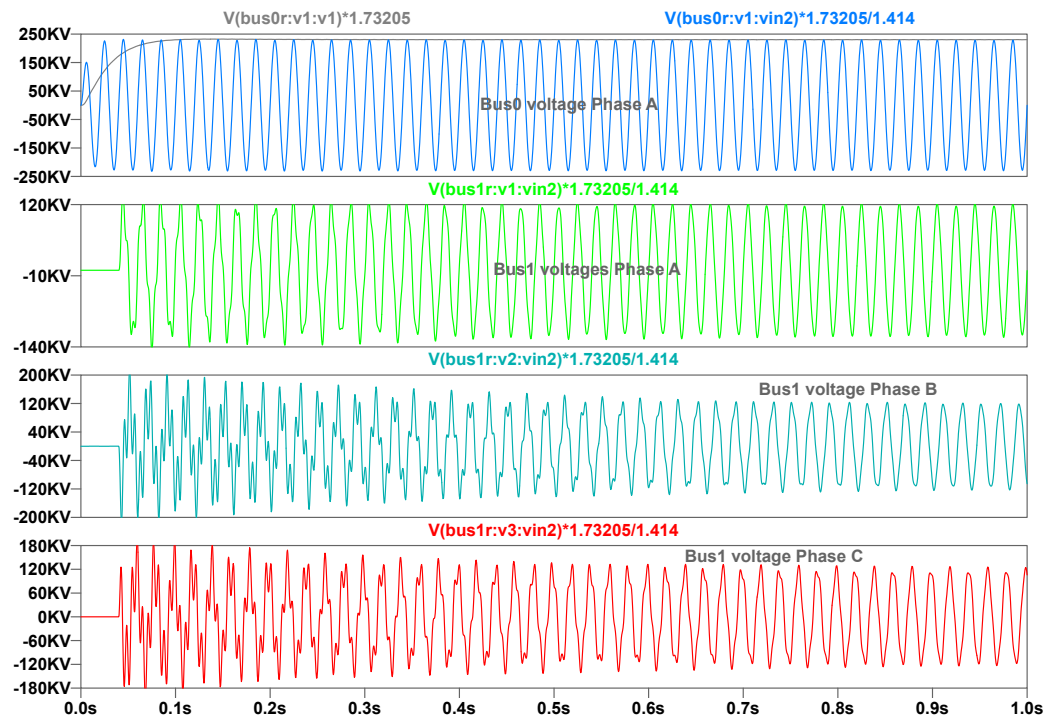


Figure 6.20: Switching on networks voltages - case5

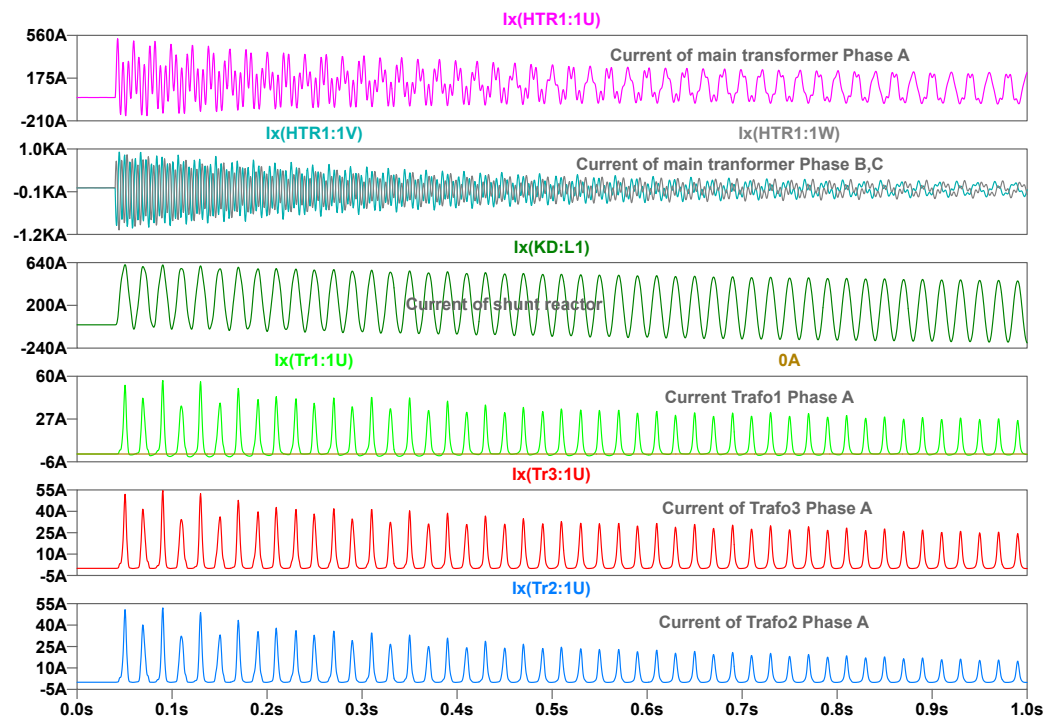


Figure 6.21: Switching on networks currents - case5

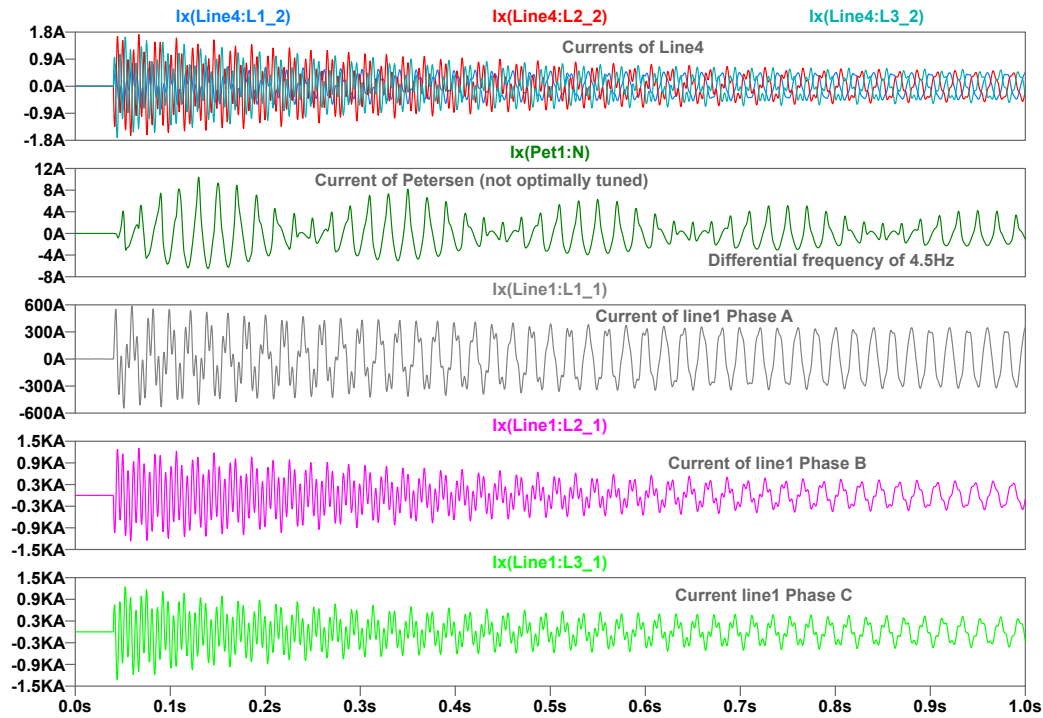


Figure 6.22: Switching on networks currents line1, line4 - case5

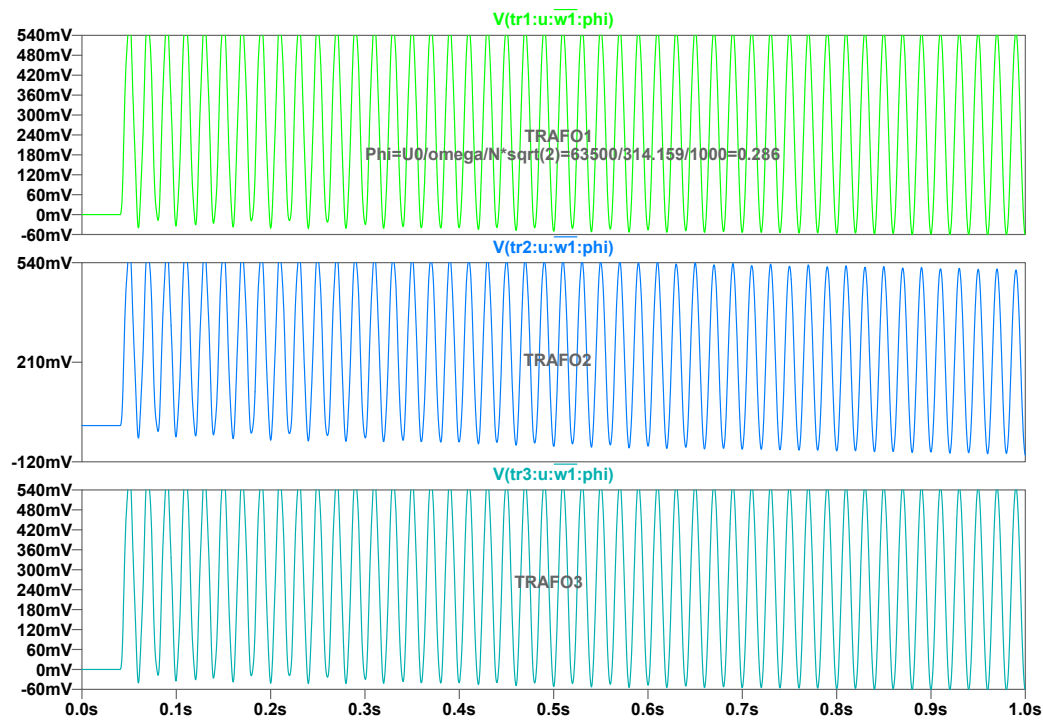


Figure 6.23: Switching on networks fluxes - case5

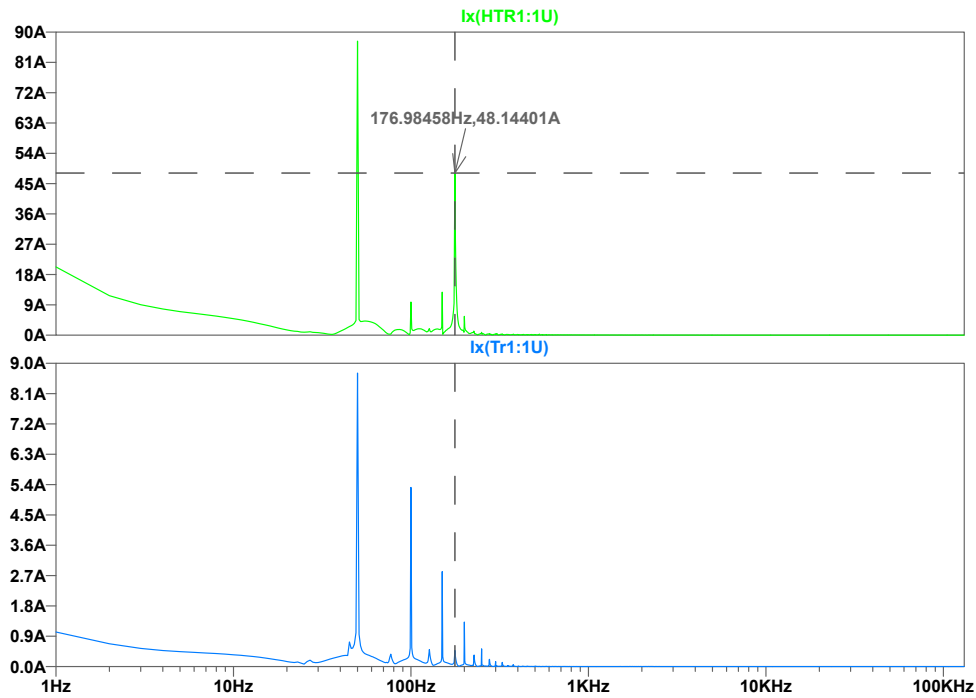


Figure 6.24: Switching on networks FFT - case5

Table 6.5: signal values case5, min-max values are all peak values, but Bus0-Bus1 values are RMS values

Meas.	Grid element	Phase	Voltage level	Min.	Max.	Notes
V	Bus0	Ph A	220 kV	-229 kV	229 kV	-
V	Bus1	Ph A,	110 kV	-140 kV	120 kV	-
V	Bus1	Ph B,C	110 kV	-180 kV	180 kV	-
I	HTr1	Ph A	220 kV	-160 A	530 A	-
I	HTr1	Ph B, C	220 kV	-1 kA	1 kA	-
I	KD1	Ph A	110 kV	0 A	620 A	Steady state: 300 A
I	Tr1	Ph A	110 kV	0 A	54 A	Fluctuating
I	Tr2	Ph A	110 kV	0 A	52 A	Fluctuating
I	Tr3	Ph A	110 kV	0 A	52 A	Fluctuating
I	Line4	Ph A	110 kV	-1.6 A	1.6 A	Small capacitive inrush current
I	Line1	Ph A	110 kV	-530 A	600 A	High capacitive inrush current due to cable
I	Line1	Ph B, C	110 kV	-1.3 kA	1.3 kA	High capacitive inrush current due to cable
I	Pet1	Ph N	110 kV	-6 A	10 A	Fluctuating, Longtime value very small
V	Pet1	Ph N	110 kV	-800 V	600 V	Fluctuating, Longtime value very small
Φ	Tr1	Ph A, B, C	110 kV	0 Wb	0.54 Wb	Nominal flux: 0.288 Wb
FFT	HTr1	Ph C	220 kV	50 Hz	177 Hz	mostly 50 Hz and 177 Hz
FFT	Tr2	Ph A	110 kV	50 Hz	250 Hz	50 Hz, 100 Hz, 150 Hz, 200 Hz, and 250 Hz

6.11 Case 6: Energization with Load

Set $1f=0.5$. The connected load strongly dampens the overvoltages caused by the high-frequency capacitive charging currents, and these oscillations decay rapidly. Transformer inrush currents remain present because they are caused by the transient core flux. Among the direct-switching cases considered so far, this case produces the smallest overvoltages.

The current on the 10.6 kV side of the load is 360 A, which is approximately 36 A on the 110 kV side. The currents on the 110 kV side are a mixture of inrush currents and load currents. It is often claimed in the literature that the load current reduces the inrush of the magnetizing current. This is not really the case. This can be easily demonstrated by simultaneously simulating three identical transformers: a) Set $m = 1$ for Transformer 1 and apply a load to it. This measures the load current on the primary side. b) Set $m = 9$ for Transformer 2 and set the load to 0 c) For Transformer 3, set $m=9$ with the load. Now you can see that when adding the primary currents $I(\text{Transformer 1}) + I(\text{Transformer 2})$, the resulting current is approximately equal to $I(\text{Transformer 3})$. The reduction in inrush current is, if any, only very slight. The transformer inrush is simply “hidden” in the total current but is always present.

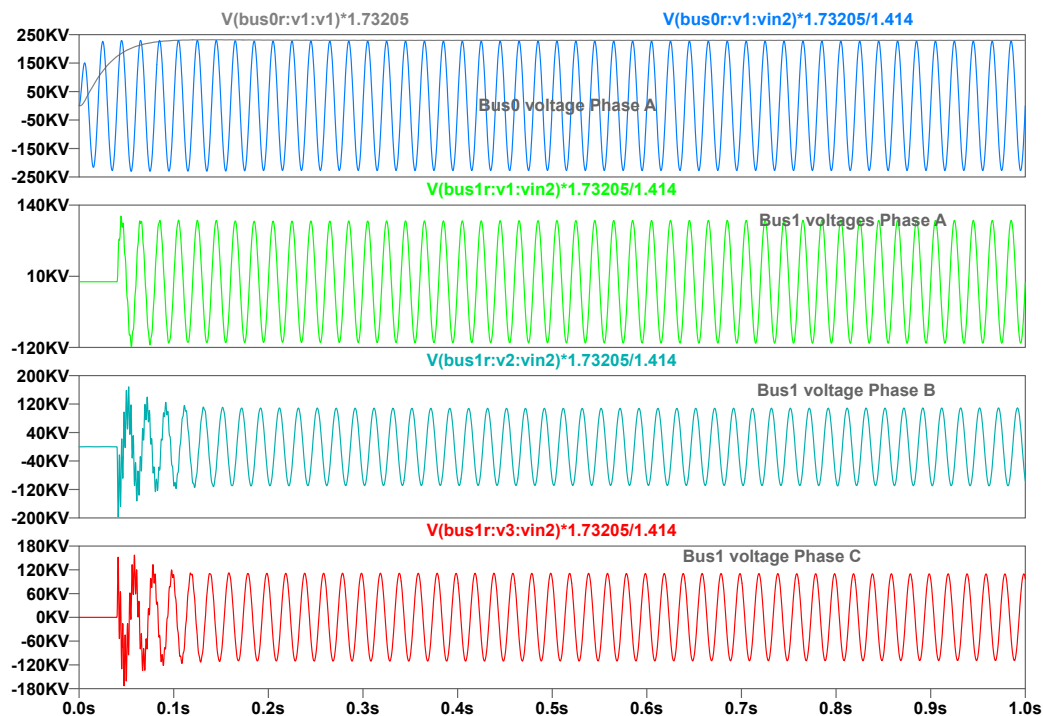


Figure 6.25: Switching on networks voltages - case6

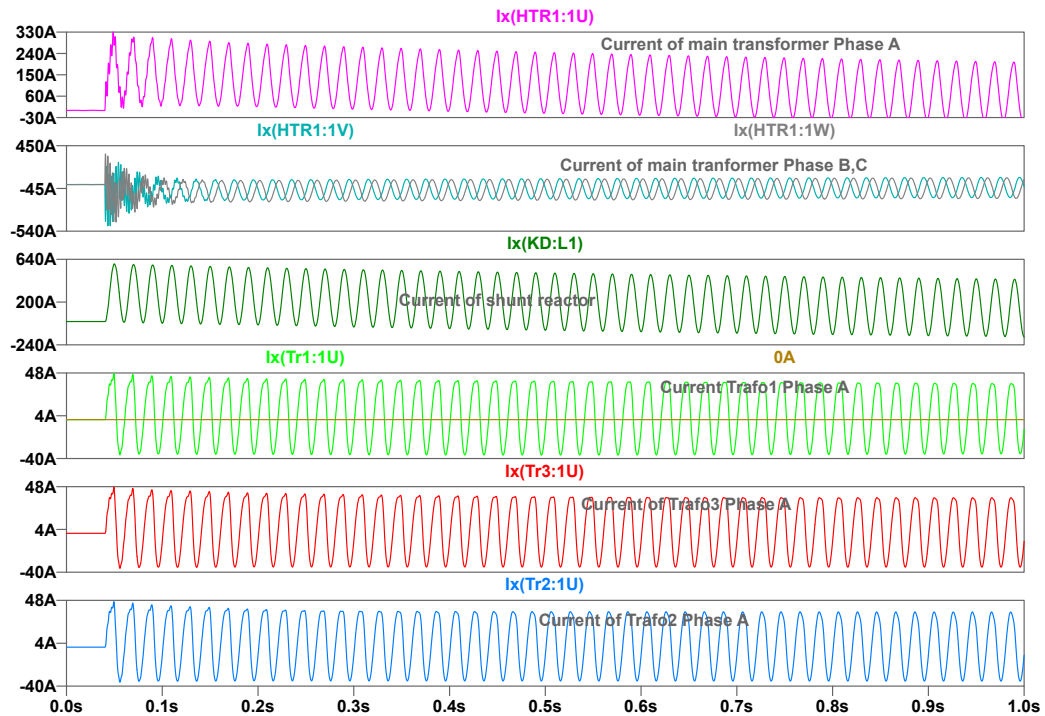


Figure 6.26: Switching on networks currents - case6

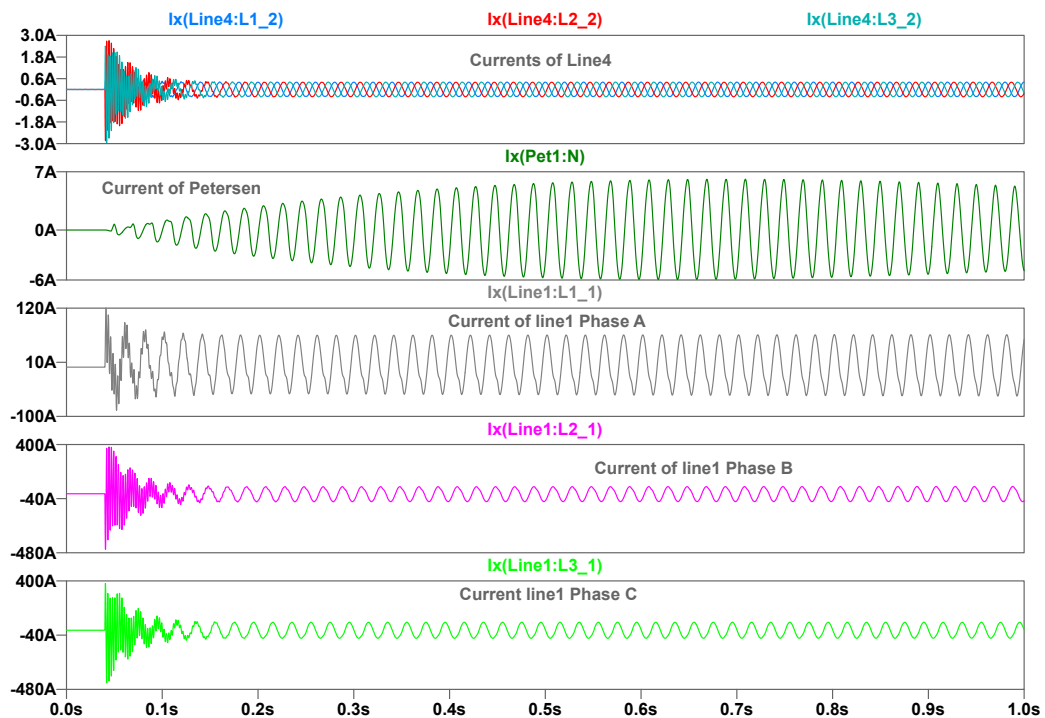


Figure 6.27: Switching on networks currents line1, line4 - case6

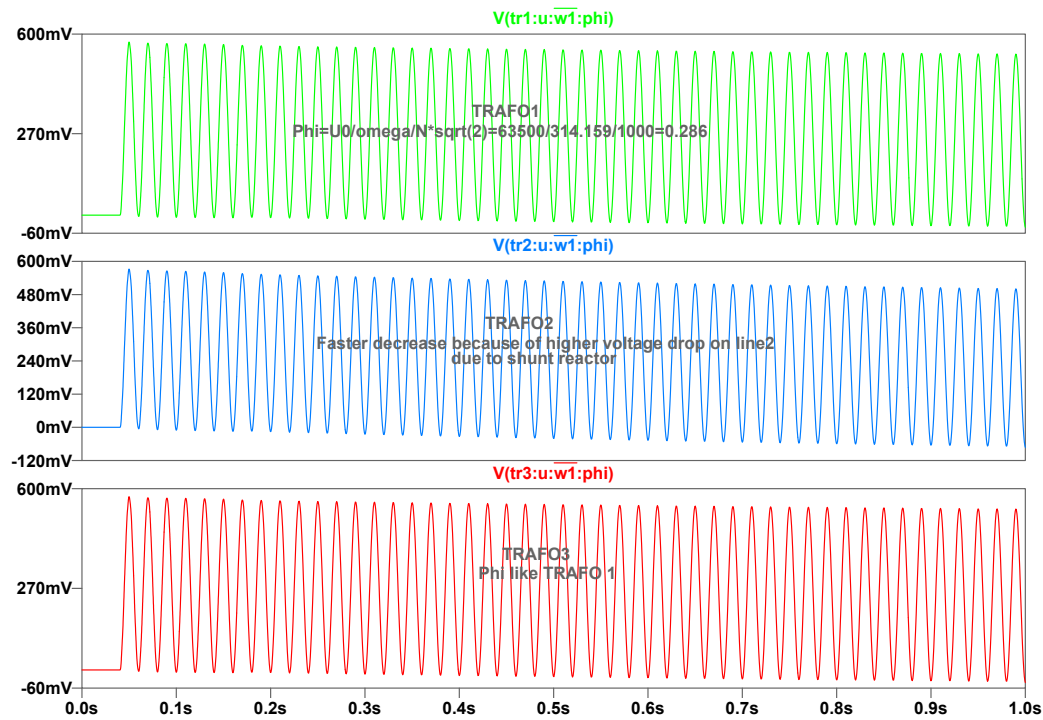


Figure 6.28: Switching on networks fluxes - case6

Table 6.6: signal values case6, min-max values are all peak values, but Bus0-Bus1 values are RMS values

Meas.	Grid element	Phase	Voltage level	Min.	Max.	Notes
V	Bus0	Ph A	220 kV	-229 kV	229 kV	-
V	Bus1	Ph A,	110 kV	-120 kV	120 kV	-
V	Bus1	Ph B,C	110 kV	-170 kV	160 kV	-
I	HTr1	Ph A	220 kV	0 A	330 A	-
I	HTr1	Ph B, C	220 kV	-480 kA	360 kA	-
I	KD1	Ph A	110 kV	0 A	590 A	Steady state: 300 A
I	Tr1	Ph A	110 kV	-36 A	54 A	under load
I	Tr2	Ph A	110 kV	-36 A	50 A	under load
I	Tr3	Ph A	110 kV	-36 A	47 A	under load
I	Line4	Ph A	110 kV	-3 A	2.5 A	Small capacitive inrush current
I	Line1	Ph A	110 kV	-90 A	120 A	High capacitive inrush current due to cable
I	Line1	Ph B, C	110 kV	-480 A	380 A	High capacitive inrush current due to cable
I	Pet1	Ph N	110 kV	-6 A	6 A	Longtime value very small
V	Pet1	Ph N	110 kV	-1.5 kV	1.5 kV	Longtime value very small
Φ	Tr1	Ph A, B, C	110 kV	0 Wb	0.575 Wb	Nominal flux: 0.288 Wb

6.12 Case 7: Skin-Effect Model

Set $\text{skin}=1$. To apply the skin effect in a rough way, we make the simplified assumption that up to 40 ms, only the 50 Hz component determines the resistance, and from 40 ms onward, only the higher frequency of 400 Hz determines the resistance. (Normally, the 50 Hz and 400 Hz components contribute equally.) This allows us to roughly determine the influence of the higher frequency. We see that the additional damping is present but small. Even smaller when split between 50 Hz and 400 Hz. The effect is expected to be more pronounced in smaller networks with higher natural frequencies, particularly when individual lines are energized.

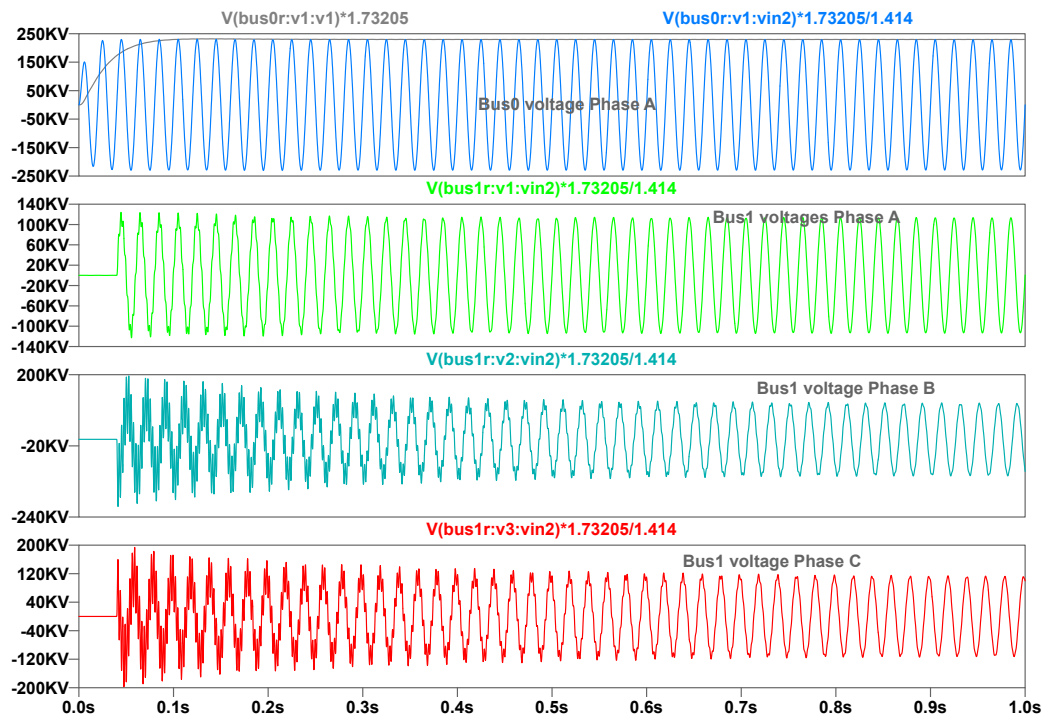


Figure 6.29: Switching on networks voltages - case7

6.13 Case 8: Energization from a Weak Network

Set $\text{weak}=40$ to increase the source impedance (This value models a second transformer in series like a situation after a blackout). The larger source impedance limits the inrush current, although it may simultaneously increase voltage sensitivity elsewhere in the network. Due to the higher voltage volatility, it is not advisable to use a shunt reactor in this circuit. It is better to regulate the voltage by tap-changing the transformer. Try it out and see the long time value of the 110kV voltages. The 110kV steady state voltage is about 106kV with shunt reactor and 120kV without shunt reactor. There is a voltage drop of about 15kV !! To see the difference in one plot add the line `.step param kd list 0 1` to the schematic !!

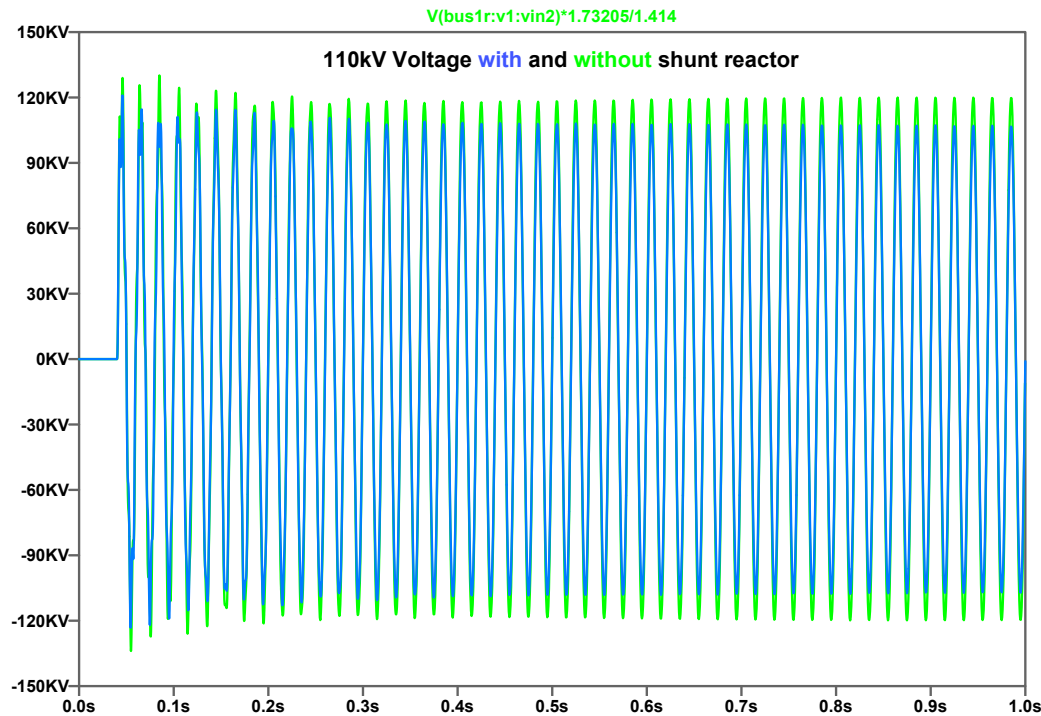


Figure 6.30: Switching on networks voltages - case8

6.14 Case 9: Network Startup by a Voltage Ramp

The simulation file is `Switching_on_networks_Voltagegetrip.asc`. Exchange the model of the voltage source with the corresponding `_AC` model. Then set the parameter of the voltage source to `tpw1` to 400 ms and remove the network switch. Set the parameter `ST` to 10s to disable it. The source voltage then increases gradually from zero to its nominal value within 400ms. NOTE: This is not really done in practice but in simulation to hold the simulation time low.

This procedure produces practically no switching transients: there are no significant overvoltages, high-frequency charging-current oscillations, or transformer magnetizing inrush currents. It is therefore the preferred method for energizing the complete network in this study. Loads should be connected only after the voltage has reached its nominal level. The currents of this network are only the charging currents of the lines and the current of the shunt reactor. The magnetizing currents of the transformers 2 and 3 are under 1A. The current of `Trafo1` is a little bit higher due to the current needed by the Petersen. The currents of `Line1` are all phases the same height. The Petersen current is 7A, the Petersen voltage at 1.7kV (measured at time=100s) and the `Line4` current is about 400mA. The flux of transformer 1, 2 and 3 are of same height and about the nominal flux (a little bit higher since the working voltage is not 110kV). The 110kV voltage is at about 110kV in phase A 113.7kV in Phase B and 112.3kV in Phase C (slightly different because of the starpoint displacement voltage) which is the steadystate value. The FFT shows only the nominal frequency of 50Hz for the whole circuit !!

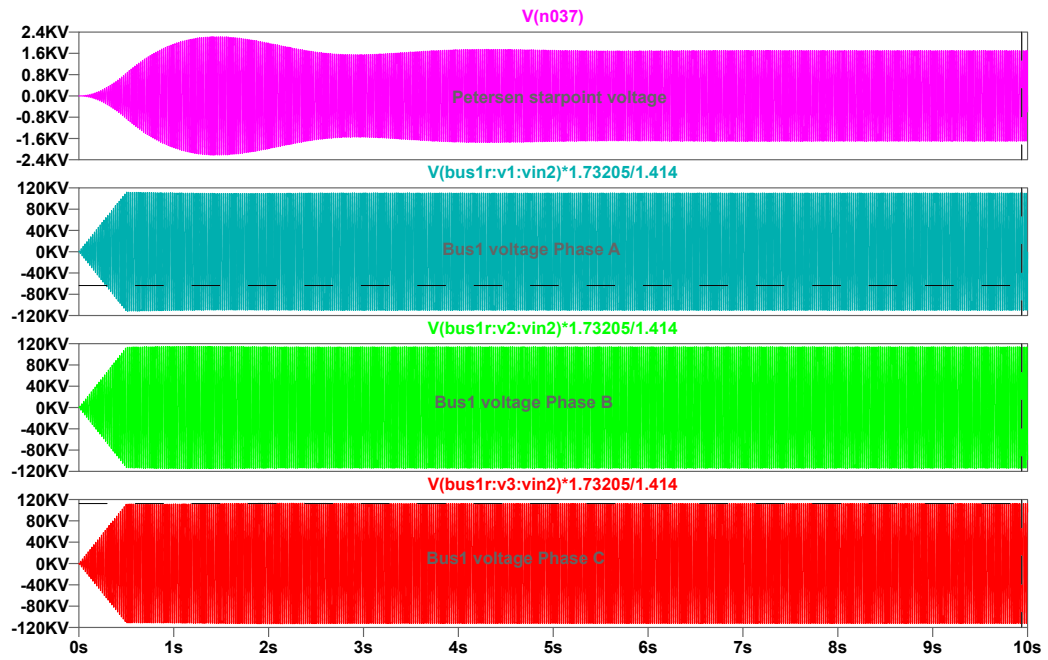


Figure 6.31: Switching on networks voltages - case9

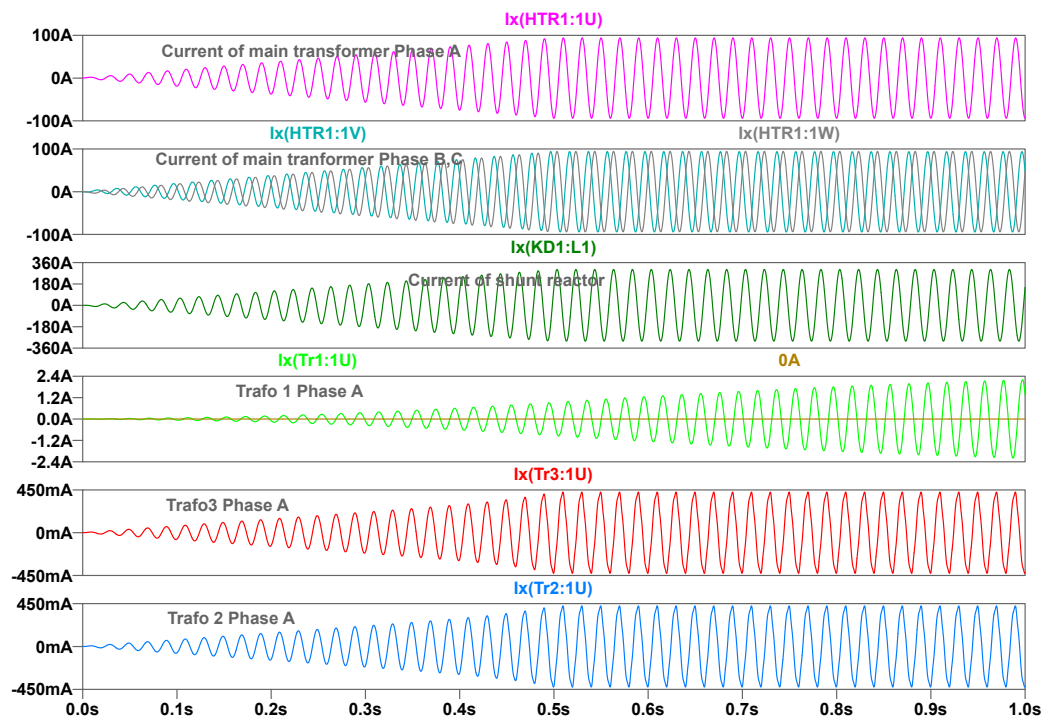


Figure 6.32: Switching on networks currents - case9

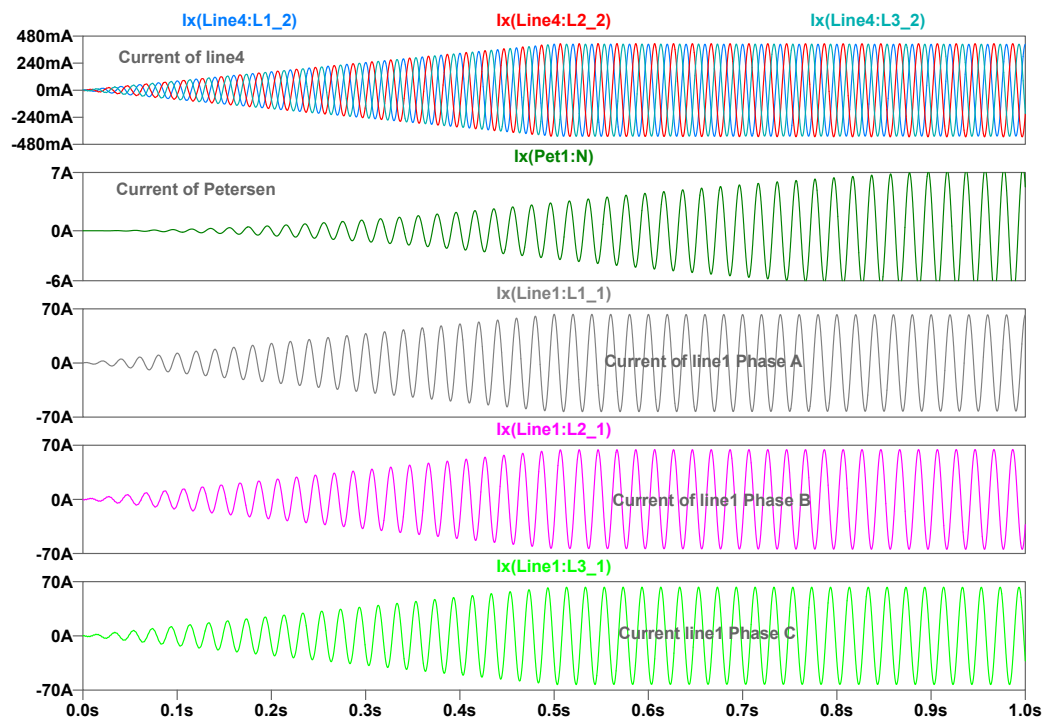


Figure 6.33: Switching on networks currents line1, line4 - case9

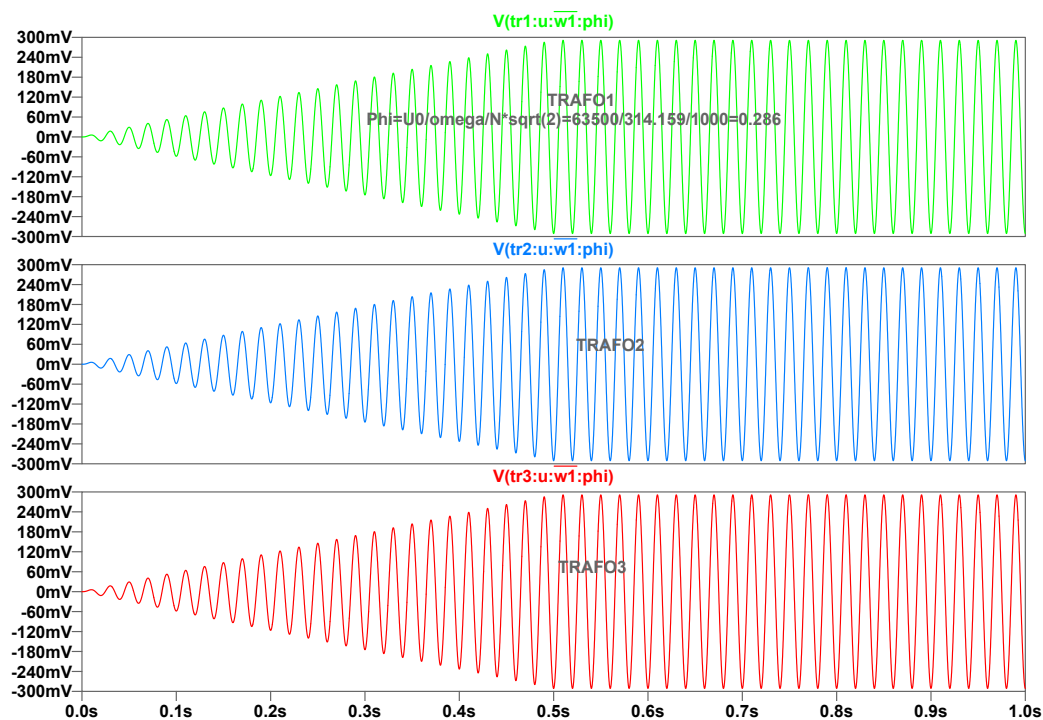


Figure 6.34: Switching on networks fluxes - case9

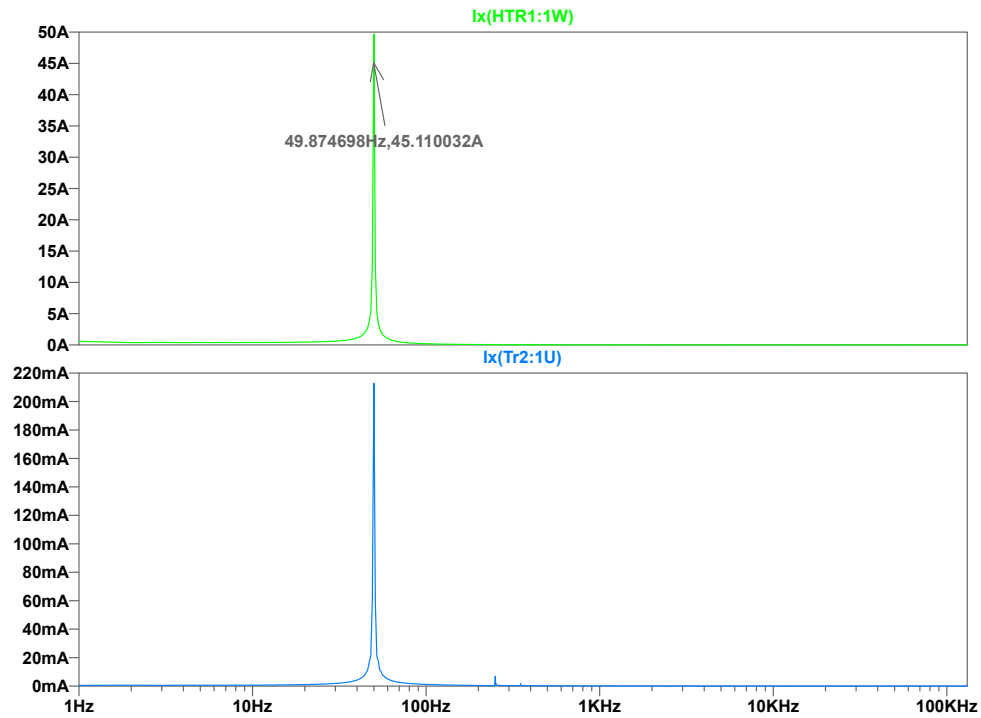


Figure 6.35: Switching on networks FFT - case9

Table 6.7: signal values case9, min-max values are all peak values, but Bus0-Bus1 values are RMS values

Meas.	Grid element	Phase	Voltage level	Min.	Max.	Notes
V	Bus0	Ph A	220 kV	-229 kV	229 kV	Steady state RMS
V	Bus1	Ph A	110 kV	-110 kV	110 kV	Steady state RMS
V	Bus1	Ph B, C	110 kV	-113 kV	113 kV	Steady state RMS
I	HTr1	Ph A	220 kV	-94 A	94 A	Steady state peak
I	HTr1	Ph B, C	220 kV	-94 A	94 A	Steady state peak
I	KD1	Ph A	110 kV	-300 A	300 A	Steady state peak
I	Tr1	Ph A	110 kV	-2 A	2 A	Due to Petersen higher than Tr2,3
I	Tr2	Ph A	110 kV	-450 mA	450 mA	Steady state zero load peak current
I	Tr3	Ph A	110 kV	-450 mA	450 mA	Steady state zero load peak current
I	Line4	Ph A	110 kV	-410 mA	410 mA	Steady state peak
I	Line1	Ph A, B, C	110 kV	-62 A	62 A	Steady state peak
I	Pet1	Ph N	110 kV	-5 A	5 A	Steady state peak
V	Pet1	Ph N	110 kV	-1.4 kV	1.4 kV	Steady state peak
Φ	Tr1	Ph A, B, C	110 kV	0.291 Wb	0.291 Wb	Nominal flux: 0.288 Wb peak
FFT	HTr1	Ph C	220 kV	50 Hz	50 Hz	only 50 Hz nominal frequ.
FFT	Tr2	Ph A	110 kV	50 Hz	50 Hz	50 Hz nominal frequ.

Important 6.1 – (Preferred energization method)

A controlled voltage ramp avoids the abrupt change in applied voltage that excites cable resonances and transformer flux offsets. The ramp time must be long compared with the dominant electrical oscillation periods, and load connection must be delayed until the voltage is established.

Chapter Summary

Energizing an entire cable-dominated network excites both transformer inrush and cable-charging transients. The switching instant determines which phases are dominated by magnetizing current and which by capacitive current. Cable capacitance, referred transformer inductance, tap position, load, and network strength determine the natural frequencies and transient amplitudes. Residual flux can raise transformer currents above rated peak current, while connected loads add effective damping. In this study, a gradual source-voltage ramp is the most effective energization method because it suppresses both cable resonances and transformer inrush.

7 Coupled Lines with Resonance

7.1 General

This chapter investigates two electromagnetically coupled 400 kV overhead lines on a common Danube-type tower. The capacitive reactive power of the two lines is compensated by an inductive choke. We will examine the case where the compensation is ideal—that is, where the inductive reactive power of the choke exactly compensates for the capacitive reactive power of the line. The following cases are simulated (Line 1 is always energized):

- Line 2 is open (lines are untransposed),
- Line 2 is open (lines are transposed),
- Line 2 is initially grounded and then ungrounded,
- Line 2 is initially energized and then switched off,
- Line 2 is initially energized and then switched off without a compensating reactor

7.2 Circuit design

The total line length is approximately 9.75 km. Mutual inductances and capacitances couple the circuits even when one line is disconnected at both ends.

The per-kilometre inductance and capacitance matrices of the coupled line were calculated with ATP and then stored in `line_coupled.lib`. To help the conversion procedure to Ltspice library code the excel file `Lines_and_cables.xlsx` is used.

Each line is almost fully compensated by an inductive shunt-compensation element, `l_batt`. Near-exact compensation creates an important operating condition: if line 1 is energized while line 2 is open at both ends, the mutual coupling can excite a resonance and produce very high voltages on the disconnected line.

7.3 Determining the Compensation Rating

Use `Coupled_lines_resonance_TRAN.asc`. Save a working copy as `test.asc`, remove the compensation elements, and run the transient simulation. Measure the three phase reactive powers with `qmeter_uvw_sgn`. The results are approximately

$$Q_R = -2.02 \text{ Mvar}, \quad Q_S = -2.40 \text{ Mvar}, \quad Q_T = -2.37 \text{ Mvar}. \quad (7.1)$$

The total capacitive reactive power is therefore approximately -6.8 Mvar . A compensation rating of 6 Mvar is selected for each line, leaving the system close to, but not exactly at, resonance.

At 400 kV, the corresponding balanced three-phase current is

Calculation 7.1 – (Current of the 6 Mvar compensation reactor)

$$I_{\text{rms}} = \frac{Q}{\sqrt{3}U_{\text{LL}}} = \frac{6 \text{ Mvar}}{\sqrt{3} \cdot 400 \text{ kV}} \approx 8.66 \text{ A}, \quad (7.2)$$

$$\hat{I} = \sqrt{2} I_{\text{rms}} \approx \boxed{12.2 \text{ A}}. \quad (7.3)$$

7.4 Line 1 Energized and Line 2 Open: Untransposed Lines

The transient model is `Coupled_lines_resonance_TRAN.asc`. Line 1 is supplied by a source with an exponential voltage startup, while line 2 remains open at both ends. The open-line voltages exhibit a slow beat and approach their final values after approximately 2 s.

Phase R of line 2 has the highest voltage, with transient peaks near 500 kV, corresponding to approximately 350 kV RMS. The other two phase peaks remain below 300 kV. For comparison, the normal phase-voltage peak of the energized 400 kV line is

$$\hat{U}_{\text{ph}} = \sqrt{2} \frac{U_{\text{LL}}}{\sqrt{3}} = \sqrt{2} \frac{400 \text{ kV}}{\sqrt{3}} \approx 326.6 \text{ kV peak}. \quad (7.4)$$

The settled phase-R peak on line 2 is approximately 350 kV, exceeding the normal phase peak on line 1 with 327 kV. The slow envelope is caused by the small difference between the 50 Hz source frequency and a nearby natural frequency formed by the line capacitances and the compensating `l_batt` reactors.

The reactor-current peaks on line 1 are approximately 12 A in all three phases, consistent with calculation ?? 7.1. On line 2, the peak currents are approximately 13.3 A, 6 A, and 7 A in phases R, S, and T, respectively. The source currents are close to zero because the line charging current is almost compensated.

The untransposed line has strongly unequal mutual capacitances and inductances. Consequently, the phase magnitudes and phase angles on open line 2 are highly asymmetric, and the sum of its three phase-to-earth voltages is not zero - 46kV difference

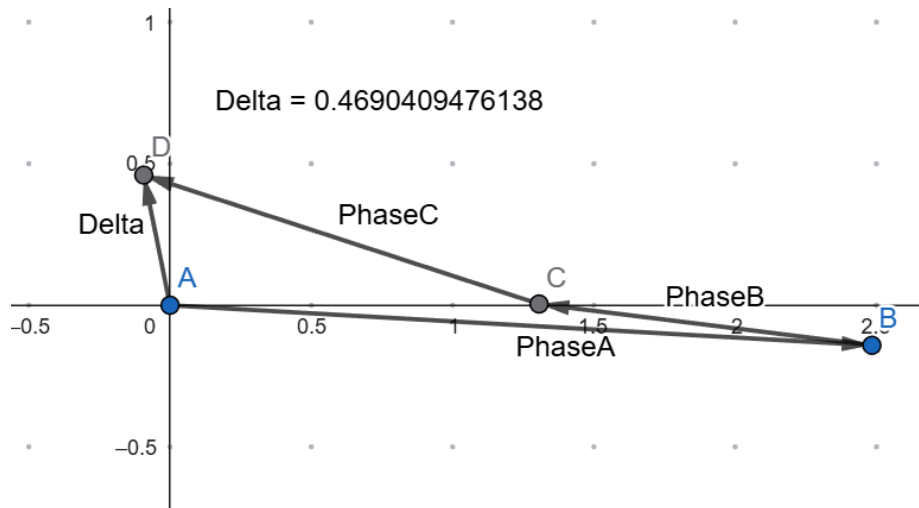


Figure 7.1: Coupled lines resonance - Sum of voltages not zero - scale*1e5

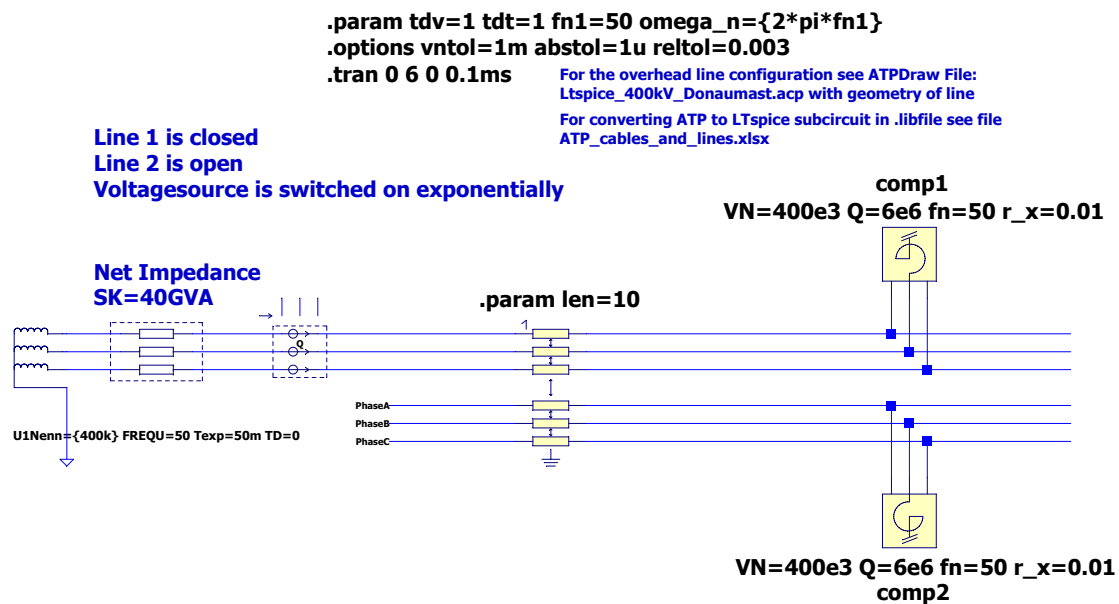


Figure 7.2: Coupled lines resonance schematic - Lines2 is open untransposed TRAN analysis

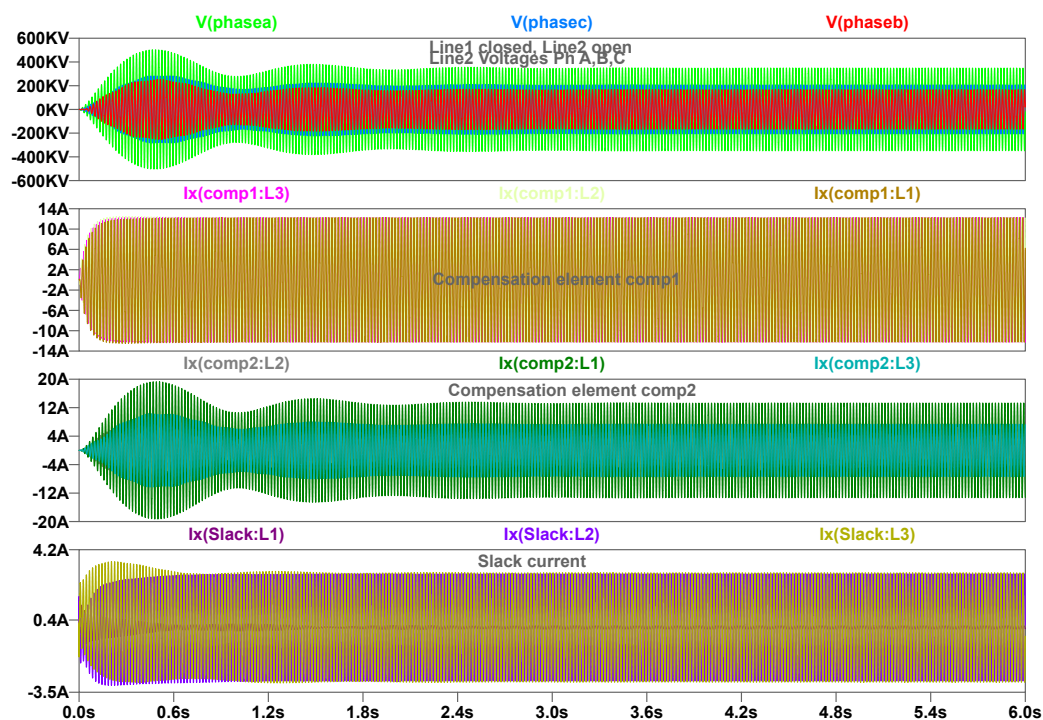


Figure 7.3: Coupled lines resonance TRAN - Lines2 is open untransposed TRAN analysis

7.5 AC Analysis of the Untransposed Open Line

The frequency-domain model is `Coupled_lines_resonance_AC.asc`. Set the vertical scale to linear by right-clicking the left axis. The principal resonance of the open-line voltage lies near 49 Hz. At 50 Hz, the phase-R voltage is approximately 250 kV RMS, compared with the normal phase voltage of approximately 231 kV RMS. This corresponds to the settled transient value of approximately 353 kV peak.

A second resonance occurs near 44 Hz. At the main resonant peak near 49 Hz, the phase-R voltage can approach approximately 1 MV peak. This demonstrates the sensitivity of the open coupled line to small changes in shunt-reactor tuning.

Important 7.1 – (Near-resonant open-line overvoltage)

An open line is not necessarily de-energized when it shares a tower with an energized line. Mutual capacitances and inductances can sustain a substantial voltage, and near-resonant shunt compensation can amplify it far above the normal phase voltage.

7.5.1 Exercises

1. Save the model as `test.asc` and increase the `l_batt` rating until the resonant peak lies at 50 Hz. Observe the resulting voltage amplification.
2. Reduce the reactor rating to 5 Mvar. Compare the resonant frequency and peak magnitude with the original case.
3. Change the reactor parameter `r_x`, which represents its ohmic component. Observe how increasing damping broadens and lowers the resonant peak.

7.6 Line 1 Energized and Line 2 Open: Transposed Lines

The transient file is `Coupled_lines_resonance_TRAN_transposed.asc`. Transposition makes the phase coupling approximately symmetrical. The three open-line voltages therefore have equal magnitudes, and the relevant resonance moves farther away from the power frequency.

The initial open-line peaks are approximately 100 kV and decay to about 70 kV after 2 s. This is a substantially more favourable operating condition than the untransposed case in Section 7.4.

Important 7.2 – (Exercise)

Save the model as `test.asc`, remove the `l_batt` elements from both lines, and compare the phase currents and reactive powers of lines 1 and 2. The transposed model should produce nearly symmetrical phase results.

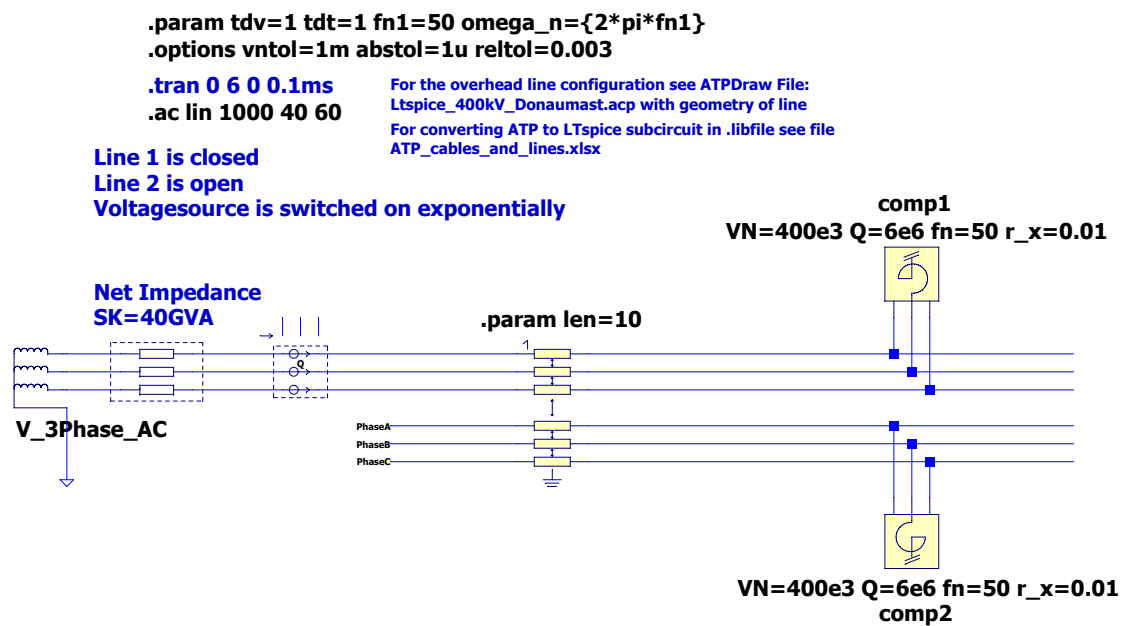


Figure 7.4: Coupled lines resonance schematic - Lines2 is open untransposed AC analysis

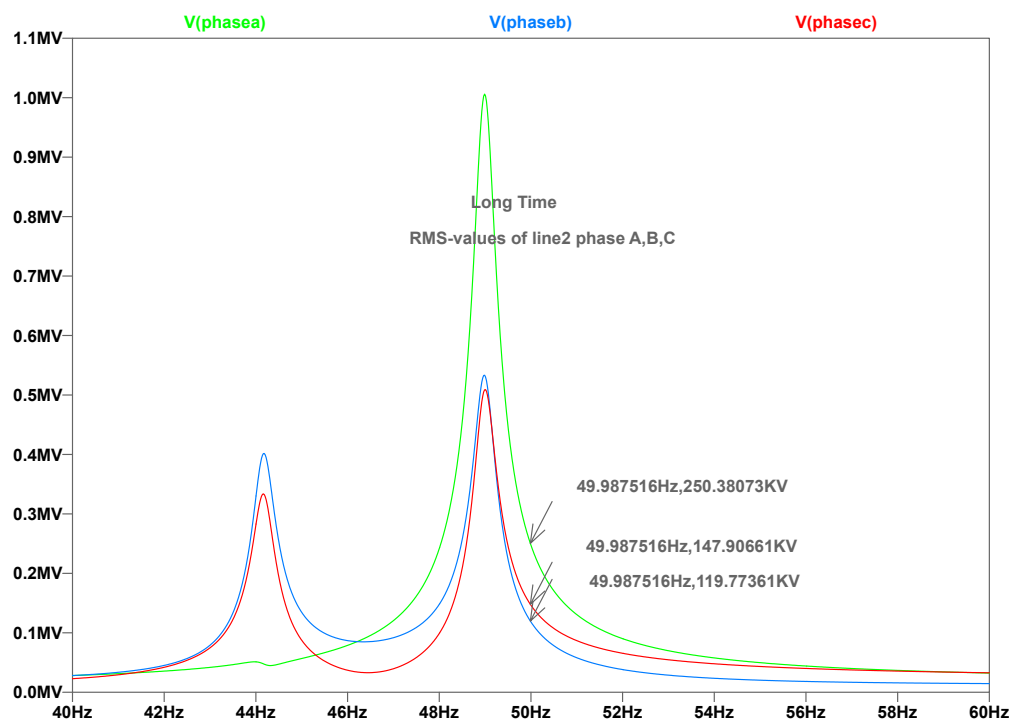


Figure 7.5: Coupled lines resonance AC - Lines2 is open untransposed

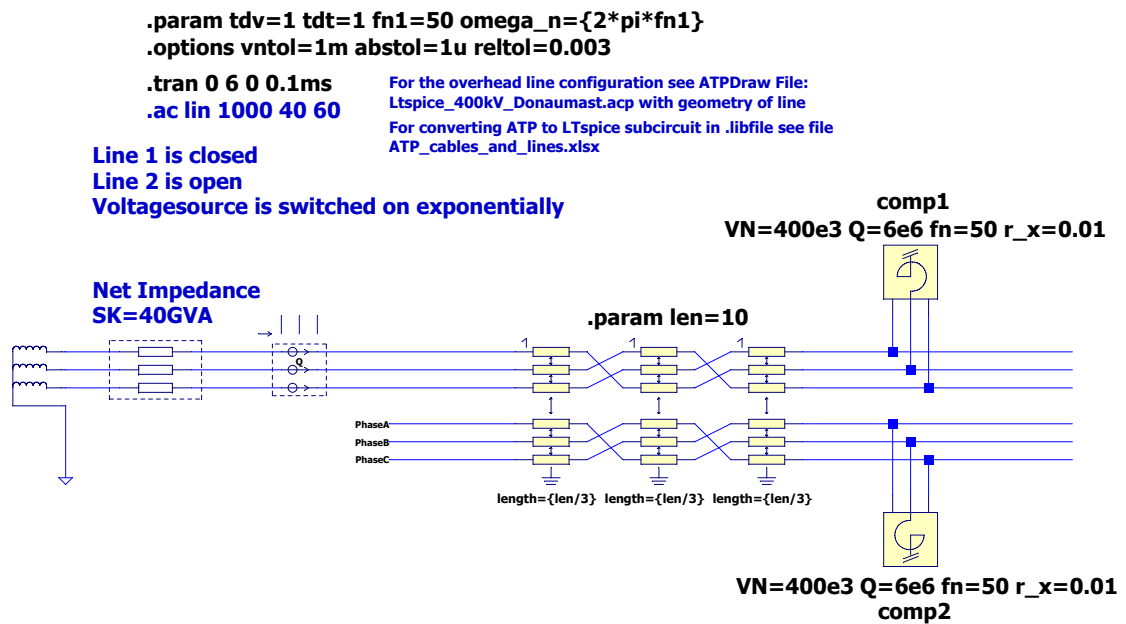


Figure 7.6: Coupled lines resonance schematic - Lines2 is open transposed - TRAN analysis

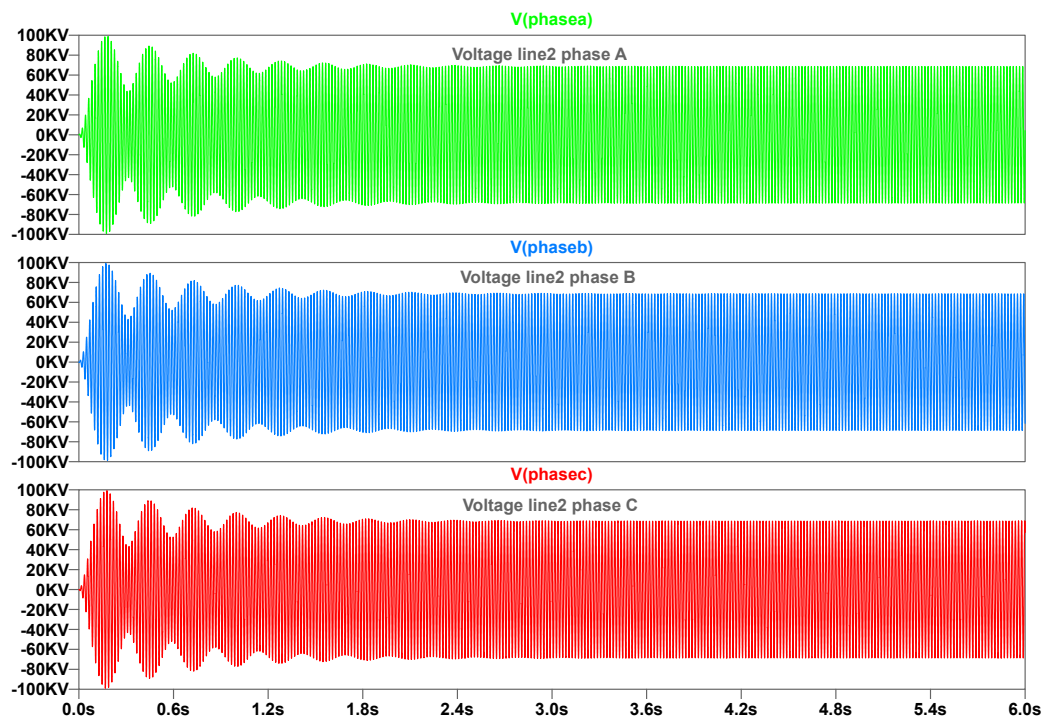


Figure 7.7: Coupled lines resonance TRAN - Lines2 is open transposed

7.7 AC Analysis of the Transposed Open Line

Use `Coupled_lines_resonance_AC_transposed.asc`. The principal resonant peak shifts to approximately 46.3 Hz. The additional lower-frequency maxima visible in the untransposed model disappear because the phase coupling has been symmetrized. At 50 Hz, all three phase voltages are approximately 49 kV RMS, or 70 kV peak, in agreement with the final values of the transient simulation.

7.8 Line 2 Initially Grounded and Then Ungrounded

The simulation file is `Coupled_lines_resonance_TRAN2.asc`. Line 1 remains energized, while line 2 is initially grounded and subsequently opened. The final response is similar to the permanently open case in Section 7.4. A second beat is particularly visible in phases S and T; it is associated with the second resonance near 44 Hz identified by the AC analysis.

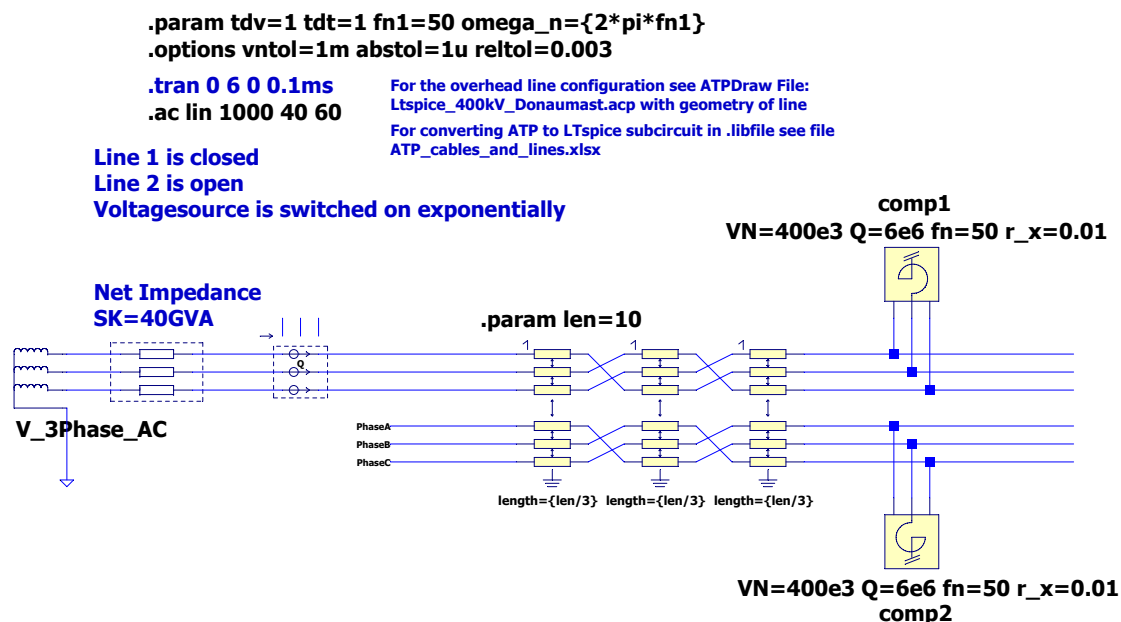


Figure 7.8: Coupled lines resonance schematic Lines2 is open transposed

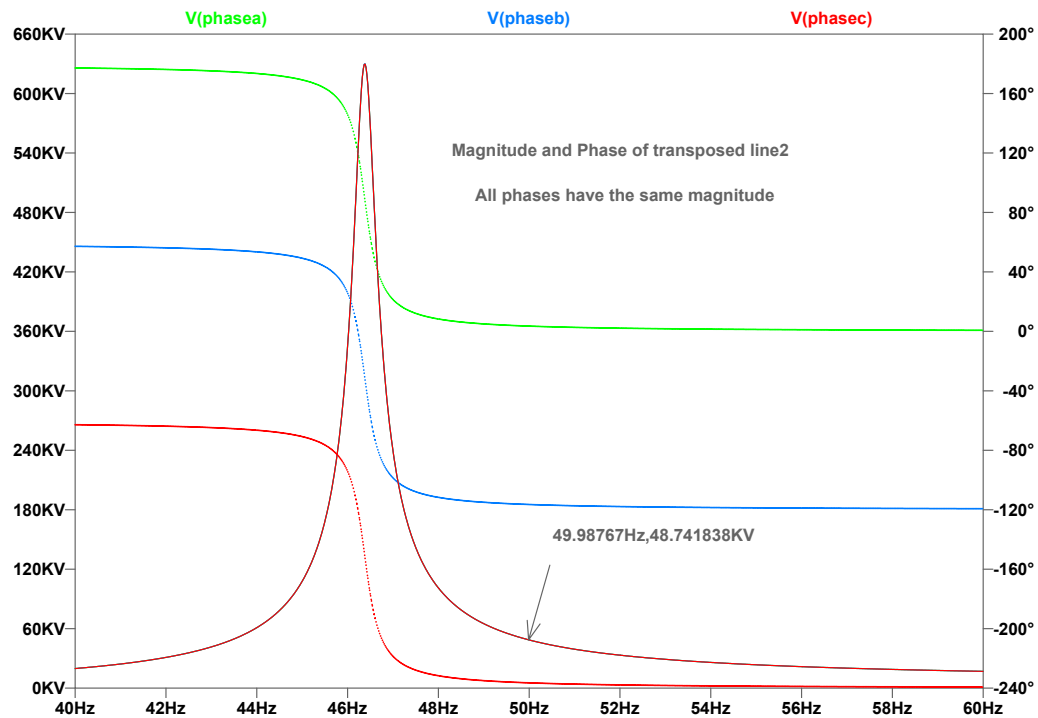


Figure 7.9: Coupled lines resonance AC - Lines2 is open transposed

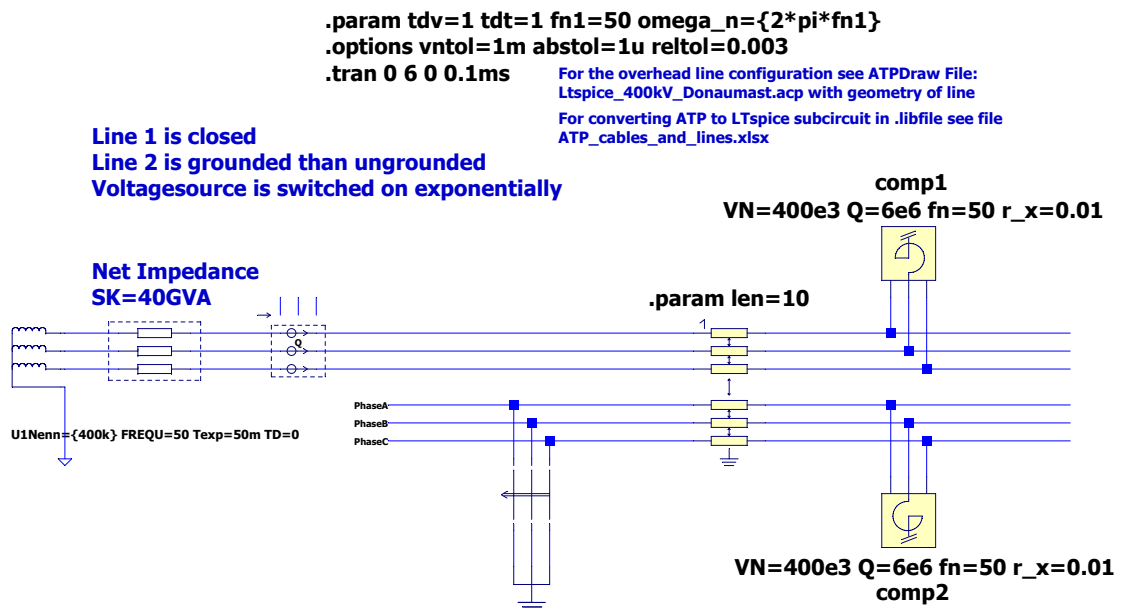


Figure 7.10: Coupled lines resonance TRAN line2 grounded than ungrounded

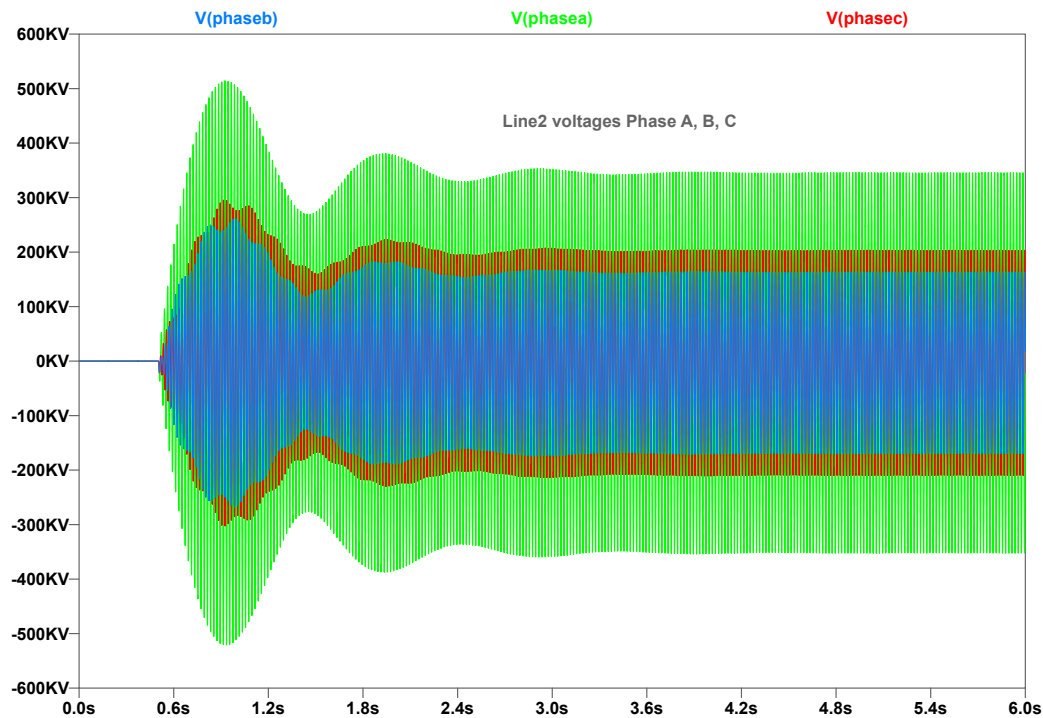


Figure 7.11: Coupled lines resonance TRAN line2 grounded than ungrounded

7.9 Line 2 Energized and Subsequently Switched Off

Use `Coupled_lines_resonance_TRAN3.asc`. Line 2 is disconnected at 500 ms. Immediately after opening, its voltage swings to approximately -430 kV. Phase R shows a long-period beat, while phases S and T show a shorter-period envelope associated with the 44 Hz resonance.

Select the phase-T voltage and draw a zoom window between two adjacent envelope maxima. The LTspice status line indicates approximately 5.7 Hz. This is close to the difference between the source frequency and the second natural frequency:

$$f_{\text{beat}} \approx |f_s - f_{r,2}| \approx |50 \text{ Hz} - 44 \text{ Hz}| \approx 6 \text{ Hz}. \quad (7.5)$$

Important 7.3 – (Exercise)

Save the model as `test.asc`, change the opening time to 0.510 s, and compare the phase-voltage peaks. The trapped initial conditions at the switching instant strongly influence the subsequent free oscillation.

7.10 Line 2 Switched Off Without a Compensation Reactor

The file is `Coupled_lines_resonance_TRAN4.asc`. After line 2 is switched off, its induced phase-voltage peaks are only approximately 20 kV to 30 kV. Without the `l_batt` element, the near-power-frequency resonance is absent. For a direct steady-state study, the switch may be deleted so that line 2 is open from the beginning.

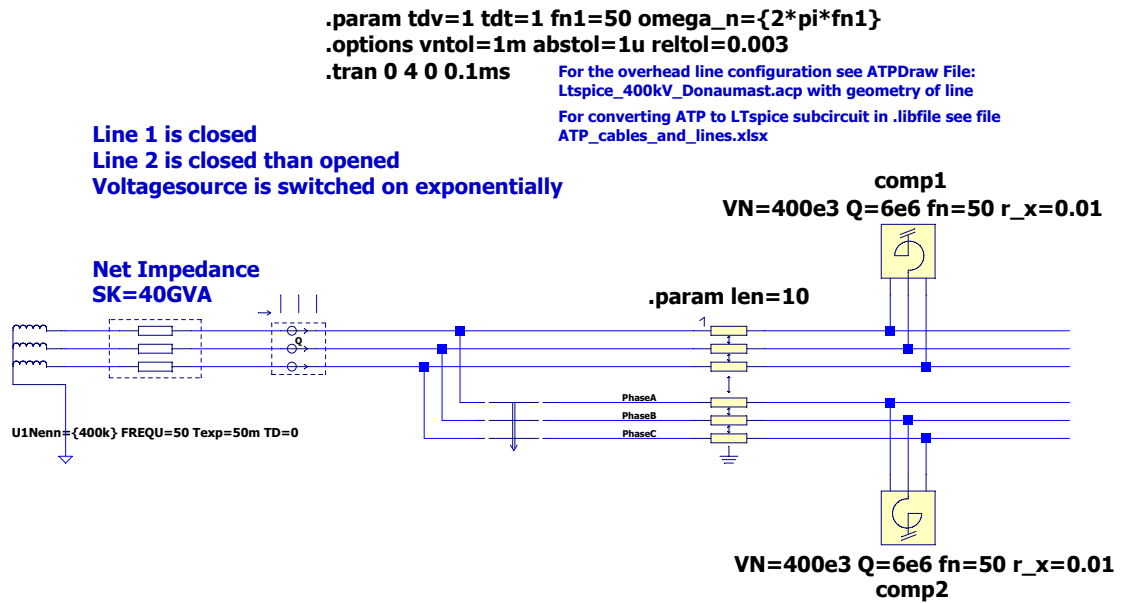


Figure 7.12: Coupled lines resonance TRAN line2 switched off schematic

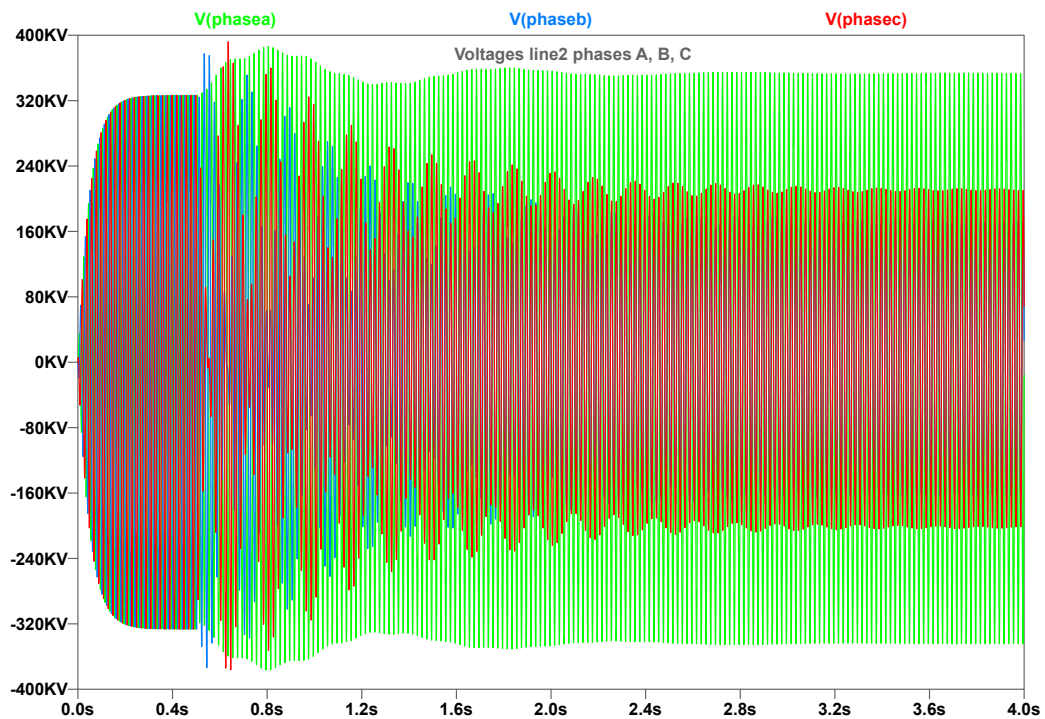


Figure 7.13: Coupled lines resonance TRAN line2 switched off

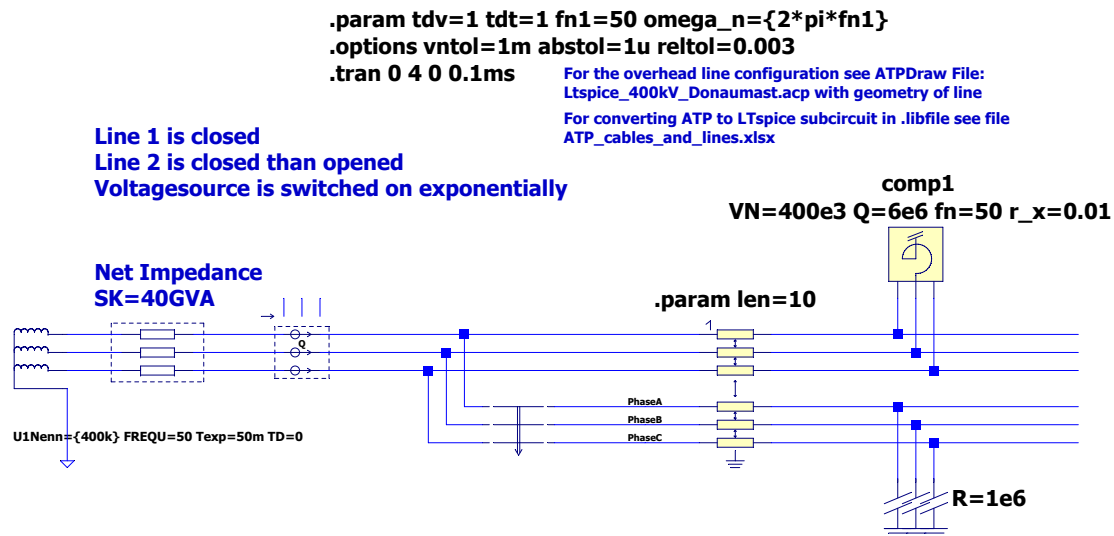


Figure 7.14: Coupled lines resonance TRAN line2 switched off without shunt reactor schematic

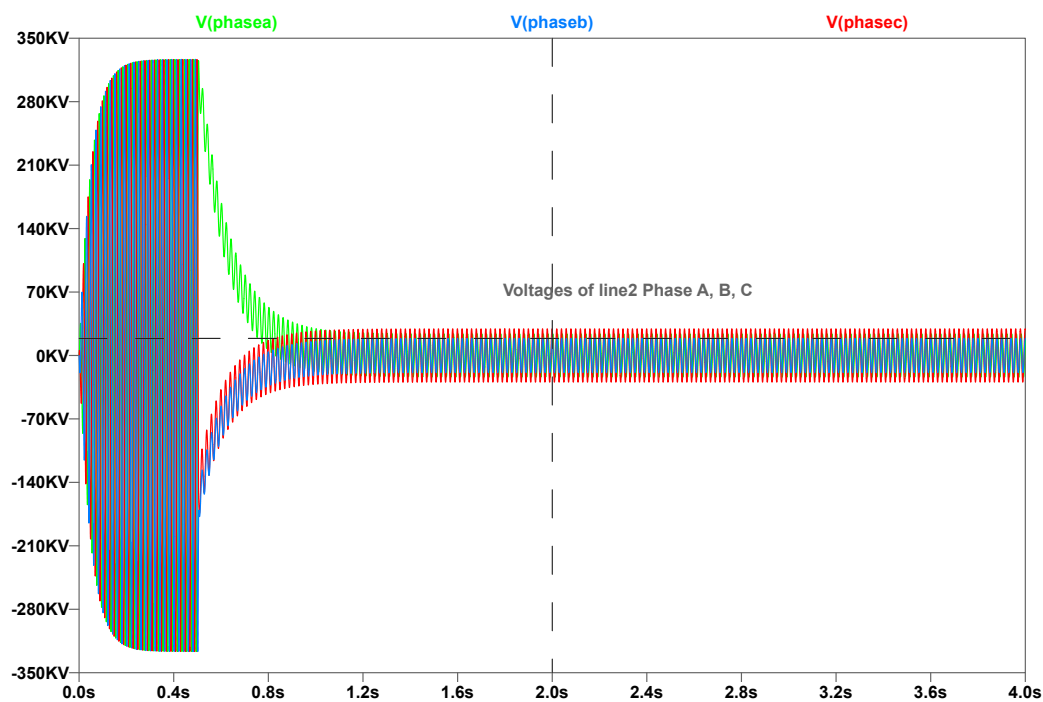


Figure 7.15: Coupled lines resonance TRAN line2 switched off without shunt reactor

7.11 Stored Energy on the Open Line

Use `Coupled_lines_resonance_TRAN5.asc`. Line 1 is initially energized and then disconnected; line 2 is subsequently grounded. To measure the dissipated energy, hold ALT and click the grounding element, then hold CTRL and click the generated power trace. LTspice integrates the power and displays the corresponding energy. NOTE: In this case, the energy should be measured from 1 s to 2 s (zoom to 1-2s) This is the range where the energy still drops significantly after switching off the line. After two seconds, only the energy transfer from Line 1 to Line 2 via capacitive coupling between both lines remains. This (small) energy should not be included in the measurement.

The energy released from line 2 is approximately 2.2 kJ. The stored energy is therefore comparatively small. With a grounding resistance of 100 Ω , the open-line voltage collapses almost immediately. It also collapses with 10 k Ω , showing that the mutual coupling path to line 1 is relatively high-impedance at 50 Hz.

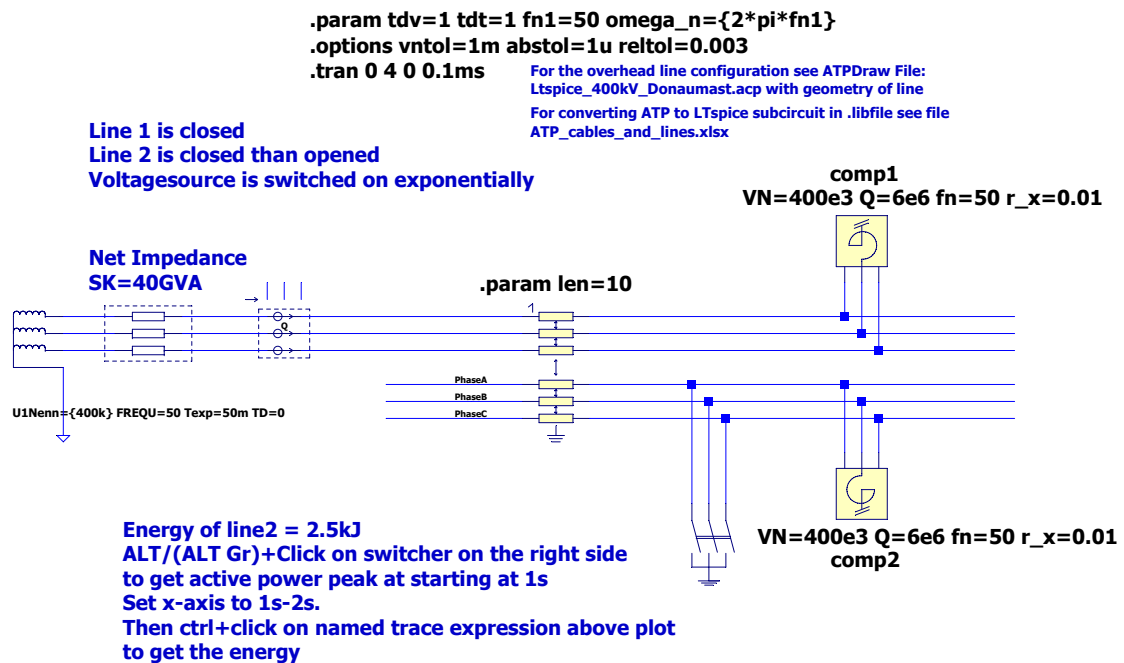


Figure 7.16: Coupled lines resonance TRAN line2 stored energy schematic

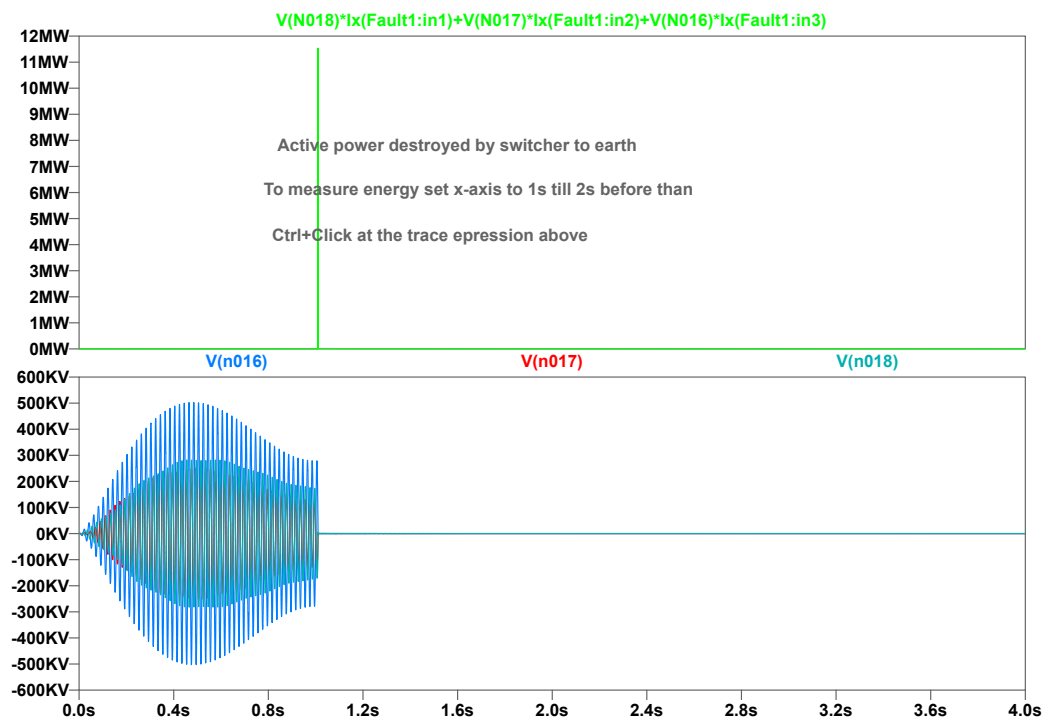


Figure 7.17: Coupled lines resonance TRAN line2 stored energy

Chapter Summary

Mutual inductive and capacitive coupling can impose substantial voltages on an open overhead-line circuit. Near-exact shunt compensation may place a natural frequency close to 50 Hz and amplify the open-line voltage to a dangerous level. Phase transposition symmetrizes the coupling and, in this example, shifts the resonance away from the operating frequency. Removing the compensation reactor eliminates the near-power-frequency resonance, while its loss parameter controls damping.

Synchronous Generator Model

Formula sheet for the $xy0$ machine model

Notation. Subscripts S , E , DX , and DY denote the stator, excitation winding, and the damper windings on the x - and y -axes. The dot denotes a time derivative, e.g. $\dot{\psi} = d\psi/dt$. The symbols x and y correspond to the rotating machine axes used in the source model.

Clarke transformation: three-phase to $xy0$

$$u_0 = \frac{u_1 + u_2 + u_3}{3} = R_0 i_0 + L_0 \dot{i}_0, \quad (\text{A.1})$$

$$u_{SXS} = \frac{2u_1 - (u_2 + u_3)}{3}, \quad (\text{A.2})$$

$$u_{SYS} = \frac{u_2 - u_3}{\sqrt{3}}. \quad (\text{A.3})$$

The stationary components are rotated through the electrical angle α :

$$u_{SX} = u_{SXS} \cos \alpha + u_{SYS} \sin \alpha, \quad (\text{A.4})$$

$$u_{SY} = u_{SYS} \cos \alpha - u_{SXS} \sin \alpha. \quad (\text{A.5})$$

Electrical equations in the rotating reference frame

$$u_{SX} = R_S i_{SX} + \dot{\psi}_{SX} - p\omega \psi_{SY}, \quad (\text{A.6})$$

$$g u_E = g^2 \frac{2}{3} R_E i_E + \dot{\psi}_E, \quad (\text{A.7})$$

$$0 = R_{DX} i_{DX} + \dot{\psi}_{DX}, \quad (\text{A.8})$$

$$u_{SY} = R_S i_{SY} + \dot{\psi}_{SY} + p\omega \psi_{SX}, \quad (\text{A.9})$$

$$0 = R_{DY} i_{DY} + \dot{\psi}_{DY}. \quad (\text{A.10})$$

Flux linkages and current components

The common magnetizing flux linkages are

$$\psi_{hX} = \psi_{SX} - L_S i_{SX} = \psi_{DX} - L_{DX} i_{DX} = \psi_E - L_E \frac{i_E}{g}, \quad (\text{A.11})$$

$$\psi_{hY} = \psi_{SY} - L_S i_{SY} = \psi_{DY} - L_{DY} i_{DY}. \quad (\text{A.12})$$

The associated magnetizing currents are

$$i_{\mu X} = f(\psi_{hX}) = i_{SX} + i_{DX} + \frac{i_E}{g}, \quad (\text{A.13})$$

$$i_{\mu Y} = f(\psi_{hY}) = i_{SY} + i_{DY}. \quad (\text{A.14})$$

For the nonlinear magnetization characteristic shown in the source model,

$$i_{\mu}(\psi) = i_{\mu N} \left[0.9 \frac{\psi}{\psi_N} + 0.1 \left(\frac{\psi}{\psi_N} \right)^7 \right]. \quad (\text{A.15})$$

Mechanical equations

$$M = M_{RBG} - M_i, \quad (\text{A.16})$$

$$M_i = \frac{3}{2} p (i_{SY} \psi_{hX} - i_{SX} \psi_{hY}), \quad (\text{A.17})$$

$$\alpha = p \int \omega \, dt, \quad (\text{A.18})$$

$$M_{RBG} = M_{\text{Reibung}} \, \text{sign}(n). \quad (\text{A.19})$$

Here, p is the number of pole pairs and n is the mechanical speed.

Inverse transformation: $xy0$ to three-phase

First rotate from the machine frame back to stationary coordinates:

$$i_{SXS} = i_{SX} \cos \alpha - i_{SY} \sin \alpha, \quad (\text{A.20})$$

$$i_{SYS} = i_{SX} \sin \alpha + i_{SY} \cos \alpha. \quad (\text{A.21})$$

Then recover the phase currents:

$$i_1 = i_{SXS} + i_0, \quad (\text{A.22})$$

$$i_2 = \frac{-i_{SXS} + \sqrt{3} i_{SYS}}{2} + i_0, \quad (\text{A.23})$$

$$i_3 = \frac{-i_{SXS} - \sqrt{3} i_{SYS}}{2} + i_0. \quad (\text{A.24})$$

Default model simplifications (if not otherwise supported by the parameter line):

$$\frac{i_E}{g} = i'_E, \quad L_E = L_S, \quad L_0 = L_S, \quad L_{DX} = L_S, \quad L_{DY} = L_S,$$

$$R_0 = R_S, \quad R_{DX} = R_D, \quad R_{DY} = R_D.$$

Constant machine parameters

The rated input data used for the 400 MW synchronous generator are

$$U_{N,\text{verkettet}} = 20 \text{ kV}, \quad I_N = 14.434 \text{ kA}, \quad P_{EL} = 400 \text{ MW}, \quad (\text{A.25})$$

$$f_N = 50 \text{ Hz}, \quad K_C = 0.5, \quad p = 2, \quad (\text{A.26})$$

$$U_{E0} = 600 \text{ V}, \quad I_{E0} = 2000 \text{ A}, \quad \text{Streuung} = 0.05, \quad (\text{A.27})$$

$$r_{cu} = 0.001, \quad r_{bg} = 0.001, \quad \text{Schenkelpolfaktor} = 1, \quad (\text{A.28})$$

$$\text{Daempferfaktor} = 1. \quad (\text{A.29})$$

The apparent power and power factor obtained from the rated voltage and current are

$$S_N = \sqrt{3} U_{N,\text{verkettet}} I_N \quad (\text{A.30})$$

$$= \sqrt{3} \cdot 20 \text{ kV} \cdot 14.434 \text{ kA} = 500.008 \text{ MV A} \approx 500 \text{ MV A}, \quad (\text{A.31})$$

$$\cos \varphi_N = \frac{P_{EL}}{S_N} = \frac{400 \text{ MW}}{500.008 \text{ MV A}} = 0.799987 \approx 0.8. \quad (\text{A.32})$$

The constant machine parameters are calculated from

$$U_N = \frac{U_{N,\text{verkettet}}}{\sqrt{3}}, \quad Z_N = \frac{U_N}{I_N}, \quad (\text{A.33})$$

$$\omega_{EL} = 2\pi f_N, \quad R_S = Z_N r_{cu}, \quad (\text{A.34})$$

$$L_S = \frac{\text{Streuung} Z_N}{K_C \omega_{EL}}, \quad \Psi_N = \frac{\sqrt{2} U_N}{\omega_{EL}}, \quad (\text{A.35})$$

$$g = \frac{I_{E0}(1 - \text{Streuung})}{K_C \sqrt{2} I_N}, \quad R_D = \frac{R_S}{\text{Daempferfaktor}}, \quad (\text{A.36})$$

$$I_{MNX} = \frac{I_{E0}}{g}, \quad I_{MNY} = \frac{I_{MNX}}{\text{Schenkelpolfaktor}}, \quad (\text{A.37})$$

$$M_N = \frac{p P_{EL}(1 - r_{bg} - r_{cu})}{\omega_{EL}}. \quad (\text{A.38})$$

Inserting the rated data gives

$$U_N = \frac{20 \text{ kV}}{\sqrt{3}} = \boxed{11.547 \text{ kV}}, \quad (\text{A.39})$$

$$Z_N = \frac{11.547 \text{ kV}}{14.434 \text{ kA}} = \boxed{0.799 \text{ } \Omega}, \quad (\text{A.40})$$

$$\omega_{EL} = 2\pi \cdot 50 \text{ Hz} = \boxed{314.159 \text{ rad/s}}, \quad (\text{A.41})$$

$$R_S = 0.799 \text{ } \Omega \cdot 0.001 = \boxed{7.999 \text{ } \Omega \cdot 10^{-4}}, \quad (\text{A.42})$$

$$L_S = \frac{0.05 \cdot 0.799 \text{ } \Omega}{0.5 \cdot 314.159 \text{ rad/s}} = \boxed{2.546 \text{ H} \cdot 10^{-4}}, \quad (\text{A.43})$$

$$\Psi_N = \frac{\sqrt{2} \cdot 11.547 \text{ kV}}{314.159 \text{ rad/s}} = \boxed{51.979 \text{ Wb}}. \quad (\text{A.44})$$

For the excitation-current transformation,

$$g = \frac{2 \text{ } 000 \text{ A}(1 - 0.05)}{0.5\sqrt{2} \cdot 14.434 \text{ kA}} = \boxed{0.186158}, \quad (\text{A.45})$$

$$I_{MNX} = \frac{2 \text{ } 000 \text{ A}}{0.186158} = \boxed{10.743 \text{ kA}}, \quad (\text{A.46})$$

$$I_{MNY} = \frac{10.743 \text{ kA}}{1} = \boxed{10.743 \text{ kA}}. \quad (\text{A.47})$$

Because Daempferfaktor = 1, the damper resistance becomes

$$R_D = \frac{R_S}{1} = \boxed{7.999 \text{ } \Omega \cdot 10^{-4}}. \quad (\text{A.48})$$

The rated electromagnetic torque, including the specified relative friction and copper losses, is

$$M_N = \frac{2 \cdot 400 \text{ MW}(1 - 0.001 - 0.001)}{314.159 \text{ rad/s}} \quad (\text{A.49})$$

$$= \boxed{2.541 \text{ } 39 \cdot 10^6 \text{ N m}}. \quad (\text{A.50})$$

The excitation-winding resistance and its resistance referred by the model equation are

$$R_E = \frac{U_{E0}}{I_{E0}} = \frac{600 \text{ V}}{2 \text{ } 000 \text{ A}} = \boxed{0.300 \text{ } 000 \text{ } \Omega}, \quad (\text{A.51})$$

$$R'_E = g^2 \frac{2}{3} R_E = (0.186158)^2 \frac{2}{3} \cdot 0.3 \text{ } \Omega = \boxed{6.930 \text{ } 97 \cdot 10^{-3} \text{ } \Omega}, \quad (\text{A.52})$$

$$U'_{E0} = g U_{E0} = 0.186158 \cdot 600 \text{ V} = \boxed{111.695 \text{ V}}. \quad (\text{A.53})$$

For $p = 2$, the synchronous mechanical speed is

$$n_N = \frac{60 f_N}{p} = \boxed{1 \text{ } 500 \text{ rpm}}, \quad \omega_{mN} = \frac{\omega_{EL}}{p} = \boxed{157.080 \text{ rad/s}}. \quad (\text{A.54})$$

Interpretation of Ψ_N . The value $\Psi_N = 51.9798 \text{ Wb}$ is the rated peak stator flux linkage in volt-seconds, not the physical air-gap flux in webers per pole. A physical flux value would additionally require the effective number of stator turns and the winding factor.

Parameter definitions

Symbol	Meaning
Streuung	Leakage factor
Daempferfaktor	Damping factor
Schenkelpolfaktor	Salient-pole factor
r_{bg}	Friction-loss factor
r_{cu}	Copper-loss (resistance) factor
p	Number of pole pairs
K_C	Model scaling or correction factor
$U_{N, \text{verkettet}}$	Rated line-to-line RMS voltage
U_N, I_N, Z_N	Rated phase voltage, rated current, and base impedance
f_N, ω_{EL}	Rated electrical frequency and angular frequency
I_{E0}	Reference excitation current
P_{EL}	Electrical power

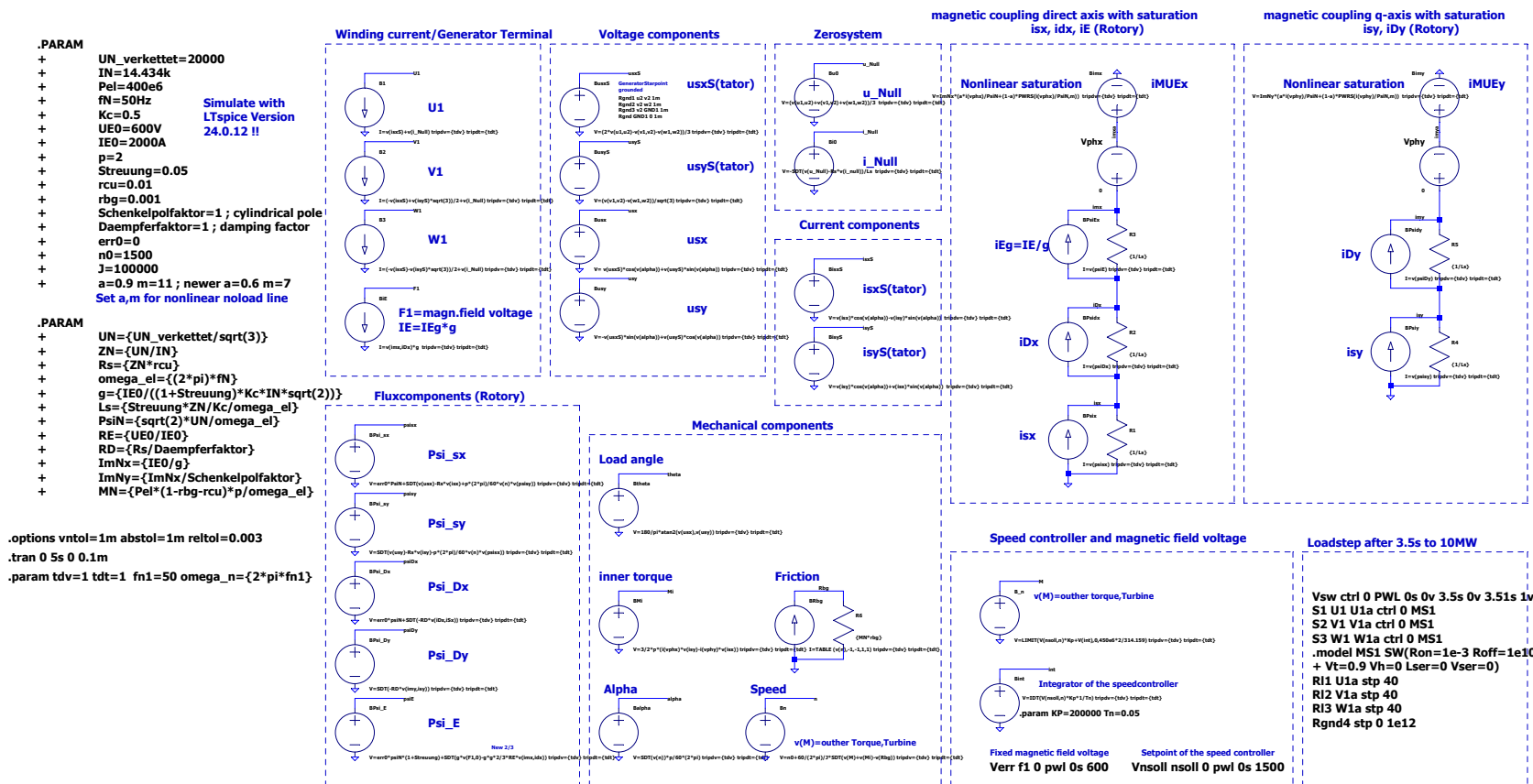


Figure A.1: Synchronous machine schematic model

```

1 * NOTE: idt() = integration function
2 .SUBCKT Block1_fixe_Drehzahl U1 V1 W1 F1 M n GND1
3 + PARAMS:
4 + UN_verkettet=20000
5 + IN=14.434k
6 + Pel=400e6 ;UN_verkettet*IN*sqrt(3)*cosphi of 0.8
7 + fn=50
8 + Kc=0.5
9 + UE0=600V ; Power of exciter = 0.25-5% * SN machine (smaller values for
    higher SN)
10 + IE0=2000A
11 + p=2
12 + Streuung=0.05 ;
13 + rcu=0.001
14 + rbg=0.001
15 + Schenkelpolfaktor=1 ;(1=cylindrical pole 0.5=Salient pole)
16 + Daempferfaktor=1
17 + err0=0
18 + RE_factor=0.6666
19 + n0=1500
20 + n1={n0} ;starts with 1500U/min
21 + alpha_0=0
22 + a=0.9 ; Parameter for nonlinear noload line (should be about 0.6-0.9)
23 + m=7
24 .PARAM
25 + a1={a}; Saturation parameter d-axis
26 + m1={m}; Saturation parameter d-axis
27 + a2={a1}; Saturation parameter q-axis
28 + m2={m1}; Saturation parameter q-axis
29 + UN={UN_verkettet/sqrt(3)}
30 + ZN={UN/IN}
31 + Rs={ZN*rcu}
32 + omega_el={(2*pi)*fn}
33 + Ls={Streuung*ZN/Kc/omega_el}
34 + PsiN={sqrt(2)*UN/omega_el}
35 + RE={UE0/IE0}
36 + RD={Rs/Daempferfaktor}
37 + RDx={RD} ; can be overwritten by setting this parameters on modelline
38 + RDy={RD} ; can be overwritten by setting this parameters on modelline
39 + LDx={Ls} ; can be overwritten by setting this parameters on modelline
40 + LDy={Ls} ; can be overwritten by setting this parameters on modelline
41 + LE={Ls} ; can be overwritten by setting this parameters on modelline
42 + R0={Rs} ; can be overwritten by setting this parameters on modelline
43 + L0={Ls} ; can be overwritten by setting this parameters on modelline (X0
    is 0.03-0.1 p.u)
44 + Lsd={Ls}
45 + Lsq={Ls}
46 + XD={UN/IN/Kc}
47 + XQ={XD*Schenkelpolfaktor}
48 + g={UE0/(UN*sqrt(2)*RE/(XD-omega_el*Lsd))} ; updated formula for g
    parameter
49 + g1={UE0/(UN*sqrt(2)*RE/(XQ-omega_el*Lsq))} ; updated formula for salient

```

```

    pole machine
50 + ImNx={IE0/g} ; d-axis magnetizing current
51 + ImNy={IE0/g1} ;q-axis magnetizing current
52 + MN={Pel*(1-rbg-rcu)*p/omega_el}
53 *
54 * currents of windings
55 G1 U1 U2 VALUE={v(isxS)+v(i_Null)}
56 G2 V1 V2 VALUE={{(-v(isxS)+v(isyS)*sqrt(3))/2+v(i_Null)}}
57 G3 W1 W2 VALUE={{(-v(isxS)-v(isyS)*sqrt(3))/2+v(i_Null)}}
Synchronergenerator_spicecode.txt Gedruckt am 15. August 2026
Seite 2
58 GiE F1 0 VALUE={v(ie)*g}
59 * voltage components
60 EuxS usxS 0 VALUE={{(2*v(u1,u2)-v(v1,v2)-v(w1,w2))/3}}
61 EuyS usyS 0 VALUE={{(v(v1,v2)-v(w1,w2))/sqrt(3)}}
62 Eux usx 0 VALUE={ v(usxS)*cos(v(alpha))+v(usyS)*sin(v(alpha))}
63 Euy usy 0 VALUE={-v(usxS)*sin(v(alpha))+v(usyS)*cos(v(alpha))}
64 * Starpoint
65 R2 v2 GND1 1u
66 R12 u2 GND1 1u
67 R23 w2 GND1 1u
68 RGND1 GND1 0 1e6
69 * Zerosystem
70 Eu0 u_Null 0 VALUE={{(v(u1,u2)+v(v1,v2)+v(w1,w2))/3}}
71 Ei0 i_Null 0 VALUE={idt(v(u_Null)-R0*v(i_null))/L0}
72 * current components
73 EisxS isxS 0 VALUE={v(isx)*cos(v(alpha))-v(isy)*sin(v(alpha))}
74 EisyS isyS 0 VALUE={v(isy)*cos(v(alpha))+v(isx)*sin(v(alpha))}
75 * magnetic coupling of direct axis with saturation
76 Gpsix 0 isx VALUE={v(psisx)}
77 Rsx isx 0 {1/Lsd}
78 Gpsidx isx iDx1 VALUE={v(psiDx)} ;
79 Rsdx iDx1 isx {1/LDx}
80 GpsiEx iDx1 imx1 VALUE={v(psiE)}
81 RsEx imx1 iDx1 {1/LE}
82 vphx imx1 imxa1 0
83 Eimx imxa1 0 VALUE={ImNx*(a1*i(vphx)/PsiN+(1-a1)*PWRS(i(vphx)/PsiN,m1))}
84 * magnetic coupling of quadrature axis with saturation
85 Gpsiy 0 isy VALUE={v(psisy)}
86 Rsy isy 0 {1/Lsq}
87 Gpsidy isy imy1 VALUE={v(psiDy)}
88 Rsdy imy1 isy {1/LDy}
89 vphy imy1 imya1 0
90 Eimy imya1 0 VALUE={ImNy*(a2*i(vphy)/PsiN+(1-a2)*PWRS(i(vphy)/PsiN,m2))}
91 * damper currents
92 Eidx idx 0 VALUE={v(idx1)-v(isx)}
93 Eidy idy 0 VALUE={v(imy1)-v(isy)}
94 * exciter current
95 Eie ie 0 VALUE={v(imx1)-v(idx1)}
96 * Flux components
97 Epsi_sx psisx 0 VALUE={err0*PsiN+idt(v(usx)-Rs*v(isx)+p*(2*pi)/60*v(n)*v(
    psisy))}
98 Epsi_sy psisy 0 VALUE={idt(v(usy)-Rs*v(isy)-p*(2*pi)/60*v(n)*v(psisx))}

```

```

99 Epsi_Dx psiDx 0 VALUE={err0*psiN+idt(-RDx*v(idx))}
100 Epsi_Dy psiDy 0 VALUE={idt(-RDy*v(idy))}
101 Epsi_E psiE 0 VALUE={err0*psiN*(1+Streuung)+idt(v(F1,0)*g*RE_factor-RE*
    RE_factor*g*g*v(ie))}
102 * Load angle
103 Etheta 0 theta VALUE={idt(180/pi*atan2(v(usx),v(usy)))}
104 * inner torque
105 Emi Mi 0 VALUE={1.5*p*(i(vphx)*v(isy)-i(vphy)*v(isx))}
106 * outhet torque
107 EMoment M 0 VALUE={-v(Mi)+v(Rbg)}
108 Vn n 0 {n1}
109 * friction
110 GRbg 0 Rbg TABLE {v(n)} (-1,-1) (1,1)
111 RRbg Rbg 0 {MN*rbg}
112 * Compute angle alpha
113 Ealpha alpha 0 VALUE={alpha_0*pi/180+idt(v(n))*p/60*(2*pi)}
114 .ENDS

```

Listing A.1: Behavioral implementation of a synchronous generator.

```

1  %%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
2  % Standard Parameters Xd,Xq,Xd1,Xd2,..Td01,Td02,..
3  % to Fundamental absolut parameters for ltspice model
4  %%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
5
6  % Physical parameters of Synchronous generator
7  SN=250e6
8  UN_verkettet=13800
9  UN=UN_verkettet/sqrt(3)
10 cosphi=0.8
11 Pel=SN*cosphi
12 IN=SN/UN_verkettet/sqrt(3)
13 ZN=UN/IN
14 ZBase=UN/IN
15 fN=60
16 omega=2*pi()*fN
17 % Exciter Voltage and current
18 Ue0=200 % (choosen free)
19 Ie0=767 % (choosen to meet Td01)
20 % Input of Standard Parameters(Reactances and time constants)
21 x1=0.18
22 xd=1.305
23 xq=0.474
24 xd1=0.296
25 xq1=0
26 xd2=0.252
27 xq2=0.243
28 rcu=0.003
29 % open circuit time constants
30 Td01=4.455 % Td0'
31 Tq01=1 % Tq0'
32 Td02=0.053 % Td0''
33 Tq02=0.1 % Tq0''
34 % computed short circuit time constants
35 Td1=Td01*xd1/xd % (Td')
36 Td2=Td02*xd2/xd1 % (Td'')
37 % Intermediate calculation
38 Xd=xd*ZBase
39 Xq=xq*ZBase
40 xmd=xd-x1
41 xmq=xq-x1
42 xe=xmd^2/(xd-xd1)
43 xrd=xmd^2.0/(xd1-xd2)*(1.0-xmd/xe)^2.0+xmd^2.0/xe

```

Figure A.2: Matlab Listing for converting standard to fundamental parameters

```

44 xrq=xmq^2/(xq-xq2)
45 sigmae=1-xmd/xe
46 sigmaxd=1-xmd/xd
47 sigmard=1-xmd/xrd
48 % Computation of Fundamental parameters for LTspice model
49 % Delete Formulas and overwrite with the values of
50 % Rs,Ls,RE,RDx,RDy,LDx,LDy,LE,R0,L0 below
51 Rs=rcu*ZBase % Rs
52 Ls=x1*ZBase/omega % Ls
53 Lmd=xmd*ZBase/omega % (Lhd3)
54 Lmq=xmq*ZBase/omega % (Lhq3)
55 Lfd=Lmd*sigmae % Le
56 Lkd=(xrd-xmd)*ZBase/omega % LDx
57 Lkq=(xrq-xmq)*ZBase/omega % LDy
58 Rkd=(xrd-xmd^2/xe)*ZBase/omega/Td02 % RDx
59 Rkq=(xrq*xmq*ZBase/omega/Tq02) % RDy
60 Re=Ue0/Ie0*2/3 % RE
61 Re0=Ue0/Ie0
62 g=Ue0/(UN*sqrt(2)*Re0/(Xd-omega*Ls))
63 Res=Re*g*g
64 R0=Rs % R0
65 L0=Ls % L0
66 Td01=Xd/Res/omega % Should be same as above
67 % If not change Ie0 to meet Td01
68
69

```

Figure A.3: Matlab Listing for converting standard to fundamental parameters used in LTspice model

Transformer Model

Formula sheet for a three-phase two-winding transformer

Notation. Indices $k = 1, 2, 3$ identify the transformer legs or phases; p and s denote the primary and secondary windings. Uppercase U and I denote electrical quantities, Φ the magnetic flux, $\Psi = N\Phi$ the flux linkage, and $\Theta = NI$ the magnetomotive force. The example uses vector group Yy0.

Transformer-leg equations

For each leg $k \in \{1, 2, 3\}$, the reluctance associated with the iron-loss resistance is

$$\mathcal{R}_{\text{Fe}} = \frac{N_1^2}{R_{\text{Fe}}}. \quad (\text{B.1})$$

The nonlinear magnetizing characteristic is represented by

$$\Theta_{\mu k} = N_1 I_{\mu N} \left[a \frac{\Phi_k}{\Phi_N} + (1-a) \left(\frac{\Phi_k}{\Phi_N} \right)^m \right], \quad k = 1, 2, 3. \quad (\text{B.2})$$

Equivalently, the magnetizing current of one leg is

$$I_{\mu k} = I_{\mu N} \left[a \frac{\Phi_k}{\Phi_N} + (1-a) \left(\frac{\Phi_k}{\Phi_N} \right)^m \right]. \quad (\text{B.3})$$

Primary-winding equations

For every phase k ,

$$\Phi_{kp} = \frac{\Psi_{kp}}{N_1} = \frac{1}{N_1} \int (U_{kp} - R_1 I_{kp}) dt, \quad I_{kp} = \frac{\Theta_k}{N_1}. \quad (\text{B.4})$$

Written separately for the three phases, this relation applies for $k = 1, 2$, and 3 with the corresponding phase quantities.

Secondary-winding equations

For every phase k ,

$$\Phi_{ks} = \frac{\Psi_{ks}}{N_2} = \frac{1}{N_2} \int (U_{ks} - R_2 I_{ks}) dt, \quad I_{ks} = \frac{\Theta_k}{N_2}. \quad (\text{B.5})$$

The voltage and current reference directions must be chosen consistently with the winding polarities used in the circuit model.

Common core flux and winding flux linkages

For an ideal magnetic coupling of the windings on each leg,

$$\Phi_{kp} = \Phi_{ks} = \Phi_k, \quad k = 1, 2, 3. \quad (\text{B.6})$$

The corresponding flux linkages are

$$\Psi_{kp} = N_1 \Phi_k, \quad \Psi_{ks} = N_2 \Phi_k. \quad (\text{B.7})$$

Thus, in general,

$$\Psi_{kp} \neq \Psi_{ks} \quad \text{when} \quad N_1 \neq N_2, \quad (\text{B.8})$$

even though both windings link the same core flux Φ_k .

Leakage-flux branch

With $\mathcal{R}_{\Phi\sigma}$ denoting the equivalent magnetic reluctance of the leakage path,

$$\Phi_{k\sigma} = \frac{\Theta_k}{\mathcal{R}_{\Phi\sigma}}, \quad k = 1, 2, 3. \quad (\text{B.9})$$

For a leakage inductance $L_{1\sigma}$ referred to the primary winding,

$$L_{1\sigma} = \frac{N_1^2}{\mathcal{R}_{\Phi\sigma}} \quad \Longleftrightarrow \quad \mathcal{R}_{\Phi\sigma} = \frac{N_1^2}{L_{1\sigma}}. \quad (\text{B.10})$$

Tank representation

The tank is represented by an additional magnetic reluctance $\mathcal{R}_{\text{tank}}$. The source text recommends the following approximate choices:

$$\mathcal{R}_{\text{tank}} \approx (0.1 \dots 0.01) \frac{N_1^2}{L_{1\sigma}}, \quad \text{rough initial estimate - (10x-100x leakage inductance),} \quad (\text{B.11})$$

$$\mathcal{R}_{\text{tank}} \approx 10^5 \dots 10^6, \quad \text{tank magnetic reluctance in the model units,} \quad (\text{B.12})$$

$$\mathcal{R}_{\text{tank}} \approx 10^{20}, \quad \text{tank branch absent (practically open).} \quad (\text{B.13})$$

Transformer main data:

Symbol	Meaning
S_N	Three-phase rated apparent power
$U_{1N,LL}$	Primary rated line-to-line voltage
$U_{2N,LL}$	Secondary rated line-to-line voltage
f_N	Rated frequency
N_1	Primary number of turns
u_R	Resistive part of relative short-circuit voltage
u_X	Inductive part of relative short-circuit voltage
i_0	Relative no-load current
p_0	Relative no-load loss, with $p_0 < i_0$
a	Linear weighting in the magnetizing characteristic
m	Exponent of the nonlinear magnetizing term

Per-leg quantities for vector group Yy0

The three-phase values are first converted to one transformer leg:

$$S_{N,\text{leg}} = \frac{S_N}{3}, \quad U_{1N} = \frac{U_{1N,LL}}{\sqrt{3}}, \quad U_{2N} = \frac{U_{2N,LL}}{\sqrt{3}}, \quad (\text{B.14})$$

$$I_{1N} = \frac{S_{N,\text{leg}}}{U_{1N}}, \quad Z_{1N} = \frac{U_{1N}}{I_{1N}}, \quad \omega_N = 2\pi f_N. \quad (\text{B.15})$$

Winding and iron-loss parameters

The short-circuit impedance is split equally between the two windings and referred initially to the primary side:

$$R_1 = \frac{Z_{1N} u_R}{2}, \quad L_{1\sigma} = \frac{Z_{1N} u_X}{2\omega_N}, \quad (\text{B.16})$$

$$R_{\text{Fe}} = \frac{U_{1N}^2}{p_0 S_{N,\text{leg}}}, \quad \mathcal{R}_{R\text{Fe}} = \frac{N_1^2}{R_{\text{Fe}}}, \quad (\text{B.17})$$

$$N_2 = N_1 \frac{U_{2N}}{U_{1N}}, \quad R_2 = R_1 \left(\frac{N_2}{N_1} \right)^2, \quad (\text{B.18})$$

$$\mathcal{R}_{\Phi\sigma} = \frac{N_1^2}{L_{1\sigma}}. \quad (\text{B.19})$$

Magnetizing branch and rated flux

From the no-load current and no-load losses,

$$X_h = \frac{U_{1N}^2}{S_{N,\text{leg}} \sqrt{i_0^2 - p_0^2}}, \quad (\text{B.20})$$

$$I_\mu = \frac{U_{1N}}{X_h}, \quad (\text{B.21})$$

$$I_{\mu N} = \sqrt{2} I_\mu, \quad (\text{B.22})$$

$$\Phi_N = \frac{\sqrt{2} U_{1N}}{\omega_N N_1}. \quad (\text{B.23})$$

The nonlinear characteristic then becomes

$$I_\mu(\Phi) = I_{\mu N} \left[a \frac{\Phi}{\Phi_N} + (1 - a) \left(\frac{\Phi}{\Phi_N} \right)^m \right]. \quad (\text{B.24})$$

Parameter definitions

Symbol	Meaning
Θ_k	Magnetomotive force of leg k
$\Phi_k, \Phi_{k\sigma}$	Main and leakage fluxes of leg k
Ψ_{kp}, Ψ_{ks}	Primary and secondary flux linkages
$\mathcal{R}_{RFe}$	Magnetic reluctance associated with the iron-loss branch
$\mathcal{R}_{\Phi\sigma}$	Equivalent leakage-path reluctance
$\mathcal{R}_{\text{tank}}$	Tank-path magnetic reluctance
R_1, R_2	Primary and secondary winding resistances
R_{Fe}	Equivalent iron-loss resistance
$L_{1\sigma}$	Primary-referred leakage inductance
X_h	Main magnetizing reactance
$I_{\mu N}, \Phi_N$	Rated peak magnetizing current and rated peak flux
a, m	Shape parameters of the nonlinear magnetization curve

Implementation notes. The time integrals may be implemented with behavioural sources in LTspice. When forming the winding equations, verify the chosen voltage polarities, current reference directions, initial flux, and the sign of each magnetomotive-force contribution. The numerical tank-reluctance range is model- and unit-dependent and should be validated against the intended zero-sequence behaviour.

Typeset from the supplied transformer-model notes. English wording and notation have been standardized; explicitly identified dimensional inconsistencies in the source have been corrected.

Rated data: 300 MVA, 400 kV / 120 kV, 50 Hz

Symbol	Value	Meaning
S_N	$300 \times 10^6 \text{ VA}$	Three-phase rated apparent power
$U_{1N,LL}$	$400 \times 10^3 \text{ V}$	Primary rated line-to-line voltage
$U_{2N,LL}$	$120 \times 10^3 \text{ V}$	Secondary rated line-to-line voltage
f_N	50 Hz	Rated frequency
N_1	1000	Primary number of turns
u_R	0.002	Resistive part of relative short-circuit voltage
u_X	0.2	Inductive part of relative short-circuit voltage
i_0	0.0006	Relative no-load current
p_0	0.0004	Relative no-load loss, with $p_0 < i_0$
a	0.75	Linear weighting in the magnetizing characteristic
m	9	Exponent of the nonlinear magnetizing term

Assumptions. The calculation uses a balanced per-phase equivalent circuit for vector group Yy0. The total short-circuit resistance and leakage reactance are split equally between the primary winding and the secondary winding referred to the primary side. All magnetizing-branch quantities are initially referred to the 400 kV side.

Per-leg rated quantities

The three-phase rated values are converted to one transformer leg:

$$S_{N,\text{leg}} = \frac{S_N}{3} = \frac{300 \text{ MV A}}{3} = 100 \text{ MV A}, \quad (\text{B.25})$$

$$U_{1N} = \frac{U_{1N,LL}}{\sqrt{3}} = \frac{400 \text{ kV}}{\sqrt{3}} = 230.940 \text{ kV}, \quad (\text{B.26})$$

$$U_{2N} = \frac{U_{2N,LL}}{\sqrt{3}} = \frac{120 \text{ kV}}{\sqrt{3}} = 69.282 \text{ kV}, \quad (\text{B.27})$$

$$I_{1N} = \frac{S_{N,\text{leg}}}{U_{1N}} = 433.013 \text{ A}, \quad (\text{B.28})$$

$$Z_{1N} = \frac{U_{1N}}{I_{1N}} = \frac{U_{1N,LL}^2}{S_N} = 533.333 \Omega, \quad (\text{B.29})$$

$$\omega_N = 2\pi f_N = 314.159 \text{ rad/s}. \quad (\text{B.30})$$

The turns ratio and secondary number of turns are

$$u = \frac{N_1}{N_2} = \frac{U_{1N}}{U_{2N}} = \frac{400}{120} = 3.33333, \quad (\text{B.31})$$

$$N_2 = N_1 \frac{U_{2N}}{U_{1N}} = 1000 \frac{120}{400} = \boxed{300}. \quad (\text{B.32})$$

Winding parameters

The total short-circuit resistance and leakage reactance referred to the primary side are

$$R'_k = u_R Z_{1N} = 0.002 \cdot 533.333 \, \Omega = 1.06667 \, \Omega, \quad (\text{B.33})$$

$$X'_{k\sigma} = u_X Z_{1N} = 0.2 \cdot 533.333 \, \Omega = 106.667 \, \Omega, \quad (\text{B.34})$$

$$L'_{k\sigma} = \frac{X'_{k\sigma}}{\omega_N} = 0.339531 \, \text{H}. \quad (\text{B.35})$$

With equal division between the two windings,

$$R_1 = R'_2 = \frac{R'_k}{2} = \boxed{0.533333 \, \Omega}, \quad (\text{B.36})$$

$$L_{1\sigma} = L'_{2\sigma} = \frac{L'_{k\sigma}}{2} = \boxed{0.169765 \, \text{H}}. \quad (\text{B.37})$$

The actual secondary-side parameters follow from $(N_2/N_1)^2 = 0.09$:

$$R_2 = R'_2 \left(\frac{N_2}{N_1} \right)^2 = 0.533333 \, \Omega \cdot 0.09 = \boxed{0.048000 \, \Omega}, \quad (\text{B.38})$$

$$L_{2\sigma} = L'_{2\sigma} \left(\frac{N_2}{N_1} \right)^2 = 0.169765 \, \text{H} \cdot 0.09 = \boxed{0.0152789 \, \text{H}}. \quad (\text{B.39})$$

For the magnetic-circuit leakage representation,

$$\mathcal{R}_{\Phi\sigma} = \frac{N_1^2}{L_{1\sigma}} = \frac{1000^2}{0.169765 \, \text{H}} = \boxed{5.89049 \cdot 10^6 / \text{H}}. \quad (\text{B.40})$$

Iron-loss parameters

The total rated no-load loss is

$$P_0 = p_0 S_N = 0.0004 \cdot 300 \, \text{MV A} = 120 \, \text{kW}. \quad (\text{B.41})$$

Thus, each transformer leg represents 40 kW of iron loss. The primary-referred iron-loss

resistance is

$$R_{\text{Fe}} = \frac{U_{1N}^2}{p_0 S_{N,\text{leg}}} \quad (\text{B.42})$$

$$= \frac{(230.940 \text{ kV})^2}{0.0004 \cdot 100 \text{ MV A}} = \boxed{1.333 \text{ 33 M}\Omega}. \quad (\text{B.43})$$

The corresponding RMS iron-loss current per phase is

$$I_{\text{Fe}} = \frac{U_{1N}}{R_{\text{Fe}}} = \boxed{0.173 \text{ 205 A}}. \quad (\text{B.44})$$

In the magnetic-circuit representation used by the transformer model,

$$\mathcal{R}_{R_{\text{Fe}}} = \frac{N_1^2}{R_{\text{Fe}}} = \frac{1000^2}{1.333 \text{ 33} \cdot 10^6 \Omega} = \boxed{0.750000}. \quad (\text{B.45})$$

Magnetizing branch and rated flux

The rated RMS no-load current is

$$I_0 = i_0 I_{1N} = 0.0006 \cdot 433.013 \text{ A} = 0.259 \text{ 808 A}. \quad (\text{B.46})$$

After subtracting the active iron-loss component vectorially, the RMS magnetizing current is

$$I_\mu = I_{1N} \sqrt{i_0^2 - p_0^2} \quad (\text{B.47})$$

$$= 433.013 \text{ A} \sqrt{0.0006^2 - 0.0004^2} = \boxed{0.193 \text{ 649 A}}. \quad (\text{B.48})$$

The magnetizing reactance and inductance referred to the primary side are

$$X_h = \frac{U_{1N}}{I_\mu} = \frac{U_{1N}^2}{S_{N,\text{leg}} \sqrt{i_0^2 - p_0^2}} = \boxed{1.192 \text{ 57 M}\Omega}, \quad (\text{B.49})$$

$$L_h = \frac{X_h}{\omega_N} = \boxed{3.796 \text{ 07} \cdot 10^3 \text{ H}}. \quad (\text{B.50})$$

The peak magnetizing current used in the nonlinear characteristic is

$$I_{\mu N} = \sqrt{2} I_\mu = \boxed{0.273 \text{ 861 A}}. \quad (\text{B.51})$$

For a sinusoidal phase voltage, the rated peak core flux is

$$\Phi_N = \frac{\sqrt{2} U_{1N}}{\omega_N N_1} \quad (\text{B.52})$$

$$= \frac{\sqrt{2} \cdot 230.940 \text{ kV}}{314.159 \text{ rad/s} \cdot 1000} = \boxed{1.039 \text{ 60 Wb}}. \quad (\text{B.53})$$


With $a = 0.75$ and $m = 9$, the numerical magnetizing characteristic becomes

$$I_{\mu}(\Phi) = 0.273\,861\,\text{A} \left[0.75 \frac{\Phi}{1.039\,60\,\text{Wb}} + 0.25 \left(\frac{\Phi}{1.039\,60\,\text{Wb}} \right)^9 \right]. \quad (\text{B.54})$$

Calculated parameter summary

Parameter	Calculated value	Reference
N_2	300	Secondary number of turns
R_1	0.533 333 Ω	Primary winding resistance
$L_{1\sigma}$	0.169 765 H	Primary leakage inductance
R'_2	0.533 333 Ω	Secondary resistance referred to primary
$L'_{2\sigma}$	0.169 765 H	Secondary leakage inductance referred to primary
R_2	0.048 000 Ω	Actual secondary resistance
$L_{2\sigma}$	0.015 278 9 H	Actual secondary leakage inductance
R_{Fe}	1.333 33 M Ω	Iron-loss resistance, primary-referred
X_h	1.192 57 M Ω	Magnetizing reactance, primary-referred
L_h	$3.796\,07 \cdot 10^3$ H	Linear magnetizing inductance
$I_{\mu N}$	0.273 861 A	Rated peak magnetizing current
Φ_N	1.039 60 Wb	Rated peak core flux
$\mathcal{R}_{\text{Fe}}$	0.750000	Iron-loss magnetic-model parameter
$\mathcal{R}_{\Phi\sigma}$	$5.890\,49 \cdot 10^6$ /H	Leakage-path magnetic parameter

One Winding

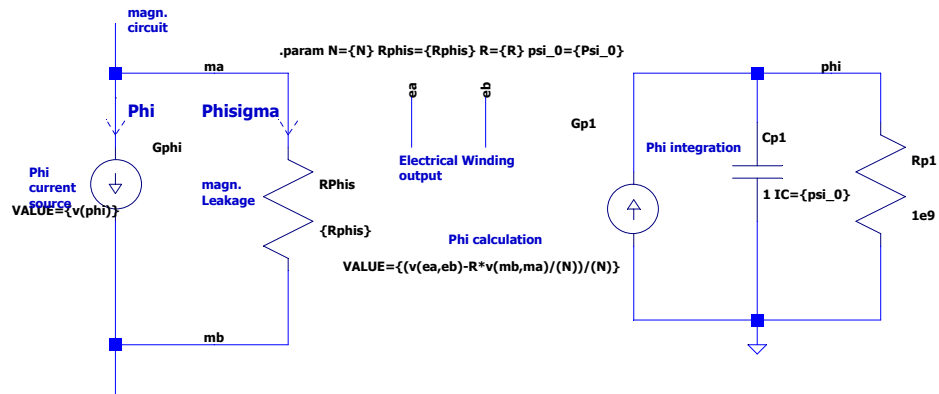

One Transformerleg

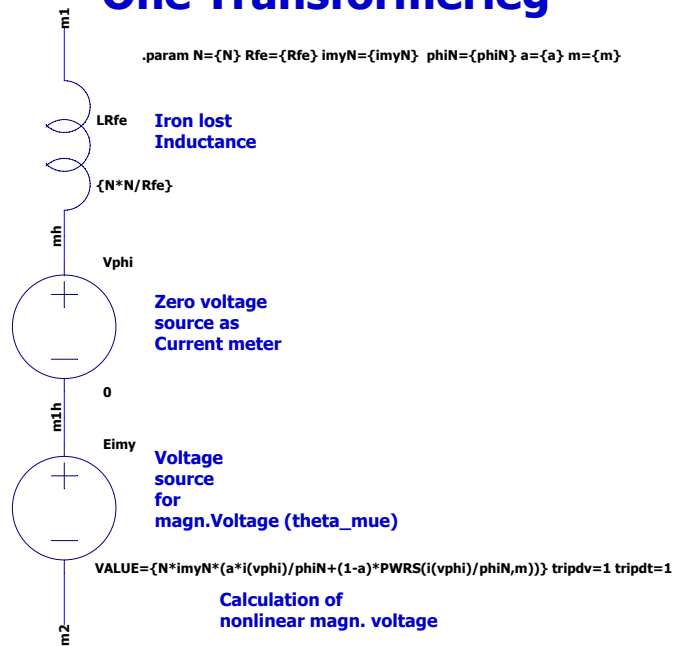


Figure B.2: One winding and one leg of the transformer model

```

1 .SUBCKT RUYy0_400k_120k_300MVA 1U 1V 1W 1N 2U 2V 2W 2N
2 + PARAMS:
3 + SN=300e6
4 + U1Nenn=400e3
5 + U20=120e3
6 + fn={fn1}
7 + N1=1000
8 + uR=0.002
9 + uX=0.2
10 + i0=0.0006
11 + p0=0.0004
12 + a=0.75 ; FS
13 + m=9;FS
14 + psi_0=0 ; Remanence-parameter 0,1,-1
15 + psir=1
16 + psis=-0.5
17 + psit=-0.5
18 + tpsi0=1000s ; Remanence-timepoint
19 + tpsid=0.1ms ; On-time of remanent flux
20 + ron=0.00001 ; On - Parameter of switcher for remanent flux
21 + bf=0 ; bf=1 -> middle leg with shorter magn. path correction factor
22 + rkessel=6e5 ; Tank resistance
23 + l_=0
24 + middle=0
25 + stproz=1.0
26 + ctrl={1+(l_-middle)*stproz/100} ; simple Tap changer
*****
27 Xu 1U 1N 2U 2N magn1 magn2 Trafoschenkel2_Yy
28 + PARAMS:
29 + SN={SN/3} U1N={U1Nenn/sqrt(3)} U20={U20/sqrt(3)} fn={fn} N1={N1} uR={uR}
30 + uX={uX} i0={i0*IF(bf==0,1,1.2)} p0={p0*IF(bf==0,1,1.2)} a={a} m={m}
31 + psi_0={psir*psi_0} tpsi0={tpsi0} tpsid={tpsid} ron={ron} ctrl={ctrl}
*****
32 Xv 1V1N 2V 2N magn1 magn2 Trafoschenkel2_Yy
33 + PARAMS:
34 + SN={SN/3} U1N={U1Nenn/sqrt(3)} U20={U20/sqrt(3)} fn={fn} N1={N1} uR={uR}
35 + uX={uX} i0={i0*IF(bf==0,1,0.6)} p0={p0*IF(bf==0,1,1.2)} a={a} m={m}
36 + psi_0={psir*psi_0} tpsi0={tpsi0} tpsid={tpsid} ron={ron} ctrl={ctrl}
*****
37 Xw 1W 1N 2W 2N magn1 magn2 Trafoschenkel2_Yy
38 + PARAMS:
39 + SN={SN/3} U1N={U1Nenn/sqrt(3)} U20={U20/sqrt(3)} fn={fn} N1={N1} uR={uR}
40 + uX={uX} i0={i0*IF(bf==0,1,1.2)} p0={p0*IF(bf==0,1,1.2)} a={a} m={m}
41 + psi_0={psir*psi_0} tpsi0={tpsi0} tpsid={tpsid} ron={ron} ctrl={ctrl}
*****
42 Rm magn1 0 1MEG
43 Rkessel magn1 magn2 {rkessel}
44 RGND1U 1U 0 1e12
45 RGND1V 1V 0 1e12
46 RGND1W 1W 0 1e12
47 RGND2U 2U 0 1e12

```

```

48 RGND2V 2V 0 1e12
49 RGND2W 2W 0 1e12
50 RGND1N 1N 0 1e12
51 RGND2N 2N 0 1e12
52 .ENDS
*****
54 .SUBCKT Trafoschenkel2_Yy 1_1 1_2 2_1 2_2 magnP1 magnP2
55 + PARAMS:
56 + SN=10kVA
57 + U1N=400V
58 + U20=400V
59 + fn={fn1}
60 + N1=1000
61 + uR=0.04
62 + uX=0.08
63 + i0=0.05
64 + p0=0.005
65 + a={0.3} ; FS
66 + m={7} ; FS
67 + psi_0=0 ; Remanenzparameter 0,1,-1
68 + tpsi0=40ms
69 + tpsid=0.1ms
70 + ron=0.00001
71 + ctrl=1
72 .PARAM
73 + I1N={SN/U1N}
74 + Z1N={U1N/I1N}
75 + omegaN={(2*pi)*fn}
76 + R1={Z1N*uR/2}
77 + L1s={Z1N*uX/2/omegaN}
78 + RFe={U1N*U1N/(p0*SN)}
79 + N2={N1*U20/U1N}
80 + R2={R1*N2/N1*N2/N1}
81 + Xh={(U1N*U1N)/(SN*sqrt(i0*i0-p0*p0))} ;FS
82 + iu={U1N/Xh} ;FS
83 + ImyN={sqrt(2)*iu} ;FS
84 + phiN={sqrt(2)*U1N/omegaN/N1}
85 + a={a} ; FS
86 + m={m} ; FS
*****
87 * Windingscurrents
88 Gi1 1_1 1_2 VALUE={v(a,magnP1)/(N1*ctrl)}
89 Rpi1 1_1 1_2 1000MEG
90 Gi2 2_1 2_2 VALUE={v(b,a)/N2}
91 Rpi2 2_1 2_2 1000MEG
92 * Windings
*****
93 X_W1 magnP1 a 1_1 1_2 winding_Yy
94 +PARAMS: R={R1} N={N1} Rphis={N1*N1/L1s}
95 +psi_0={psi_0*phiN} tpsi0={tpsi0} tpsid={tpsid} ron={ron} ctrl={ctrl}
*****
96 X_W2 a b 2_1 2_2 winding_Yy
97 +PARAMS: R={R2} N={N2} Rphis={N1*N1/L1s}

```

```

98 +psi_0={psi_0*phiN} tpsi0={tpsi0} tpsid={tpsids} ron={ron} ctrl=1
*****
99 * Iron leg
100 X_SCH b magnP2Leg_Yy PARAMS:
101 + N={N1} RFe={RFe} ImyN={ImyN} ctrl={ctrl}
102 + phiN={phiN} a={a} m={m}
103 .ENDS
104 *****
105 .SUBCKT winding_Yy ma mb ea eb
106 +PARAMS: R=1 N=1 Rphis=1 psi_0=0 tpsi0=1000s
+ tpsid=0.1ms ron=0.00001 ctrl=1
107 Gphi ma mb VALUE={v(phi)}
108 Rphis ma mb {Rphis*ctrl*ctrl}
109 ; Flux phi
110 Gp 0 phi VALUE={(v(ea,eb)-R*ctrl*v(mb,ma))/(N*ctrl)}/(N*ctrl)}
111 Cp phi 0 1 IC=0
112 Rpphi 01000MEG
113 Vctrl ctrl 0 pw1 0s 0v {tpsi0+1p} 0v {tpsi0+tpsids+2p} 1v
+ v{tpsi0+2*tpsids+3p} 1v {tpsi0+3*tpsids+4p} 0v
114 S1 phi phix ctrl 0 MS1
115 .model MS1 SW(Ron={Ron} Roff=1e9 Vt=0.9 Vh=0 Lser=0 Vser=0)
116 E1 phix 0 value={psi_0}
117 .ENDS ;
118 *****
119 * magnetic leg
120 .SUBCKT Leg_Yy m1 m2
121 +PARAMS: N=1 RFe=1 ImyN=1 a=1 phiN=1 m=9 ctrl=1
122 LRFem1 mh {N*ctrl*N*ctrl/RFe} Rser={0.001m*N*N/RFe} ; Rser=parasitic
Value
123 vphi mh mh1 0
124 rphi mh 0 1e12
125 Eimy mh1 m2
126 +VALUE={N*imyN*(a*i(vphi)/phiN+(1-a)*PWRS(i(vphi)/phiN,m))}
127 .ENDS;
128 *****

```

Listing B.1: Behavioral implementation of a three-phase transformer.

C Mathematical Modelling with Behavioral Sources in LTspice

C.1 Behavioral E and G Sources

Behavioral voltage and current sources make it possible to implement mathematical models directly in LTspice. Node voltages, branch currents, parameters, arithmetic operations, logical operations, and built-in functions can be combined in one expression.

Basic LTspice syntax

An E source generates a voltage between its output nodes:

```
E1 node1 node2 VALUE={mathematical_expression}
```

A G source generates a branch current between its output nodes:

```
G1 node1 node2 VALUE={mathematical_expression}
```

Typical expression operands are

```
V(node)           ; node voltage relative to ground  
V(node_plus,node_minus) ; differential node voltage  
I(Vsense)          ; current through a voltage source  
Ix(U1:pin)         ; current into a subcircuit pin
```

Elements used in the toolboxes. The principal element designators are V, I, L, C, R, K, E, G, S, T, and O. Consult the LTspice help for the precise syntax, sign convention, and analysis restrictions of each element.

Important C.1 – (Dimensional consistency)

The value returned by an E-source expression is interpreted as volts; the value returned by a G-source expression is interpreted as amperes. LTspice does not enforce physical dimensional consistency inside a behavioral expression. The model author must therefore verify all scaling factors and units.

C.2 Functions in Behavioral Expressions

The following functions can be used in behavioral E and G sources. Optional arguments are shown in square brackets. Function availability can depend on the installed LTspice version.

Table C.1: Functions available in LTspice behavioral expressions.

Function	Description
<code>abs(x)</code>	Absolute value of x .
<code>absdelay(x, t[, tmax])</code>	Delays x by t ; the optional maximum delay is $t_{\max}$.
<code>acos(x)</code>	Real part of the arc cosine. For example, <code>acos(-5)</code> returns 3.14159, not a complex result.
<code>arccos(x)</code>	Synonym for <code>acos(x)</code> .
<code>acosh(x)</code>	Real part of the inverse hyperbolic cosine.
<code>asin(x)</code>	Real part of the arc sine. Out-of-domain arguments are limited to the real result.
<code>arcsin(x)</code>	Synonym for <code>asin(x)</code> .
<code>asinh(x)</code>	Inverse hyperbolic sine.
<code>atan(x)</code>	Arc tangent of x .
<code>arctan(x)</code>	Synonym for <code>atan(x)</code> .
<code>atan2(y, x)</code>	Four-quadrant arc tangent of y/x .
<code>atanh(x)</code>	Inverse hyperbolic tangent.
<code>buf(x)</code>	Returns 1 if $x > 0.5$; otherwise returns 0.
<code>cbrt(x)</code>	Real cube root of x .
<code>ceil(x)</code>	Smallest integer greater than or equal to x .
<code>cos(x)</code>	Cosine of x ; the argument is in radians.
<code>cosh(x)</code>	Hyperbolic cosine of x .
<code>ddt(x)</code>	Time derivative dx/dt .
<code>delay(x, t[, tmax])</code>	Same as <code>absdelay(x, t[, tmax])</code> .
<code>dnlim(x, A, Delta)</code>	Smooth approximation of $\max(x, A)$ with first-derivative transition width Δ .
<code>exp(x)</code>	Exponential function e^x .
<code>floor(x)</code>	Largest integer less than or equal to x .
<code>hypot(x, y)</code>	Returns $\sqrt{x^2 + y^2}$ with suitable numerical scaling.
<code>idt(x[, ic[, a]])</code>	Integrates x ; ic is the optional initial condition and the integrator is reset when a is true.
<code>idtm(x[, ic[, m[, o]])</code>	Integrates x , resets on reaching modulus m , and offsets the output by o .
<code>if(x, y, z)</code>	Returns y if $x > 0.5$; otherwise returns z .
<code>int(x)</code>	Converts x to an integer.
<code>inv(x)</code>	Returns 0 if $x > 0.5$; otherwise returns 1.
<code>limit(x, y, z)</code>	Returns the intermediate value of x , y , and z .
<code>ln(x)</code>	Natural logarithm of x .
<code>log(x)</code>	Alternate syntax for <code>ln(x)</code> .
<code>log10(x)</code>	Base-10 logarithm of x .
<code>max(x, y)</code>	Greater of x and y .
<code>min(x, y)</code>	Smaller of x and y .
<code>mod(x, y)</code>	Remainder of the division x/y .
<code>noise()</code>	Returns 1 during a .noise analysis; otherwise returns 0.
<code>pow(x, y)</code>	Real part of x^y ; for example, <code>pow(-1, 0.5)</code> returns 0 rather than an imaginary value.

Continued on next page

Table C.1: Functions available in LTspice behavioral expressions (continued).

Function	Description
<code>pwr(x, y)</code>	Returns $ x ^y$.
<code>pwrsgn(x, y)</code>	Returns $\text{sgn}(x) x ^y$.
<code>rand(x)</code>	Pseudorandom value between 0 and 1 determined by the integer value of x .
<code>random(x)</code>	Similar to <code>rand(x)</code> , but transitions smoothly between values.
<code>round(x)</code>	Integer nearest to x .
<code>sdt(x[, ic[, assert]])</code>	Alternate syntax for <code>idt(x[, ic[, assert]])</code> .
<code>sgn(x)</code>	Sign of x : -1, 0, or 1.
<code>sin(x)</code>	Sine of x ; the argument is in radians.
<code>sinh(x)</code>	Hyperbolic sine of x .
<code>smallsig()</code>	Returns 1 during a .ac or .noise analysis; otherwise returns 0.
<code>square(x)</code>	Returns x^2 .
<code>sqrt(x)</code>	Square root of x .
<code>table(x, a, b, c, d, ...)</code>	Linearly interpolates a value for x from the point pairs $(a, b), (c, d), \dots$
<code>table(x, .include `filename')</code>	Interpolates from point pairs stored as numbers in an included file.
<code>tan(x)</code>	Tangent of x .
<code>tanh(x)</code>	Hyperbolic tangent of x .
<code>u(x)</code>	Unit step: 1 if $x > 0$; otherwise 0.
<code>uplim(x, A, Delta)</code>	Smooth approximation of $\min(x, A)$ with first-derivative transition width Δ .
<code>uramp(x)</code>	Returns x if $x > 0$; otherwise returns 0.
<code>white(x)</code>	Pseudorandom value between -0.5 and 0.5 with smoother transitions than <code>random(x)</code> .
<code>xor(x, y)</code>	Converts x and y to Boolean values and returns their exclusive OR.
<code>!(x)</code>	Alternate syntax for <code>inv(x)</code> .
<code>~(x)</code>	Alternate syntax for <code>inv(x)</code> .

C.3 Operators and Precedence

Table C.2 lists the behavioral-expression operators in ascending order of precedence. Operators in the same group have equal precedence; parentheses should be used whenever the intended evaluation order could be ambiguous.

Table C.2: LTspice behavioral-expression operators in ascending order of precedence.

Operator	Description
<code>&</code>	Converts both operands to Boolean values and returns logical AND.
<code> </code>	Converts both operands to Boolean values and returns logical OR.
<code>^</code>	Converts both operands to Boolean values and returns logical XOR.
<code>>, <</code>	Greater-than and less-than comparisons.
<code>>=, <=</code>	Greater-than-or-equal and less-than-or-equal comparisons.

Table C.2: LTspice behavioral-expression operators (continued).

Operator	Description
==	Returns true if both expressions are equal.
!=, <>	Returns true if both expressions are unequal.
+, -	Floating-point addition and subtraction.
*, /	Floating-point multiplication and division.
%	Floating-point remainder; equivalent to $\text{mod}(x, y)$.
**	Raises the left operand to the power of the right operand. Only the real part is returned.
!, ~	Unary Boolean inversion of the following expression.

Boolean conversion. For the behavioral functions `buf()`, `if()`, and `inv()`, LTspice treats values greater than 0.5 as true. The exact threshold behavior of logical operators should be checked when expressions can take non-binary analog values.

C.4 Example: Single-Phase Transformer

The example implements the voltage equations by numerical integration and solves the flux-current relations as a simultaneous linear system.

C.4.1 Differential equations

The winding-voltage equations are

$$u = R_1 i_1 + \frac{d\psi_1}{dt}, \quad (\text{C.1})$$

$$0 = (R_2 + R_{\text{load}}) i_2 + \frac{d\psi_2}{dt}. \quad (\text{C.2})$$

Consequently,

$$\frac{d\psi_1}{dt} = u - R_1 i_1, \quad (\text{C.3})$$

$$\frac{d\psi_2}{dt} = -(R_2 + R_{\text{load}}) i_2. \quad (\text{C.4})$$

C.4.2 Flux-current equations

The coupled linear system is

$$\begin{bmatrix} \psi_1 \\ \psi_2 \end{bmatrix} = L_{1h} \begin{bmatrix} 1 + \sigma_1 & 1 \\ 1 & 1 + \sigma_2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}. \quad (\text{C.5})$$

Equivalently, the two residual equations are

$$0 = \psi_1 - (1 + \sigma_1) L_{1h} i_1 - L_{1h} i_2, \quad (\text{C.6})$$

$$0 = \psi_2 - L_{1h} i_1 - (1 + \sigma_2) L_{1h} i_2. \quad (\text{C.7})$$

C.4.3 LTspice netlist

```

* Single-phase transformer using behavioral sources
* Parameters
.PARAM U=20 R1=10 R2=8 R_Last=17
.PARAM L1h=0.1 sigma1=0.1 sigma2=0.15

* Integrator for flux psi1.
* G-C-R realization is used because idt() can be less robust.
Gpsi1 0 psi1 VALUE={ U - R1*V(i1) }
Cpsi1  psi1 0 1 IC=0
Rpsi1  psi1 0 1E6

* Integrator for flux psi2
Gpsi2 0 psi2 VALUE={ -(R2+R_Last)*V(i2) }
Cpsi2  psi2 0 1 IC=0
Rpsi2  psi2 0 1E6

* Simultaneous linear system
Gi1 0 i1 VALUE={ V(psi1)
+ (-(1+sigma1)*L1h*V(i1)-L1h*V(i2)) }
Ri1 i1 0 1E12

Gi2 0 i2 VALUE={ V(psi2)
+ (-L1h*V(i1)-(1+sigma2)*L1h*V(i2)) }
Ri2 i2 0 1E12

.TRAN 0.001 0.04 0 0.001 UIC

```

Listing C.1: Behavioral implementation of a single-phase transformer.

Remark C.1 – (Solution of the algebraic system)

The resistances R_{i1} and R_{i2} are set to $1 \cdot 10^{12} \Omega$. The G-source currents can therefore produce only negligible node voltages unless their behavioral expressions are nearly zero. During each Newton iteration, LTspice consequently adjusts $V(i1)$ and $V(i2)$ until both residual equations are satisfied simultaneously. The node voltages thus represent the calculated currents i_1 and i_2 .

Important C.2 – (Numerical interpretation of the G-C-R integrator)

With $C_{psi1}=1 \text{ F}$, the capacitor relation gives $dV(psi1)/dt = I(Gpsi1)$, so the node voltage directly represents flux linkage. The parallel $1 \text{ M}\Omega$ resistor provides a DC path but also introduces a small leakage term. Increase its value if this artificial decay is significant, while retaining a sufficiently robust DC operating point.

Appendix Summary

Behavioral E and G sources allow differential equations, algebraic equations, logical functions, and lookup tables to be implemented directly in LTspice. E sources return voltages, whereas G sources return currents. Integrators may be formed either with `idt()` or explicitly with a G-C-R network. A simultaneous algebraic system can be solved by expressing each residual with a behavioral G source and forcing it toward zero through a very large shunt resistance. Careful attention to sign conventions, units, damping, and operator precedence is essential for numerically robust models.

D Download and Installation of LTspice and the Power-System Toolboxes

D.1 Purpose and Required Downloads

The examples in this book use LTspice Version 24.0.12 together with two power-system toolboxes:

- **Transient toolbox:** models and examples for electromagnetic transient simulations of high-energy power networks;
- **Steady-state toolbox:** models and examples for load-flow and steady-state simulations.

This book concentrates on transient simulations. The steady-state toolbox is optional and is required only when the corresponding load-flow models are to be used.

Files to download

Download the following archive from the project homepage: The transient and loadflow Toolboxes and the LTspice 24.0.12 simulator installation file in one archive `ltspice.zip`; The file is big because there is also packed the now free MicroCap12 simulator with Library file for loadflow and transient simulation and with some examples! This file seems a little messy because it's the development version.

If you only need the Ltspice toolbox files best download the archive from the ltspice usergroup in the files-z_yahoo section textttadventures with loadflow. NOTE: The ltspice simulator 24.0.12 has to be downloading separately

Project homepage:

```
my homepage: <www.friedrichschmidt.at> or  
Ltspice usergroup files at: <https://groups.io/g/LTspice/files/z_yahoo/  
adventures%20with%20loadflow>
```

Important D.1 – (Version used by this book)

The models and screenshots described in this book were prepared for LTspice Version 24.0.12. Newer releases may have problems displaying simulation results in the waveform viewer. Best Retain the 24.0.12 installer if exact reproducibility is required.

D.2 Installing LTspice 24.0.12

1. Extract the downloaded LTspice archive to a temporary folder.
2. Right-click the installer and select RUN AS ADMINISTRATOR.
3. Complete the installation using the default installation options.
4. Start LTspice once and close it again before copying the toolboxes. This confirms that the simulator has been installed correctly and allows it to create its normal user configuration files.

Administrator rights. Administrator rights are required only for the LTspice installation when the installer writes to protected Windows folders. The toolbox files themselves are installed in the user's Documents folder and should normally not require administrator rights.

D.3 Installing the Toolboxes

In the paths below, replace <username> with the actual Windows user name. Extract the transient toolbox into

```
C:\Users\<username>\Documents\ltspice
```

After extraction, the transient-toolbox folder must be

```
C:\Users\<username>\Documents\ltspice\loadflow_transient
```

If the steady-state toolbox is also required, extract it so that the following folder exists:

```
C:\Users\<username>\Documents\ltspice\loadflow_steady_state
```

Important D.2 – (Check the extracted folder level)

Avoid an additional, duplicated directory level such as ltspice\ltspice\loadflow_transient. The search paths configured in LTspice must point directly to the folders that contain the toolbox symbols and library files.

Updating an existing installation. If a toolbox folder already exists, make a backup before extracting a newer archive. This preserves locally modified symbols, models, plot settings, and example circuits.

D.4 Configuring Search Paths

Start LTspice and open the configuration dialog with

TOOLS → CONTROL PANEL.

Open the SYM. & LIB. SEARCH PATHS tab. Add the transient-toolbox path to both the **Symbol Search Path** and the **Library Search Path**:

```
C:\Users\<username>\Documents\ltspice\loadflow_transient
```

Thus, the same path is entered twice: once in each of the two search-path lists.

If the steady-state toolbox is installed, also add

```
C:\Users\<username>\Documents\ltspice\loadflow_steady_state
```

to both search-path lists.

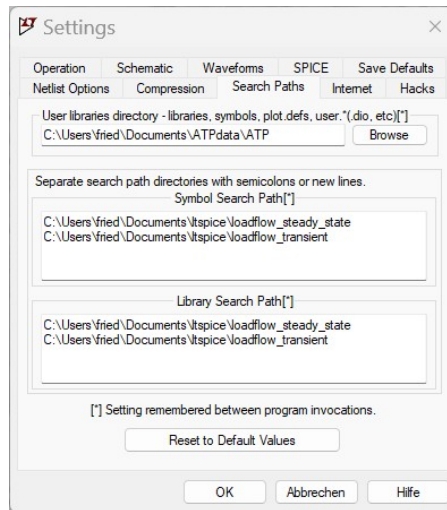


Figure D.1: Symbol and Library search path tab

Table D.1: Required LTspice symbol and library search paths.

Toolbox	Folder	Add to both lists
Transient	C:\Users\<username>\Documents\ltspice\loadflow_transient	Yes
Steady state	C:\Users\<username>\Documents\ltspice\loadflow_steady_state	Yes

D.5 Configuring the Simulator

Keep the Control Panel open and configure the following tabs.

D.5.1 SPICE tab

Set the numerical solver to

Solver: Alternate.

The alternate solver is recommended for the large networks, nonlinear magnetic models, switches, and behavioral equations used in the transient toolbox.

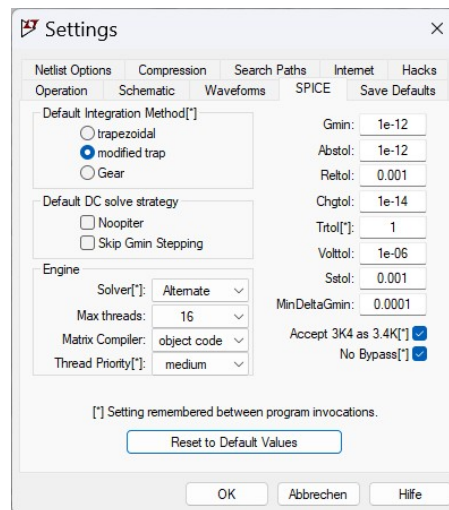


Figure D.2: Spice tab

D.5.2 Save Defaults tab

Enable the first three checkboxes on this tab. The exact labels can vary slightly between LTspice builds. These options ensure that the internal data required by many toolbox plots and hierarchical models are retained.

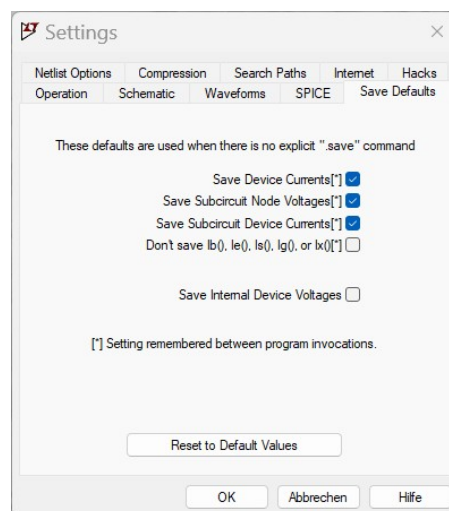


Figure D.3: Save defaults tab

Internal subcircuit quantities. Several examples inspect internal transformer fluxes, winding currents, or hierarchical node voltages. If these traces are unavailable, return to SAVE DEFAULTS and verify that the relevant subcircuit node voltages and currents are saved.

D.5.3 Schematic tab

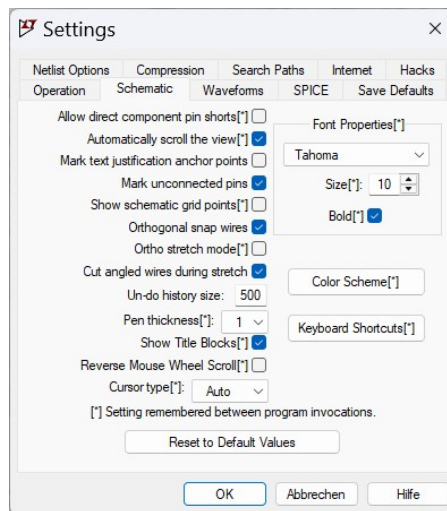


Figure D.4: Schematic tab

Set the schematic-editor font to

Arial, 10 pt, Bold.

D.5.4 Waveforms tab

Set the waveform-viewer font to

Arial, 12 pt, Data trace width=2, Cursor width=2.

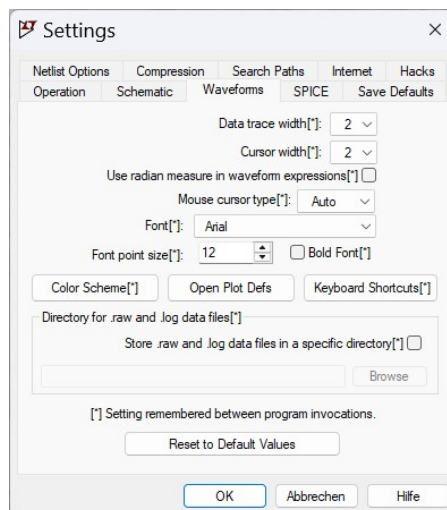


Figure D.5: Waveforms tab

D.5.5 Operation tab

Enable the following options:

- **Marching Waveforms;**
- **Generate Expanded Listing;**
- **Save all open files on start of simulation;**
- **Automatically Delete .raw Files.**

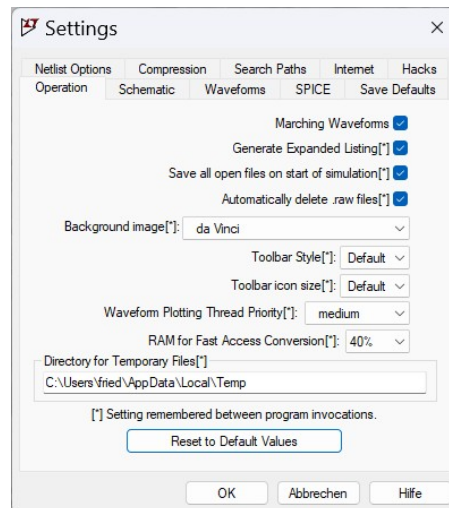


Figure D.6: Operation tab

Remark D.1 – (Automatically deleting RAW files)

RAW files from long transient simulations can become very large. Automatic deletion saves disk space after the waveform window is closed. Disable this option temporarily if a RAW file must be retained for later evaluation or shared with another user.

Table D.2: Summary of the recommended LTspice settings.

Control Panel tab	Recommended setting
Sym. & Lib. Search Paths	Add each installed toolbox folder to both the symbol and library search-path lists.
SPICE	Solver: Alternate .
Save Defaults	Enable the first three checkboxes.
Drafting Options	Arial, 10 pt, Bold.
Waveforms	Arial, 10 pt, Bold.
Operation	Enable Marching Waveforms, Generate Expanded Listing, and Automatically Delete .raw Files.

D.6 Verifying the Installation

After closing the Control Panel, restart LTspice and perform the following checks:

1. Open the component-selection dialog and verify that toolbox symbols can be selected.
2. Open one transient-toolbox example circuit.
3. Confirm that LTspice reports no missing symbol or library-file errors.
4. Run a short transient analysis.
5. Verify that the waveform viewer opens and that hierarchical quantities required by the example can be selected.
6. If the steady-state toolbox is installed, open and run one of its load-flow examples as a separate check.

Important D.3 – (If models or symbols are not found)

Check the spelling of the Windows user name, confirm the extracted folder level, and verify that the toolbox path was entered in both search-path lists. After changing a search path, restart LTspice before testing the installation again.

Appendix Summary

Install LTspice 24.0.12 with its default options, extract the transient toolbox to the user's Documents folder, and optionally install the steady-state load-flow toolbox. Add every installed toolbox folder to both the symbol and library search paths. Use the alternate solver, save the internal model data required by the examples, configure consistent schematic and waveform fonts, and enable the recommended operating options. A short example simulation should be run after installation to verify that all symbols and library models are available.

E Questions and Answers for Transient Simulation

This appendix collects practical questions that frequently arise when using the transient-simulation toolbox. The answers refer to the conventions and models used in this book.

E.1 Basic Simulation Setup

Which parameters should be present on every schematic?

The following global parameters are recommended:

```
.param tdv=1 tdt=1
.param fn1=50 omega_n={2*pi*fn1}
.options vntol=1m abstol=1u
```

Use $fn1=60$ for a 60 Hz system. The values $vntol=1m$ and $abstol=1u$ correspond to 1 mV and 1 μ A; they are included in the toolbox template `template.asc`.

For a 50 Hz to 60 Hz system, a useful maximum transient time step is between 0.1 ms and 0.6 ms. A smaller step improves temporal resolution but increases simulation time. The alternate solver is recommended under **TOOLS** → **CONTROL PANEL** → **SPICE**.

If a result is physically implausible, first check transformer orientation and all engineering prefixes. In LTspice, m means milli; use Meg for mega. A value of 400 means 400 V, not 400 kV.

How can steady state be reached quickly?

The voltage-source parameters `texp` and `tpw1` can be used to ramp the source voltage. Values between approximately 10 ms and 100 ms normally produce a final voltage buildup over roughly 50 ms to 500 ms.

Transformer energization can additionally be improved by coordinating the residual-flux parameter `psi_0` with the switching instant. For a phase-R voltage zero crossing followed by a positive voltage half-cycle:

- `psi_0=-1` can place the flux close to its steady-state path;
- `psi_0=0` can produce approximately twice rated peak flux;
- `psi_0=1` can produce approximately three times rated peak flux.

At a voltage maximum, `psi_0=0` normally gives the smallest flux offset. The exact polarity depends on the winding and voltage sign convention.

What can be done if the circuit does not converge?

Use the following sequence:

1. Verify units, polarities, initial conditions, floating nodes, and switch timing.
2. Reduce the maximum time step.

3. Use the alternate solver.
4. Provide realistic parasitic resistances and DC paths.
5. If necessary, relax `vntol`, `abstol`, or `reltol` moderately.

Increasing tolerances can help convergence but reduces numerical accuracy; repeat the final simulation with tighter tolerances as a check.

How can subcircuit currents and voltages be accessed?

Open

TOOLS → CONTROL PANEL → SAVE DEFAULTS

and enable **Save Subcircuit Node Voltages** and **Save Subcircuit Device Currents**. Restart or rerun the simulation after changing these settings.

How are power, energy, and current direction displayed?

Hold ALT and click a component to plot its instantaneous power, based on the voltages and currents at its pins. Hold CTRL and click the power trace label to integrate the trace over the displayed interval and obtain energy.

LTspice defines device-pin currents as positive into the pin. Resistors, capacitors, and inductors display a current arrow. Mirroring a symbol also mirrors this reference direction.

What must be considered for LTspice inductors?

LTspice inductors may contain a default series resistance of 1 mΩ. Right-click the inductor and set `Rser=0` if an ideal inductor is required. The global default can be changed under TOOLS → CONTROL PANEL → HACKS by enabling the option that defaults inductors to `Rser=0`.

Removing all loss can create an undamped resonant circuit and may worsen convergence. Use a physically meaningful resistance whenever possible.

E.2 Transformer Models and Magnetic Quantities

How is a nonlinear transformer changed to a linear model?

Right-click the transformer and set

`m=1`

in the value or parameter field. This removes the high-order nonlinear term in the toolbox magnetization characteristic.

Which parameters determine the magnetization curve?

The characteristic is controlled primarily by a and m :

$$i_{\mu}(\Phi) = I_{\mu N} \left[a \frac{\Phi}{\Phi_N} + (1 - a) \left(\frac{\Phi}{\Phi_N} \right)^m \right]. \quad (\text{E.1})$$

The parameter a determines the linear share and the small-signal slope, while m controls the sharpness of saturation. Typical large-transformer examples use $m = 7$ or $m = 9$. Example curves are available in `Magnetisierungskurven_different_xxx.asc`.

The quantities $I_{\mu N}$ and Φ_N must use the same amplitude convention. If peak flux is used, the rated peak values are

$$\Phi_N = \frac{\sqrt{2} U_{N,\text{ph}}}{\omega N}, \quad I_{\mu N} = \sqrt{2} I_{\mu N,\text{rms}}. \quad (\text{E.2})$$

How is residual flux specified?

Use the transformer parameter `psi_0` for a predefined residual-flux pattern. Where supported, phase-specific parameters should be used for an arbitrary residual-flux vector. The initialization time must match the desired switching event.

How is residual flux applied at an arbitrary time?

The model briefly connects an initialization voltage source to the 1 F flux-integrator capacitor. The switch on-resistance and duration determine the charging accuracy:

$$\tau = R_{\text{on}} C. \quad (\text{E.3})$$

For example,

$$R_{\text{on}} = 10^{-5} \Omega, \quad C = 1 \text{ F} \implies \tau = 0.01 \text{ ms}. \quad (\text{E.4})$$

A closing duration of 0.1 ms corresponds to 10τ and charges the capacitor essentially to its final value. The rapid initialization can produce a narrow voltage or current spike at the charging instant.

Where can introductory LTspice tutorials be found?

An introductory tutorial collection is available at http://www.simonbramble.co.uk/ltspice/ltspice_ltspice.htm.

How is the JUSTUS transformer model composed?

The model combines an electrical circuit with a magnetic equivalent circuit. Iron loss, leakage, and core paths can therefore be represented with magnetic quantities. Under the magnetic-electrical duality used in the model:

- electrical series connections correspond to magnetic parallel paths;

- electrical parallel connections correspond to magnetic series paths;
- resistance corresponds to conductance under the chosen analogy;
- voltage-source and current-source roles are interchanged;
- T and Π topologies are dual representations.

For a winding with N turns,

$$\mathcal{R}_\sigma = \frac{N^2}{L_\sigma}, \quad (\text{E.5})$$

$$\mathcal{R}_{\text{Fe}} = \frac{N^2}{R_{\text{Fe}}}, \quad (\text{E.6})$$

according to the scaling convention of the toolbox model. The placement of the corresponding branches follows the electrical-magnetic duality described above.

How can approximate data for a 300 MV A transformer be estimated?

Assume a 400 kV/120 kV Yy transformer, $N_1 = 1000$, magnetic path length $l_m = 10$ m, rated flux density $B_N = 1.8$ T, and RMS magnetizing current $I_{\mu N} = 0.5$ A.

Using RMS sinusoidal quantities,

$$\Psi_{1N,\text{rms}} = \frac{U_{1N,LL}}{\sqrt{3} \omega} = 735.1 \text{ Wb}, \quad (\text{E.7})$$

$$\Phi_{N,\text{rms}} = \frac{\Psi_{1N,\text{rms}}}{N_1} = 0.735 \text{ Wb}, \quad (\text{E.8})$$

$$A_{\text{Fe}} = \frac{\Phi_{N,\text{rms}}}{B_N} \approx 0.408 \text{ m}^2, \quad (\text{E.9})$$

$$\Theta_{\mu N} = N_1 I_{\mu N} = 500 \text{ A}, \quad (\text{E.10})$$

$$H_N = \frac{\Theta_{\mu N}}{l_m} = 50 \text{ A/m}, \quad (\text{E.11})$$

$$\mu_r = \frac{B_N}{\mu_0 H_N} \approx 2.86 \times 10^4, \quad (\text{E.12})$$

$$\mathcal{R}_m = \frac{\Theta_{\mu N}}{\Phi_{N,\text{rms}}} \approx 680/\text{H}, \quad (\text{E.13})$$

$$L_{1h} = \frac{N_1^2}{\mathcal{R}_m} \approx 1470 \text{ H}. \quad (\text{E.14})$$

The equivalent peak convention gives $\hat{\Phi}_N = \sqrt{2} \Phi_{N,\text{rms}} = 1.0396 \text{ Wb}$ and $\hat{I}_{\mu N} = \sqrt{2} I_{\mu N}$, leaving reluctance and inductance unchanged. RMS and peak quantities must not be mixed in one calculation.

What does the nonlinear curve predict at one, two, and three times rated flux?

For $a = 0.75$, $m = 9$, and a reference current of $I_{\mu N} = 0.5$ A in a consistent amplitude convention,

$$i_{\mu}(1\Phi_N) = 0.5 \text{ A}, \quad (\text{E.15})$$

$$i_{\mu}(2\Phi_N) = 64.75 \text{ A}, \quad (\text{E.16})$$

$$i_{\mu}(3\Phi_N) = 2\,461.5 \text{ A}. \quad (\text{E.17})$$

For $l_m = 10$ m and $B_N = 1.8$ T, the corresponding approximate magnetic quantities are

Φ/Φ_N	B	H	μ_r	L_{1h}
1	1.8 T	50 A/m	2.86×10^4	1 470 H
2	3.6 T	6 475 A/m	442	22.7 H
3	5.4 T	$2.46 \cdot 10^5$ A/m	17.5	0.90 H

These are point estimates based on the assumed algebraic curve. In a dynamic simulation, winding voltage drop, leakage flux, and waveform distortion reduce the effective flux and RMS current. Even at three times rated flux, the estimated main inductance remains above the example leakage inductance $L_{\sigma} \approx 0.1697$ H.

How can tank reluctance be estimated?

The tank path is strongly geometry- and frequency-dependent. A placeholder inductance of a few henries, or roughly 10 to 100 times the winding leakage inductance, may be useful for sensitivity studies, but it is not a validated transformer parameter. Measurements or field calculations are required for an accurate value.

How can transformer voltage and phase be regulated?

The rudimentary tap parameter `1_` changes the voltage in steps. For example, `1_=3` and `stproz=1.5` correspond to a nominal 4.5 % change, subject to the model sign convention.

The models `trafo_tap_1` and `trafo_tap_s` provide voltage and phase-angle regulation. Versions with fixed parameters and versions with control pins are available; the latter can be driven by a PWL source during a transient simulation.

E.3 Selecting and Analysing Models

How are alternative models selected?

Right-click the element and open the **SpiceModel** drop-down list. It contains compatible models from the associated `.lib` file. The model pin count and pin order must match the symbol. Examples include `1`, `1_int`, and `1_flux`.

How is a transient model converted to AC analysis?

Replace transient sources by sources with AC magnitude and phase definitions, and replace the `.tran` directive by an `.ac` directive. AC analysis linearizes the circuit about its operating point; it is generally not suitable for studying switching events or strongly nonlinear large-signal behaviour.

How can reactive-power transfer be recognized?

Reactive-power transfer produces a phase displacement between the fundamental voltage and current. For sinusoidal RMS phasors,

$$Q = \sqrt{3} U_{LL} I_L \sin \varphi. \quad (\text{E.18})$$

For distorted waveforms, calculate average active power from $u(t)i(t)$ and use a harmonic-aware definition of reactive power.

Why do many elements have control pins?

Control pins allow parameters such as voltage level, tap position, phase shift, switch state, or model coefficient to change during the simulation. A PWL source is commonly used to drive a discrete or continuous control input.

E.4 Inductive Coupling and Flux

How is leakage between two coupled inductors calculated?

For self-inductances L_1, L_2 and mutual inductance M ,

$$k = \frac{M}{\sqrt{L_1 L_2}}, \quad (\text{E.19})$$

$$\sigma = 1 - \frac{M^2}{L_1 L_2} = 1 - k^2. \quad (\text{E.20})$$

If the individual leakage factors are σ_1 and σ_2 ,

$$\sigma = \sigma_1 + \sigma_2 - \sigma_1 \sigma_2. \quad (\text{E.21})$$

For a symmetric transformer, $\sigma_1 = \sigma_2$, hence

$$\sigma = 2\sigma_1 - \sigma_1^2, \quad k = 1 - \sigma_1, \quad L_{1\sigma} = (1 - k)L_1. \quad (\text{E.22})$$

With $L_{1\sigma} = 0.1697 \text{ H}$ and $L_1 = 1470 \text{ H}$,

$$\sigma_1 = 1.1544 \times 10^{-4}, \quad (\text{E.23})$$

$$\sigma = 2.3087 \times 10^{-4}, \quad (\text{E.24})$$

$$k = \boxed{0.9998846}. \quad (\text{E.25})$$

The voltage ratio and inductances satisfy

$$\frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}} \quad (\text{E.26})$$

when both inductances use the same magnetic path and reference convention.

What is the rated peak flux for 1000 turns?

For sinusoidal phase voltage $U_{N,\text{ph}}$,

$$\hat{\Psi}_N = \frac{\sqrt{2} U_{N,\text{ph}}}{\omega}, \quad \hat{\Phi}_N = \frac{\hat{\Psi}_N}{N}. \quad (\text{E.27})$$

At 50 Hz and $N = 1000$:

Voltage applied to winding	Connection interpretation	$\hat{\Phi}_N$
10 kV/ $\sqrt{3}$	10 kV star phase	0.026 0 Wb
10 kV	Winding voltage	0.045 0 Wb
20 kV/ $\sqrt{3}$	20 kV star phase	0.052 0 Wb
20 kV	Winding voltage	0.090 0 Wb
110 kV/ $\sqrt{3}$	110 kV star phase	0.286 Wb
110 kV	Winding voltage	0.495 Wb
220 kV/ $\sqrt{3}$	220 kV star phase	0.572 Wb
220 kV	Winding voltage	0.990 Wb
400 kV/ $\sqrt{3}$	400 kV star phase	1.039 6 Wb

What are the time constants of RL and RC circuits?

$$\tau_{RL} = \frac{L}{R}, \quad \tau_{RC} = RC. \quad (\text{E.28})$$

A first-order response reaches approximately 99.3 % of its final change after 5τ and 99.995 % after 10τ .

What do tpsid and ron mean?

The parameter tpsid specifies how long the initialization source is connected to the 1 F flux-integrator capacitor. The parameter ron is the switch on-resistance. Suitable example values are

```
tps id=0.1m ron=1e-5
```

giving $\tau = R_{\text{on}}C = 0.01$ ms and an initialization interval of 10τ .

How can the magnetization curve be plotted?

Open the transformer secondary. In the waveform viewer, change the horizontal axis from time to primary current and plot internal flux or flux linkage versus that current. A nonzero iron-loss parameter $p0$ produces a loop-like separation because the loss current is superimposed; it should not be confused with a fully physical hysteresis model unless the model explicitly contains hysteresis state equations.

E.5 Lines, Cables, and Compensation

How is cable charging power calculated?

For line-to-line RMS voltage U_N , phase-to-earth capacitance C_E , and phase-to-phase capacitance C_L per phase set,

$$Q_0 = Q_{CE} + Q_{CL} = U_N^2 \omega C_E + 3U_N^2 \omega C_L, \quad (\text{E.29})$$

$$I_0 = \frac{Q_0}{\sqrt{3}U_N}. \quad (\text{E.30})$$

For a shielded single-core cable, C_L is commonly negligible and $Q_0 \approx Q_{CE}$. The capacitive earth-fault current is then approximately

$$I_E = 3I_0 = \frac{3Q_{CE}}{\sqrt{3}U_N}. \quad (\text{E.31})$$

How are Petersen coils and shunt reactors dimensioned?

For a Petersen coil connected from the transformer neutral to earth,

$$X_L = \frac{U_N/\sqrt{3}}{I_N}, \quad L = \frac{X_L}{\omega}. \quad (\text{E.32})$$

For an example with $U_N = 110$ kV and $I_N = 250$ A, the coil loss may initially be estimated with $R \approx X_L/100$ and later replaced by measured data.

For a three-phase reactor with total rating Q_N :

$$L_\Delta = \frac{3U_N^2}{\omega Q_N}, \quad (\text{E.33})$$

$$L_Y = \frac{U_N^2}{\omega Q_N}. \quad (\text{E.34})$$

Each delta branch sees U_N , whereas each star branch sees $U_N/\sqrt{3}$.

If $C_E = 1\,000\text{ nF}$ at 110 kV ,

$$Q_0 = U_N^2 \omega C_E \approx 3.80\text{ Mvar}, \quad (\text{E.35})$$

$$I_0 = \frac{Q_0}{\sqrt{3}U_N} \approx 19.95\text{ A}, \quad (\text{E.36})$$

$$I_E = 3I_0 \approx 59.85\text{ A}. \quad (\text{E.37})$$

A Petersen coil rated approximately 110 kV and 60 A therefore provides the required compensation.

How does coupling influence parallel lines?

Lines on the same route have mutual inductive and capacitive coupling. Depending on current direction and phase arrangement, mutual induction can reduce or increase the effective series inductance. In the idealized same-direction case, $k \rightarrow 1$ makes the differential leakage inductance approach zero.

The toolbox contains coupled-line models for one, two, and four circuits. Their coupling matrices were calculated with ATP/ATPDraw and converted to LTspice format with the supplied conversion tools.

How is source impedance obtained from short-circuit power?

For a balanced three-phase network,

$$Z_N = \frac{U_N^2}{S_k}. \quad (\text{E.38})$$

Examples are

$$U_N = 400\text{ kV}, \quad S_k = 40\text{ GV A} \Rightarrow Z_N = 4.0\ \Omega, \quad (\text{E.39})$$

$$U_N = 110\text{ kV}, \quad S_k = 7.5\text{ GV A} \Rightarrow Z_N = 1.613\ \Omega. \quad (\text{E.40})$$

If no resistance information is available, the first approximation is an inductive source impedance jX_N with $X_N \approx Z_N$.

How is the total capacitance of an overhead line calculated?

With phase-to-earth capacitance C_E and phase-to-phase capacitance C_L , the effective positive-sequence charging capacitance is

$$C_{\text{sum}} = C_E + 3C_L. \quad (\text{E.41})$$

The capacitive reactive power is

$$Q_C = U_N^2 \omega C_{\text{sum}} = \frac{U_N^2}{X_C}. \quad (\text{E.42})$$

How is the reactive power of a shunt reactor calculated?

For a balanced three-phase reactor connected in star,

$$Q_L = \frac{U_N^2}{X_L} = \frac{U_N^2}{\omega L}, \quad (\text{E.43})$$

where L is the inductance of each phase branch.

What is the difference between equal star and delta loads?

If the same branch resistance or impedance is used in both connections at the same line-to-line voltage, each delta branch receives $\sqrt{3}$ times the star branch voltage. Therefore,

$$P_\Delta = 3P_Y, \quad Q_\Delta = 3Q_Y. \quad (\text{E.44})$$

E.6 Plot Files and Verification

How is a saved plot configuration displayed?

Many examples include saved plot-setting files. In the waveform viewer, use PLOT SETTINGS → OPEN PLOT SETTINGS and select the required file. If several configurations are supplied, open them one at a time to reproduce the intended trace groups.

How should a transient simulation be verified?

Always repeat the simulation with a smaller maximum time step. A credible result should change only slightly as the time step is reduced. Also check:

- energy and power balance;
- expected steady-state RMS values and phase sequence;
- sensitivity to tolerances and parasitic resistances;
- agreement between transient, AC, and hand calculations where applicable;
- correct current reference directions and voltage bases;
- plausibility of resonant frequencies and decay time constants.

Appendix Summary

Reliable transient simulation begins with consistent global parameters, correct units, suitable time steps, and physically meaningful damping. Source ramps and coordinated residual flux reduce initialization transients, while the alternate solver and carefully selected tolerances improve numerical robustness. Transformer calculations must use consistent RMS or peak conventions, and coupled-line and compensation studies require correct three-phase voltage bases. Every important result should be repeated with a smaller time step and compared

with analytical estimates.

F LTspice Schematic Editor: Menu Bar, Toolbar, and Basic Operation

Version note This overview refers to the Windows schematic editor used in LTspice 24.0.12. The illustration shows the default LTspice 24 toolbar. Users who prefer the older, smaller icon set can select the legacy toolbar with TOOLS → SETTINGS → OPERATION → TOOLBAR STYLE → LEGACY.

F.1 Main Areas of the Schematic Editor

1. Menu bar

The menu bar provides access to all drawing, simulation, display, and program configuration commands. A toolbar icon is available only for the most commonly used commands.

2. Toolbar

The toolbar gives direct access to frequently used commands such as opening a schematic, starting a simulation, inserting components, drawing wires, and editing circuit elements. Moving the mouse pointer over an icon displays its function as a tooltip.

3. Drawing area

Components, wires, node labels, comments, and SPICE directives are placed in the drawing area. The electrical reference node must be the ground node named 0. A schematic without node 0 normally cannot be simulated.

F.2 Menu Bar

Menu	Purpose
File	Creates, opens, closes, saves, and prints schematic files. It also provides access to recently used files and program exit.
Edit	Contains undo and editing operations such as delete, duplicate, move, stretch, rotate, mirror, search, and selection commands.
Hierarchy	Creates and manages hierarchical blocks, symbols, ports, and multi-level schematics.
View	Controls zoom, grid, anchors, unconnected-pin markers, netlist display, SPICE error log, and other schematic or waveform views.
Simulate	Starts, pauses, or stops a simulation and opens the dialog for defining transient, AC, DC, noise, and operating-point analyses.
Tools	Opens program settings and provides component, symbol, and library management functions.
Window	Selects and arranges open schematic, waveform, and text windows.
Help	Opens the LTspice documentation, keyboard-shortcut information, and version information.

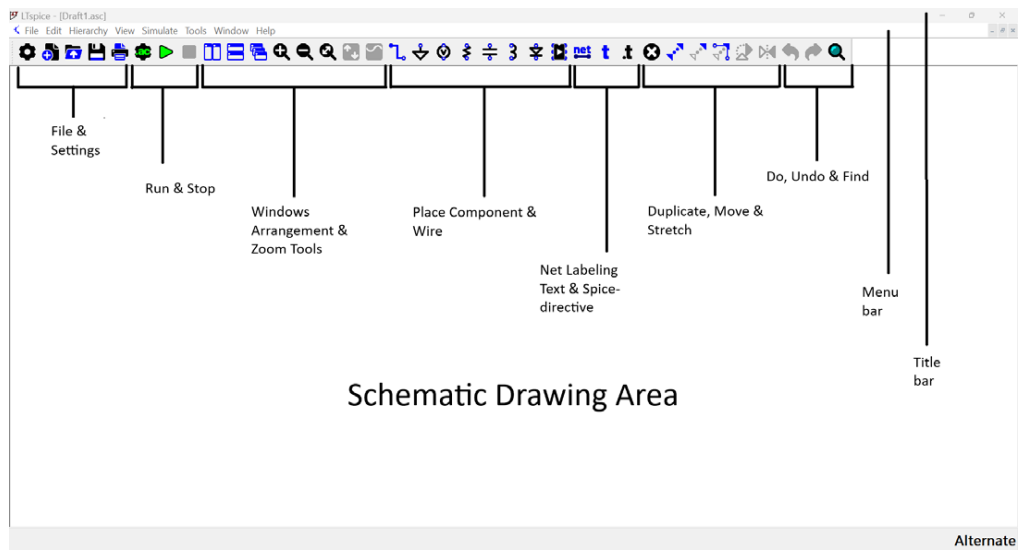


Figure F.1: Annotated LTspice 24 schematic-editor window showing the title and menu bars, functional toolbar groups, schematic drawing area, grid, and status bar. The appearance of individual icons depends on the selected toolbar style and LTspice version.

F.3 Toolbar Symbols

Command	Shortcut	Function
New Schematic	Ctrl+N	Creates a new empty schematic.
Open	Ctrl+O	Opens an existing schematic or supported LTspice file.
Save	Ctrl+S	Saves the active schematic.
Control Panel / Settings	---	Opens the general LTspice configuration.
Run	---	Starts the selected simulation.
Stop / Halt	---	Stops the active simulation.
Zoom Area	Ctrl+Z	Enlarges a rectangular part of the schematic.
Zoom Back	Ctrl+B	Returns to the preceding zoom level.
Zoom to Fit	Space	Fits the complete schematic into the window.
Wire	F3	Draws an electrical connection between nodes.
Ground	G	Places the mandatory reference node 0.
Label Net	F4	Assigns a name to a node or electrical network.
Component	F2	Opens the component and symbol selection dialog.
Resistor	R	Places a resistor.
Capacitor	C	Places a capacitor.
Inductor	L	Places an inductor.
Diode	D	Places a diode.
SPICE Directive	S	Places commands such as <code>.tran</code> , <code>.param</code> , <code>.options</code> , or <code>.measure</code> .
Text Comment	T	Places explanatory text without electrical effect.
Delete	F5	Deletes selected components, wires, labels, or text.
Duplicate / Copy	F6	Creates a copy of the selected object.
Move	F7	Moves an object; connected wires are not stretched with it.
Stretch / Drag	F8	Moves an object while retaining and adapting its wires.
Rotate	Ctrl+R	Rotates the selected component by 90 degrees.
Mirror	Ctrl+E	Mirrors the selected component.
Undo	F9*	Reverses the last editing action.

* The effective shortcut can depend on the active window and the configured hotkeys. LTspice displays the currently assigned keys in its menus and tooltips.

F.4 Basic Workflow

Creating and simulating a circuit

1. Create or open a schematic.
2. Insert the required components and assign their parameters.
3. Connect the circuit with the WIRE tool.
4. Insert ground node 0 and assign useful net labels.
5. Define the simulation with SIMULATE → CONFIGURE ANALYSIS or place the corresponding SPICE directive directly on the schematic.

6. Press RUN and select node voltages or branch currents in the waveform viewer.

Move and Stretch MOVE changes the position of a component without preserving the exact wire geometry. STRETCH moves the component together with its connected wires. Press Esc or the right mouse button to leave an active editing mode.

F.5 References

- Analog Devices, “[LTspice Basics: Schematic Capture](#).”
- Analog Devices EngineerZone, information about the LTspice 24 toolbar and the legacy toolbar style, “[Toolbar is Incomplete](#).”
- Interface illustration adapted from the LTspice schematic-entry tutorial by LEnSE, Institut d’Optique Graduate School, “[LTspice: Schematic Entry](#).”

Most used devices/symbols

	V_3phase.asy sources.lib	Three phase voltage source with optional exponential or linear swingin		sg.asy sgen.lib	Synchronous generator round pole: Schenkelpolfaktor~1 Kc~0.4-0.65 salient pole: Schenkelpolfaktor~0.5 Kc~0.8-1
	Line_special.asy Line.lib	Overhead line and cable uncoupled, transposed		trafo_Yd.asy trafo_Yd.lib	Transformers with different vector groups Yd,Dy,Yy,Yz
	Line2.asy Line2.lib	Overhead line and cable coupled, transposed, distributed or lumped		Pet.asy comp.lib	Petersen coil for earth fault compensation
	Line2_coupled Line_coupled.lib	Coupled Overhead line lumped, untransposed		trafo_gnd.asy trafo_gnd.lib	Artificial external starpoint To use for Yd Dy transformers
	Line_cable_shield.asy Line_coupled.lib	Coupled cable with shield lumped, untransposed		Switcher.asy Switcher.lib	Switcher initially open
	Load_d.asy Load.lib	Delta Load R,L,C		Switcher_off.asy Switcher.lib	Switcher initially closed
	Load_y.asy Load.lib	Wye Load R,L,C		Fault_earth.asy Switcher.lib	Earth fault switcher
	impedance.asy	Impedance with R,L		Fault_earth_1phase.asy Switcher.lib	Earth fault switcher one phase
	impedance_sk.asy impedance.lib	Impedance with sk (short circuit capacity)		isolator.asy isolator.lib	Isolator
	Lbatt.asy comp.lib	Shunt reactance for voltage regulation		bus_veff.asy measure.lib	Bus measurement VRMS L-L phase A,B,C
	Cbatt.asy comp.lib	Capacitor bank for voltage regulation		bus_veff_phase.asy measure.lib	Bus measurement VRMS L-L, L-N, Phaseangle Phase A
	v/a/p/q/s-meter.asy measure.lib	RMS-Metering devices			

Figure F.2: Most used symbols for transient toolbox

I've developed in the past about 25 years many macromodels for the LTSpice simulator. This resulted in the development of two toolboxes for nonlinear loadflow computation and transient simulation of high energy networks. I think that i was the first who adapt a spice simulator for doing nonlinear loadflow computation. My two toolboxes are for didactic use and dedicated especially to all studying electrical engineering. The sources of the Toolboxes are free and comes with hundreds of examples. This book concentrates of the simulation of transient behavior of high energy electrical networks

The Ltspice toolbox includes all important power grid elements for doing transient circuit simulation like: Voltage sources, synchronous generators with saturation, nonlinear transformers with hysteresis, initial residual flux and with phase regulation, inductive coils for earth fault compensation, shunt reactors, loads, overhead lines and cables, coupled lines, starpoint builder transformer, surge arresters and many others

LTSpice is a simulator from Analog Devices which you can download also for free use. Since i was for more than 35 years load dispatcher in the Viennese power distribution board I could collect some experience which i put into the development of the two toolboxes. I hope that you will (like me) enjoy simulating high energy networks which is sometimes tricky. Good luck!

Index

- behavioral source, 119
- cable
 - energization, 23
- controlled source, 119
- coupled lines, 81
- earth fault, 33
- inductive compensation, 81
- inrush current, 17
- line switching, 23
- line transposition, 81
- LTspice
 - behavioral source, 119
 - installation, 125
 - schematic editor, 145
 - toolbar, 145
 - troubleshooting, 133
- medium-voltage grid, 7
- network energization, 51
- neutral displacement voltage, 33
- Petersen coil, 23, 33
- remanent flux, 17
- resonance
 - parallel overhead lines, 81
- resonant grounding, 33
- short-circuit current, 7
- short-circuit reactor, 9
- shunt reactor, 1
- switching overvoltage, 51
- toolbox
 - load-flow simulation, 125
 - transient simulation, 125
- transformer, 1
 - inrush current, 51
 - parallel operation, 7
 - residual flux, 17
- transient simulation
 - questions and answers, 133
- voltage ramp, 51

About the Author

Friedrich Schmidt works since about 25 years on practical modelling and simulation of electrical power systems. You can contact him by mail: friedrich-schmidt@gmx.at The Itspice toolboxes can be downloaded from the website: www.friedrichschmidt.at and from the Itspice usergroup at https://groups.io/g/LTspice/files/z_yahoo/adventures_with_loadflow after signing in

About this book

A practical introduction for everyone interested in the simulation of high-voltage electrical power networks.

Over the past 25 years, I have developed two educational toolboxes for LTspice. The first supports nonlinear load-flow calculations; the second is designed for the transient simulation of electrical power networks.

The toolboxes contain the essential components required to build realistic power-system models:

- buses and sources;
- synchronous machines and transformers;
- overhead lines and power cables;
- loads and shunt reactors; and
- surge-protection devices, Petersen coils, and many other elements.

Some elements provide parameters that can be changed directly by the user. Others are supplied with carefully selected presets, which can also be overwritten whenever a study requires different values.

The transformer library ranges from simple models to sophisticated representations with a nonlinear iron core, hysteresis, and remanent flux. Eight vector groups and voltage levels from 400 kV down to 400 V are included. Additional vector groups can be created by editing the macro-models, because all `.lib` files are freely accessible and editable.

Hundreds of examples for both toolboxes are available on my website, ranging from simple introductory circuits to complex networks. Many schematic files contain their own documentation, and the first eight examples are explained in detail in this book.

These toolboxes are especially dedicated to students of electrical engineering, but they are equally useful to teachers, engineers, and anyone who wants to explore power-system behaviour through simulation.

I hope you enjoy experimenting with these simulations as much as I do. Your feedback is always welcome.