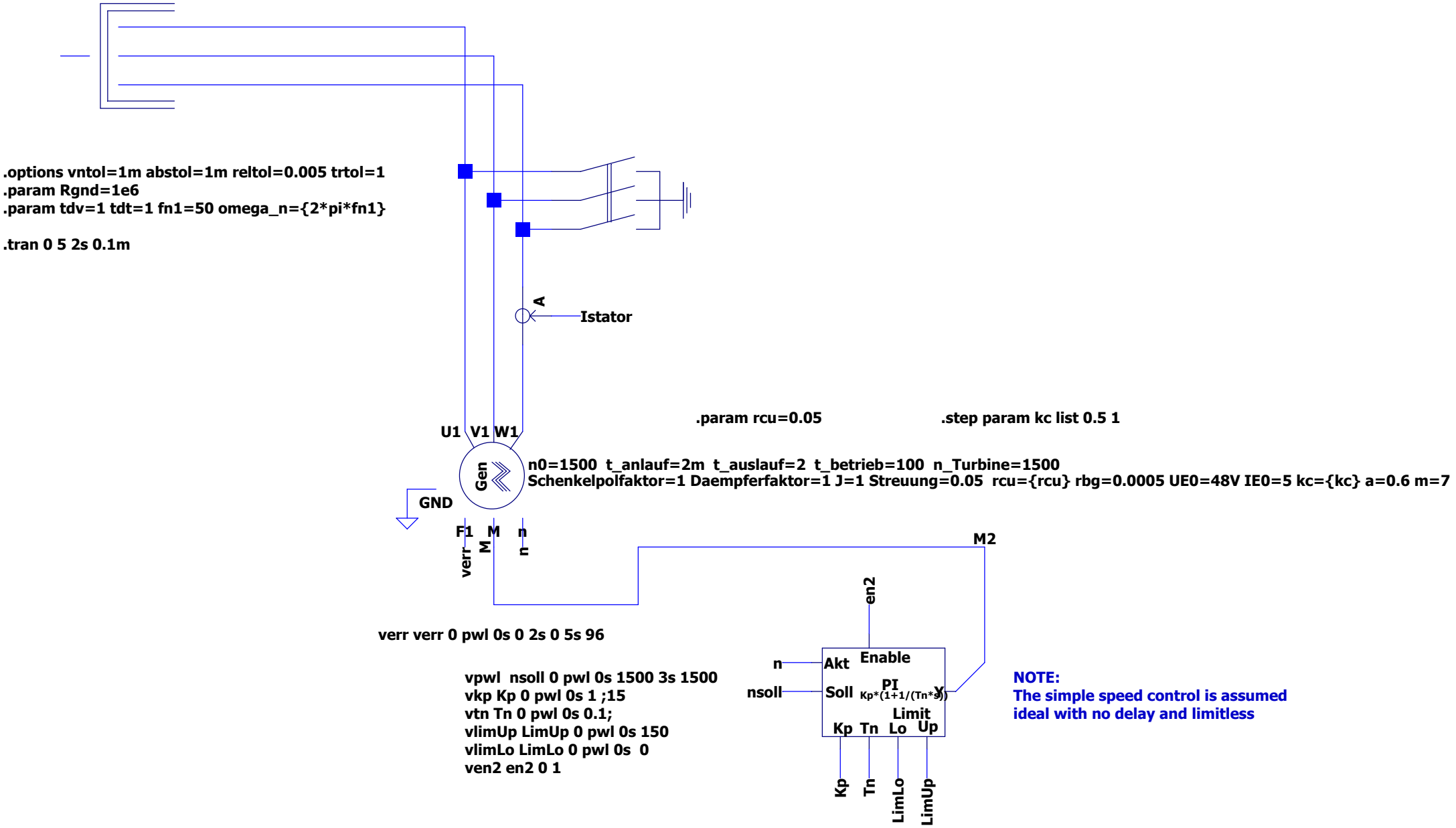Measurement of the short circuit line of the generator I1=f(IE)